

chapter3_4 Transistor Circuits for analyzing JFET Q-point conditions.

```
% Onwubolu, G. C.
% Mechatronics: Principles & Applications
% Elsevier
%
% Mechatronics: Principles & Applications Toolbox Version 1.0
% Copyright © 2005 by Elsevier
%
% Chapter 3.6: Transistor Circuits
%
% Example Example 3.4  MATLAB's calculating power is demonstrated by
analyzing
% JFET Q-point conditions.

'Example 3.4'          % Display label.
% JFET Q-point conditions
Vdd=24;
Vds=12;
Vp=4;
Idss=8E-3;
Id=5E-3;
Rd=1E+6;

% Commence computation
D=Idss/Id;
C=D-1;
B=2*D/Vp;
A=D/Vp^2;
%Solve quadratic equation
Vs=[A B C];          % Of the form A*Vs^2+B*Vs+C=0
V=roots(Vs)          % Find the roots
if V(1)>-Vp          % Check constraints
    Rs=abs(V(1))/Id
else Rs=abs(V(2))/Id
end
pause
```