

## **chapter5\_4** analyzing difference op-amps

```
% Onwubolu, G. C.  
% Mechatronics: Principles & Applications  
% Elsevier  
%  
% Mechatronics: Principles & Applications Toolbox Version 1.0  
% Copyright © 2005 by Elsevier  
%  
% Chapter 5: Operational amplifiers  
%  
% Example 5.4 MATLAB's calculating power is demonstrated by analyzing  
% difference op-amps  
  
'Example 5.4' % Display label.  
% op-amps  
R1=5E+3;  
R2=15E+3;  
V1=15;  
V2=10;  
  
% Commence computation  
'Gain:'  
G=R2/R1 %Vout/Vi=G  
'Output voltage'  
Vout=(V1-V2)*G  
pause
```