

Chapter 7

Logic Diagnosis

Outline




- **Introduction**
- **Combinational Logic Diagnosis**
- **Scan Chain Diagnosis**
- **Logic BIST Diagnosis**
- **Conclusion**

What would you do when chips fail?

- **Is it due to design bugs?**
 - **If most chip fails with the same syndrome when running an application**
- **Is it due to parametric yield loss?**
 - **Timing-related failure?**
 - Insufficient silicon speed?
 - **Noise-induced failure?**
 - supply noise, cross-talk, leakage, etc.?
 - **Lack of manufacturability?**
 - inappropriate layout?
- **Is it due to random defects?**
 - **Via misalignment, Via/Contact void, Mouse bite,**
 - **Unintentional short/open wires, etc.**

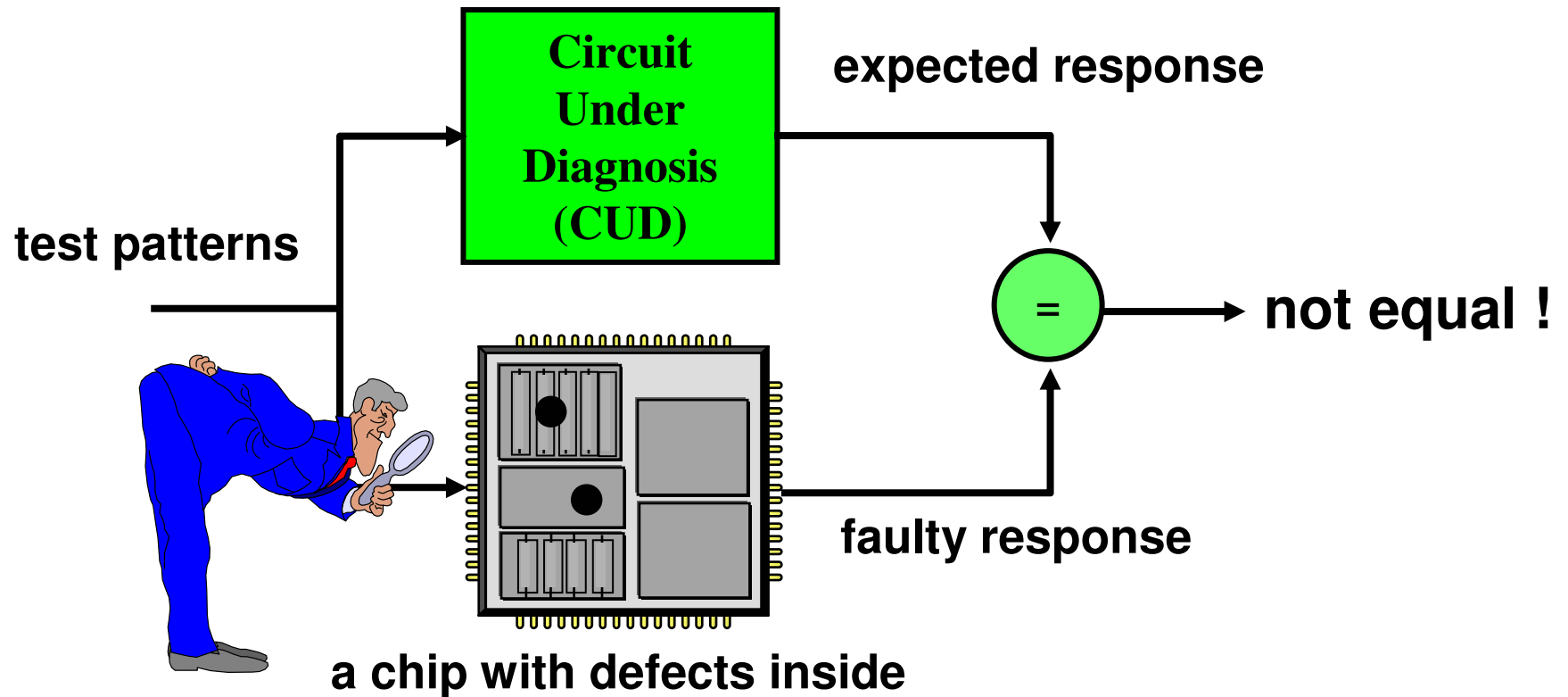
Problem: Fault Diagnosis

This chapter focuses more on diagnosis of defects or faults, not design bugs



Question: Where are the fault locations ?

Diagnosis For Yield Improvement

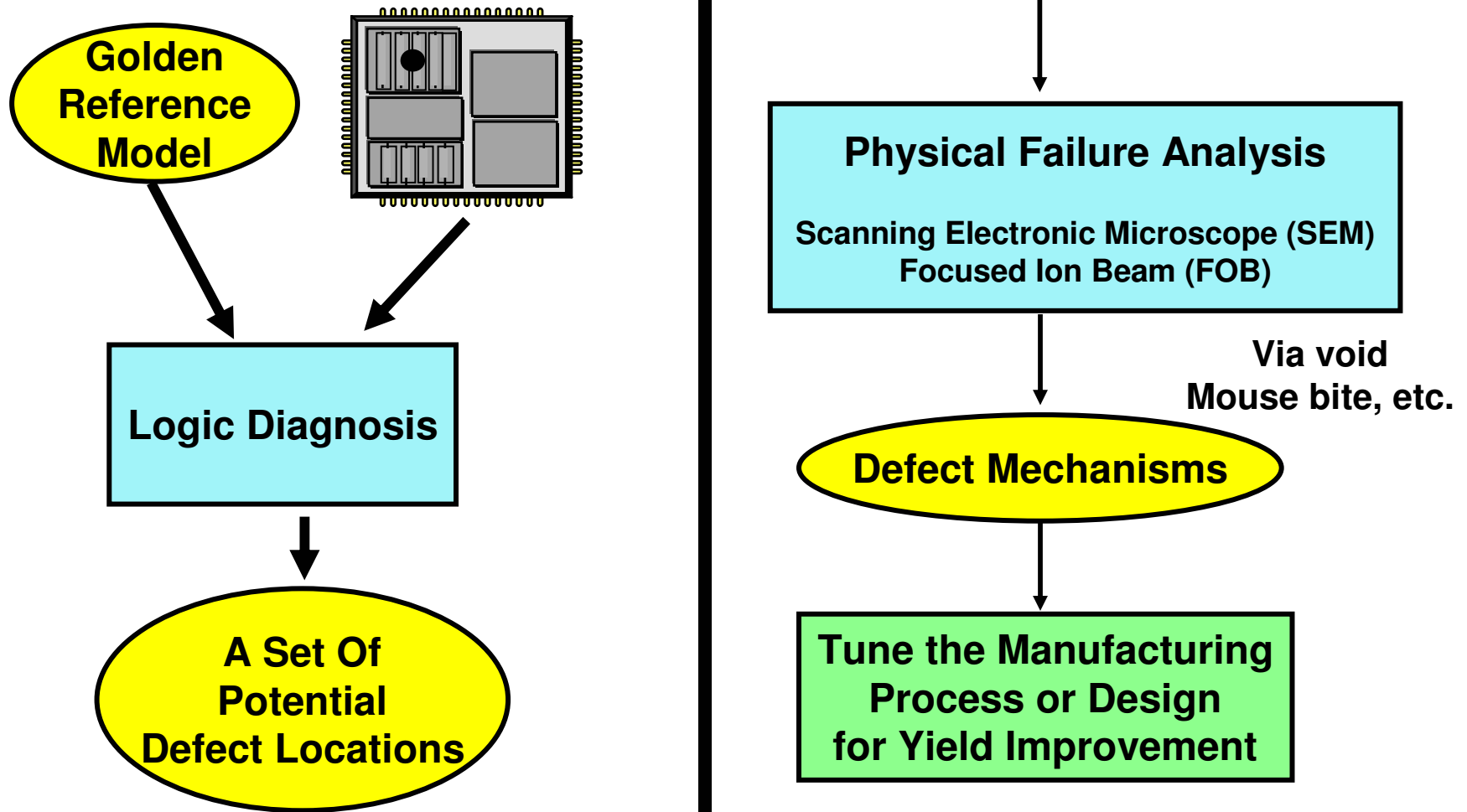

Quality Metrics of Diagnosis

- ❑ **Success rate**
 - The percentage of hitting at least one defect in the physical failure analysis
 - This is the ultimate goal of failure analysis
- ❑ **Diagnostic resolution**
 - Total number of fault candidates reported by a tool
 - The perfect diagnostic resolution is 1
 - Though perfect resolution does not necessarily imply high hit rate
- ❑ **First-hit index**
 - Used for a tool that reports a ranked list of candidates
 - Refers to the index of the first candidate in the ranked list that turns out to be a true defect site
 - Smaller first-hit index indicates higher accuracy
- ❑ **Top-10 hit**
 - Used when there are multiple defects in the failing chip
 - The number of true defects in the top 10 candidates

Challenge

Do whatever you want,
but give me that damn
bug(s) in **less than 5**
candidates.




**failure analysis people
under time-to-market pressure**


Supporting Circuitry

Supporting Circuitry:

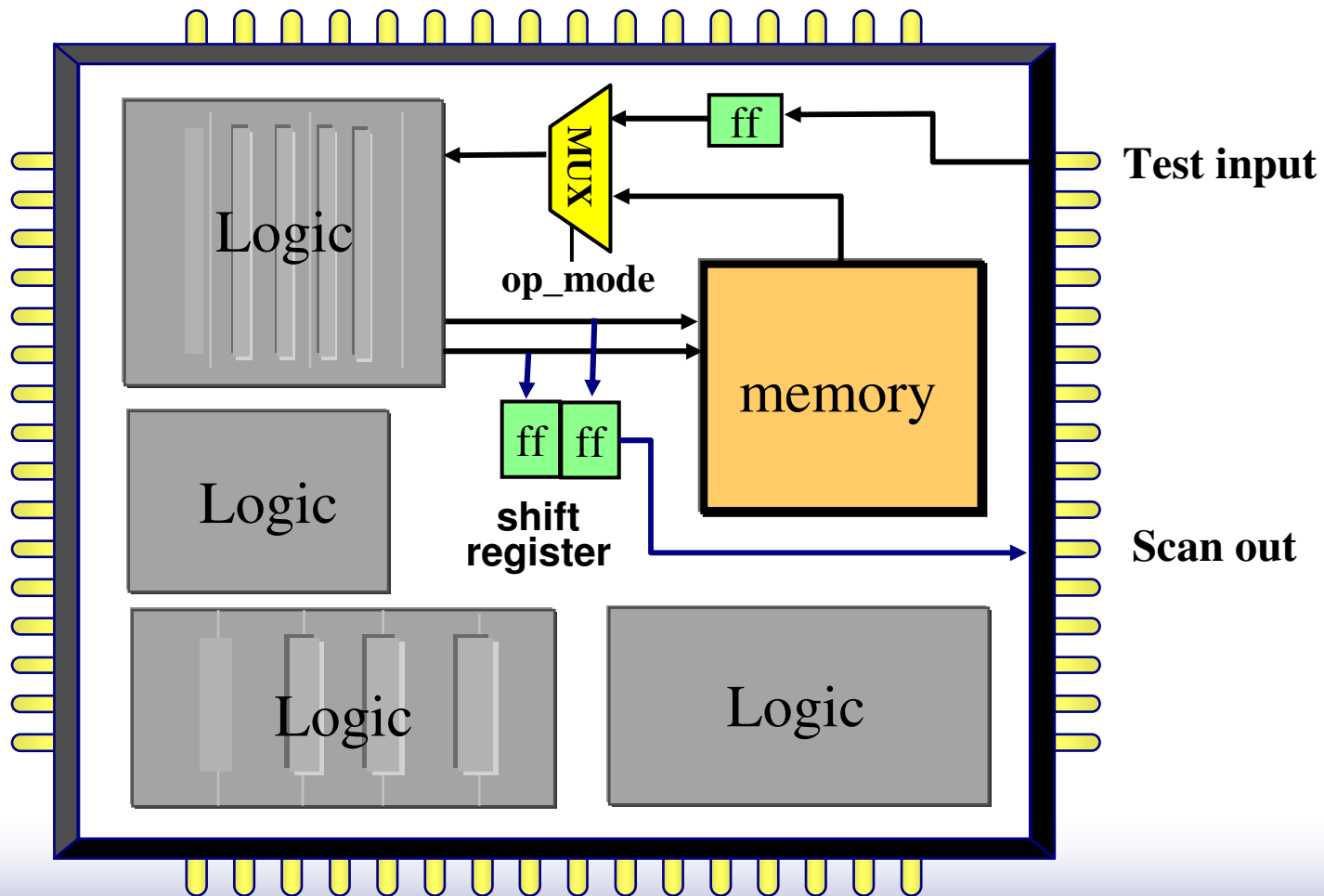Makes Logic's inputs controllable and outputs observable



Design For Diagnosis

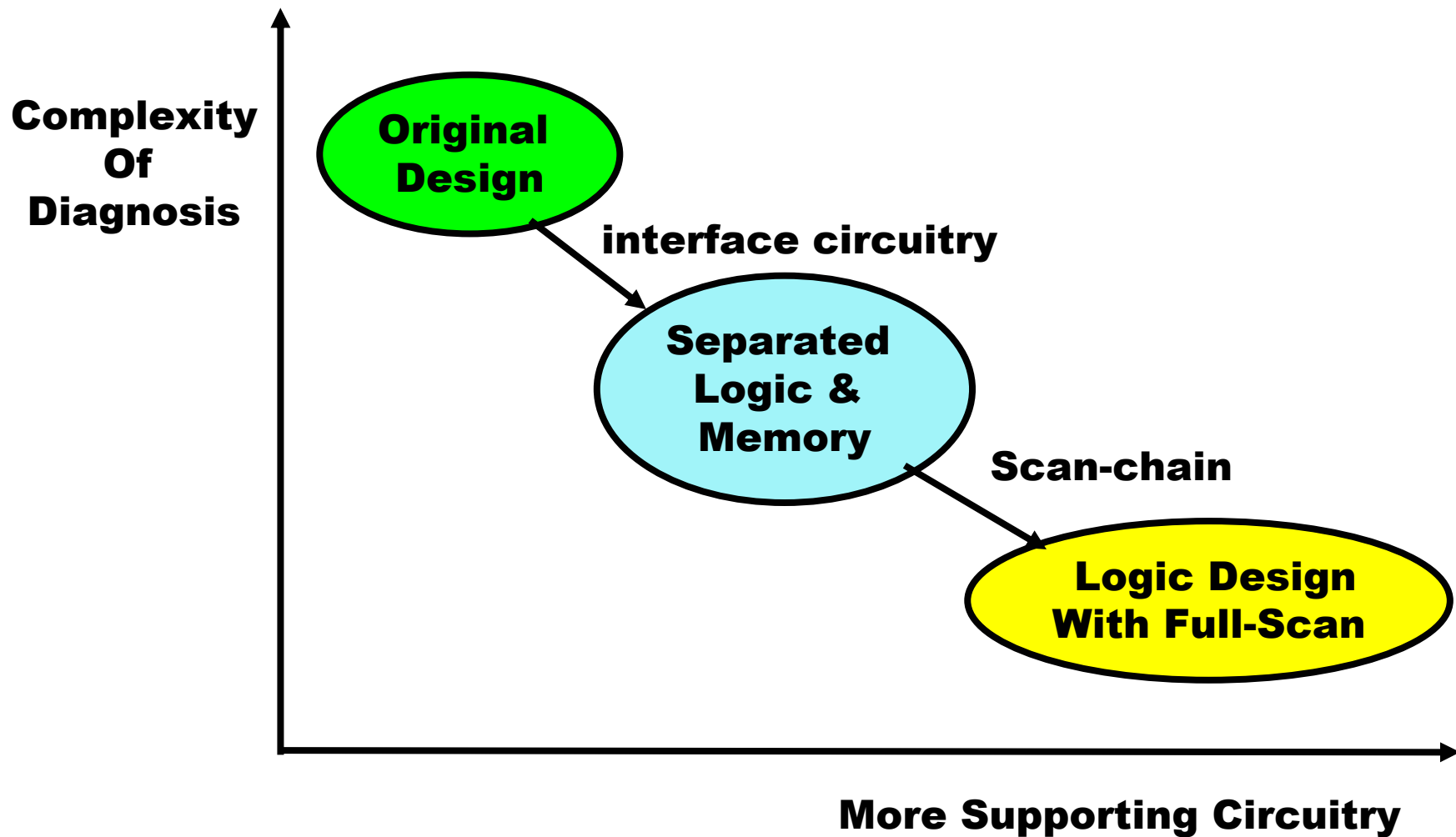


Possible Assumptions Used in Diagnosis

- ❑ **Stuck-At Fault Model Assumption**
 - The defect behaves like a stuck-at fault
- ❑ **Single Fault Assumption**
 - Only one fault affecting any faulty output
- ❑ **Logical Fault Assumption**
 - A fault manifests itself as a logical error
- ❑ **Full-Scan Assumption**
 - The chip under diagnosis has to be full-scanned


*Note: A diagnosis approach **less dependent** on the fault assumptions is more capable of dealing with practical situations.*

Examples of Faults

Node Fault

 


Short Fault (Bridging)

 


Most diagnosis algorithms performs at the gate level, trying to identify the troubling signals or cells

Byzantine Open Fault

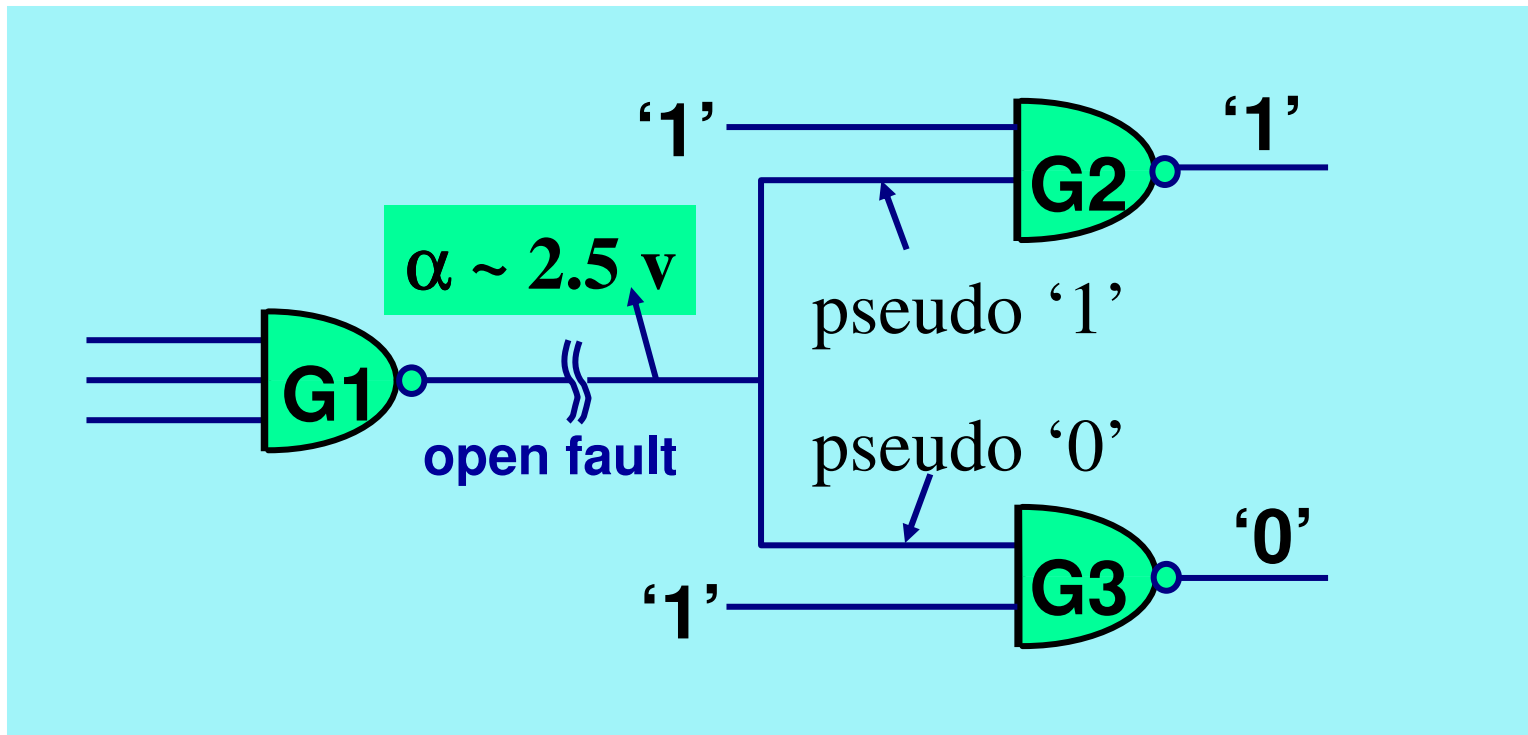- Definition of Byzantine Fault:
 - A fault that causes an ambiguous voltage level



A Byzantine Node Type

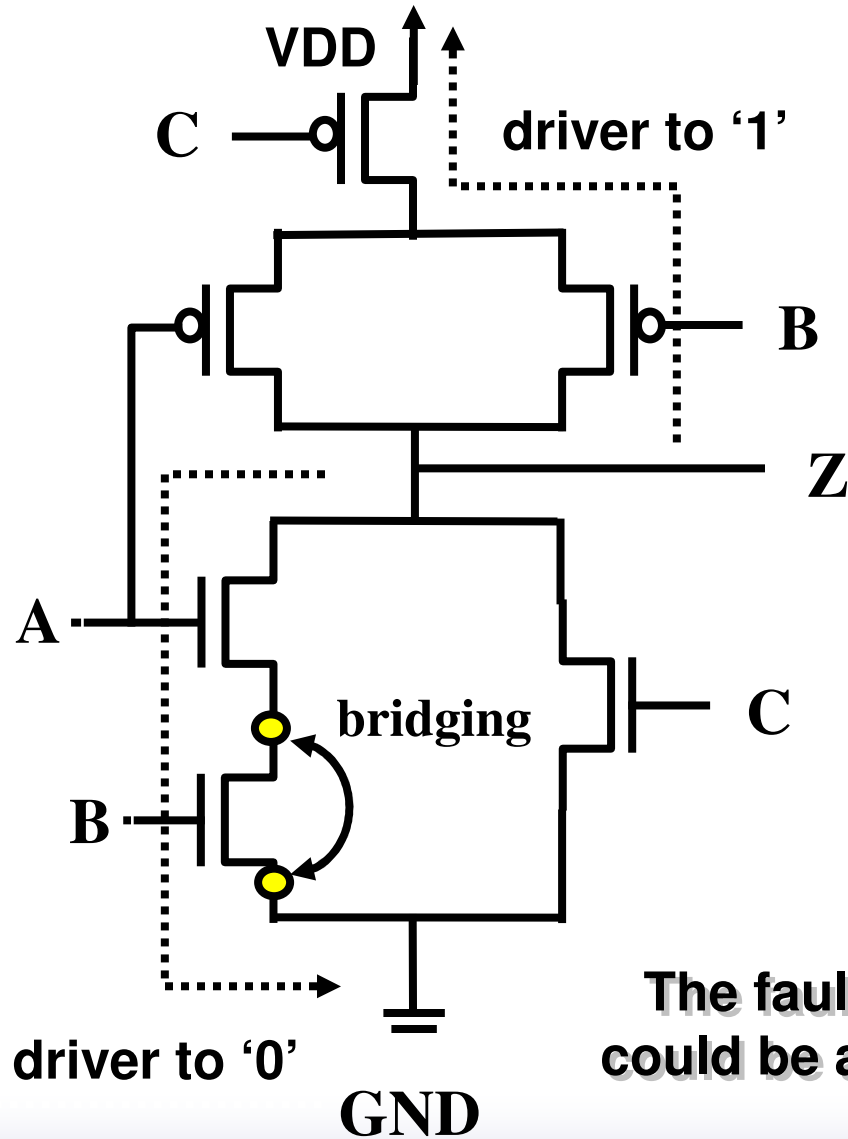


The faulty output could be ambiguous

Truth Table

A	B	C	Z	Z ^f
0	0	0	1	1
0	0	1	0	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	~0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

faulty min-term →

Fault Classification

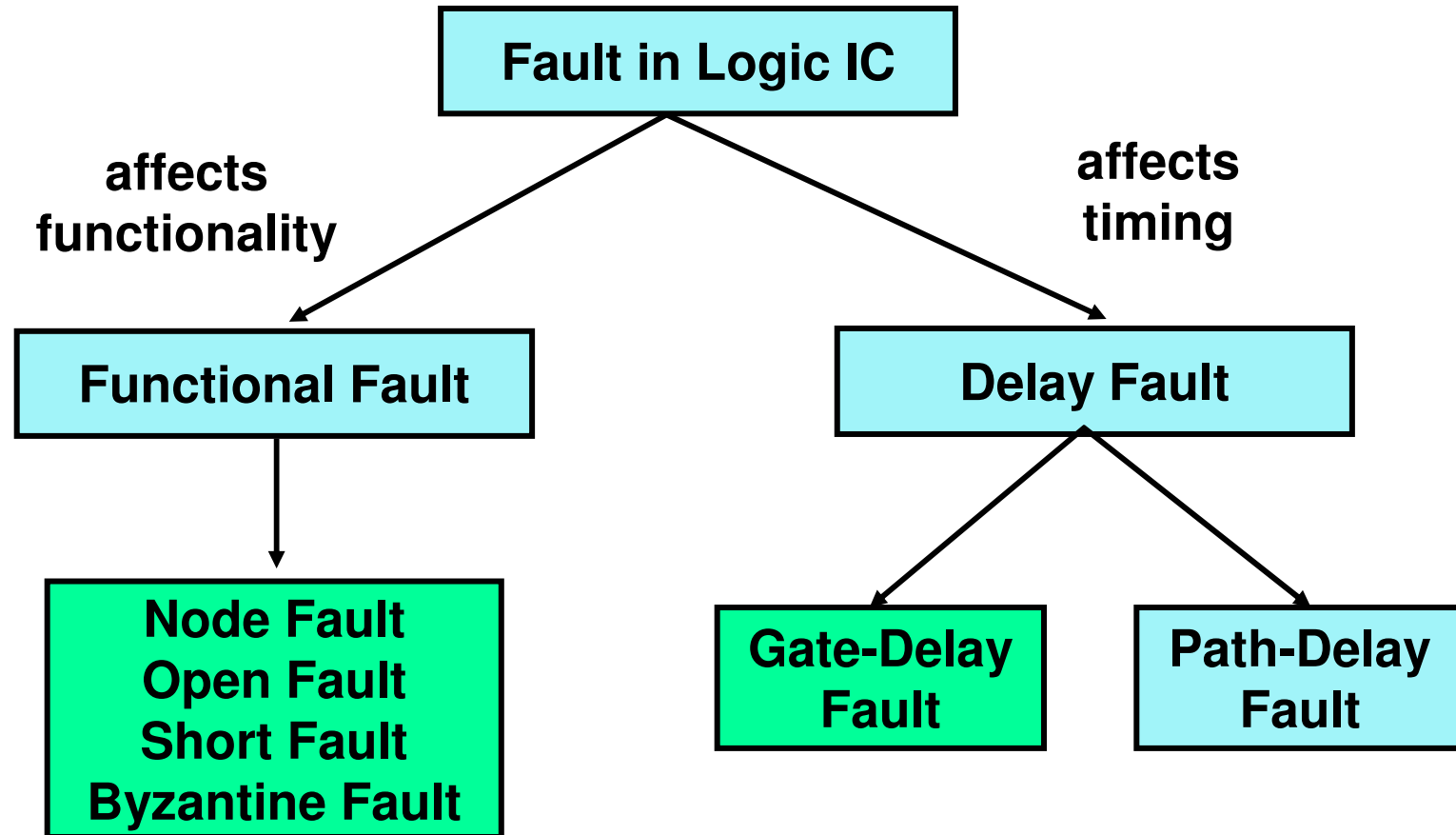


Outline

- Introduction
- □ **Combinational Logic Diagnosis**
 - **Cause-Effect Analysis**
 - **Effect-Cause Analysis**
 - **Chip-Level Strategy**
 - **Diagnostic Test Pattern Generation**
- Scan Chain Diagnosis
- Logic BIST Diagnosis
- Conclusion

Terminology

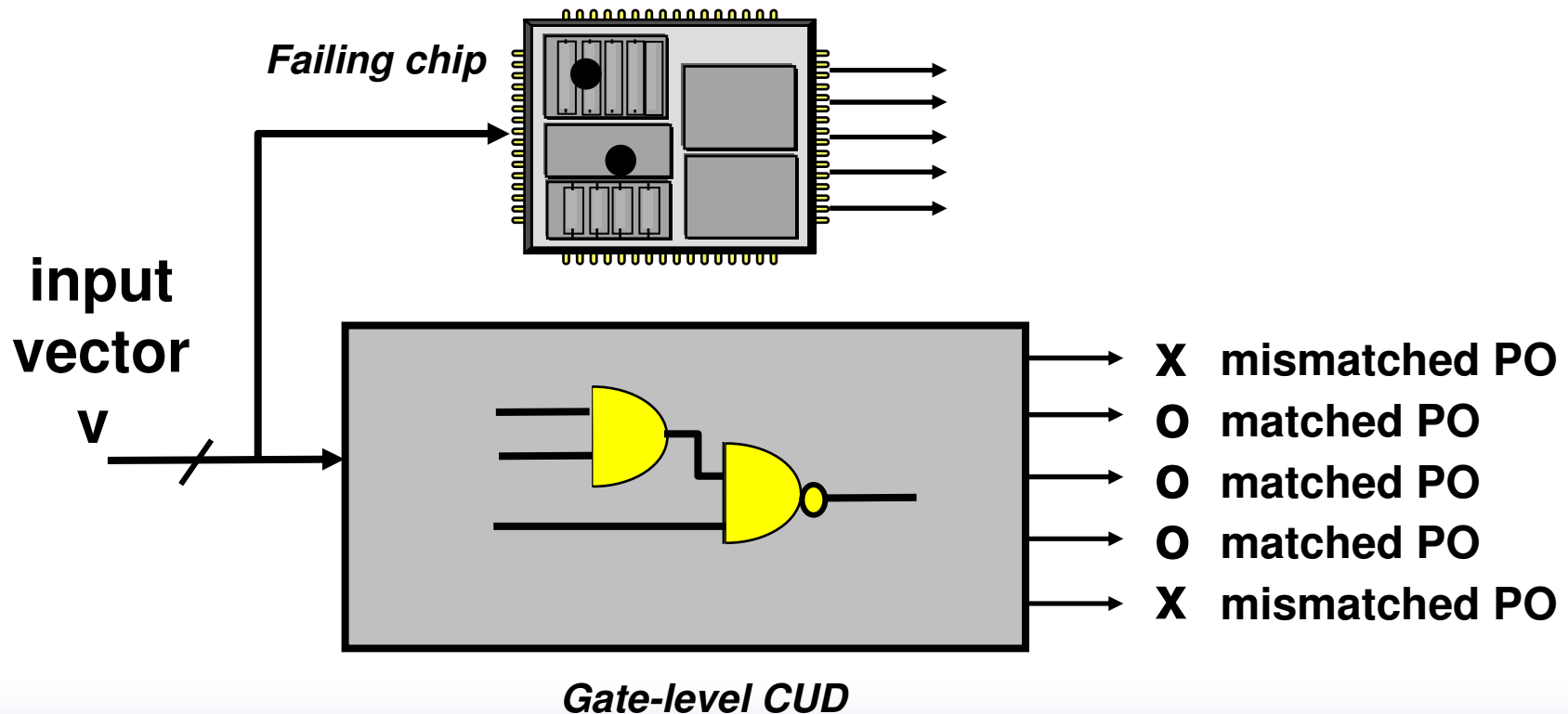- ❑ **Device Under Diagnosis (DUD): The Failing Chip**
- ❑ **Circuit Under Diagnosis (CUD): The Circuit Model**
- ❑ **Failing Input Vector: Causes Mismatches**



Cause-Effect Analysis


- **Fault dictionary (pre-analysis of all causes)**
 - **Records test response of every fault under the applied test set**
 - **Built by intensive fault simulation process**
- **A chip is diagnosed (effect matching)**
 - **By matching up the failing syndromes observed at the tester with the pre-stored fault dictionary**

Fault Dictionary Example



 (a) Circuit under diagnosis

A diagnosis session:
 traverse from a path from root to a leaf



(c) Diagnostic tree

Circuits	Test vectors in terms of (a, b, c)				
	v_1	v_2	v_3	v_4	v_5
fault-free	0	0	0	0	1
f_1	0	1	1	1	1
f_2	1	1	1	0	1
f_3	1	0	0	1	1
f_4	0	0	1	0	0
f_5	0	1	1	0	1

(b) Full-response dictionary

Fault Dictionary Reduction – P&R

(a) Full-response table

Fault	Output Response (z_1, z_2)			
	t_1	t_2	t_3	t_4
f_1	10	10	11	10
f_2	00	00	11	00
f_3	00	00	00	00
f_4	01	00	00	01
f_5	01	00	01	01
f_6	01	00	01	01
f_7	10	00	10	00
f_8	11	11	11	11

Fault	Pass (0) or Fail (1)			
	t_1	t_2	t_3	t_4
f_1	1	1	0	1
f_2	1	0	0	1
f_3	1	0	1	1
f_4	1	0	1	0
f_5	1	0	1	0
f_6	1	0	1	0
f_7	1	0	1	1
f_8	0	1	0	1

(c) P&R compression dictionary

Fault ID	Pass-fail + Extra outputs			
	t_1	t_2	t_3	t_4
f_1	1 1	1	0 1	1
f_2	1 0	0	0 1	1
f_3	1 0	0	1 0	1
f_4	1 0	0	1 0	0
f_5	1 0	0	1 1	0
f_6	1 0	0	1 1	0
f_7	1 1	0	1 0	1
f_8	0 1	1	0 1	1

Response of z_1

Response of z_2

Detection Fault Dictionary

(a) Full-response table

Fault ID	Output Response (z_1, z_2)			
	t_1	t_2	t_3	t_4
f_1	10	10	11	10
f_2	00	00	11	00
f_3	00	00	00	00
f_4	01	00	00	01
f_5	01	00	01	01
f_6	01	00	01	01
f_7	10	00	10	00
f_8	11	11	11	11

failing output vectors

(c) Detection dictionary

Fault ID	Detection information (Test ID : Output Vector)
f_1	$t_1:10$ $t_2:10$ $t_4:10;$
f_2	$t_1:00$ $t_4:00;$
f_3	$t_1:00$ $t_3:00$ $t_4:00;$
f_4	$t_1:01$ $t_3:00;$
f_5	$t_1:01$ $t_3:01;$
f_6	$t_1:01$ $t_3:01;$
f_7	$t_1:10$ $t_3:10$ $t_4:00;$
f_8	$t_2:10$ $t_4:11;$

(b) Pass-fail dictionary


Fault ID	Pass (1) or Fail (0)			
	t_1	t_2	t_3	t_4
f_1	1	1	0	1
f_2	1	0	0	1
f_3	1	0	1	1
f_4	1	0	1	0
f_5	1	0	1	0
f_6	1	0	1	0
f_7	1	0	1	1
f_8	0	1	0	1

Outline


- ❑ Introduction
- ❑ Combinational Logic Diagnosis
 - Cause-Effect Analysis
 - ➔ ▪ **Effect-Cause Analysis**
 - Chip-Level Strategy
 - Diagnostic Test Pattern Generation
- ❑ Scan Chain Diagnosis
- ❑ Logic BIST Diagnosis
- ❑ Conclusion

Terminology: Mismatched Output

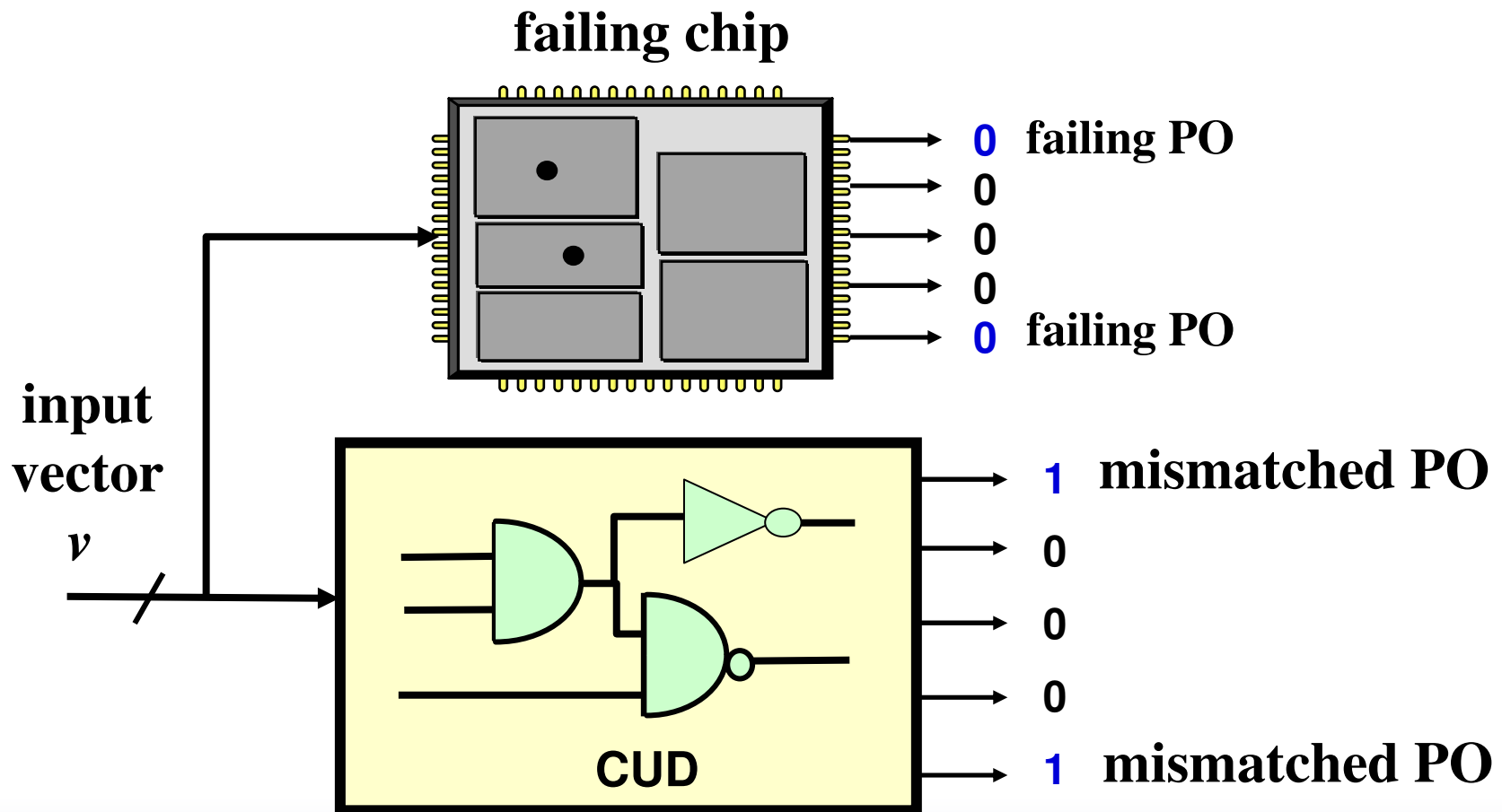
*Effect-cause analysis does not build fault dictionary
It predicts fault locations by analyzing CUD from mismatch PO's*



 Structural Pruning – Intersection or Union?



(a) Cone intersection.

 


(b) Cone union when there are multiple faults.

Backtrace Algorithm

- ❑ **Trace back from each mismatched PO**
 - To find out suspicious faulty locations
- ❑ **Functional Pruning**
 - During the traceback, some signals can be disqualified from the fault candidate set based on their signal values.
- ❑ **Rules**
 - (1) At a controlling case (i.e., 0 for a NAND gate): Its fanin signals with non-controlling values (i.e., 1) are excluded from the candidate set.
 - (2) At a non-controlling case (i.e., 1 for a NAND gate): Every fanin signal remains in the candidate set.


Backtrace Example

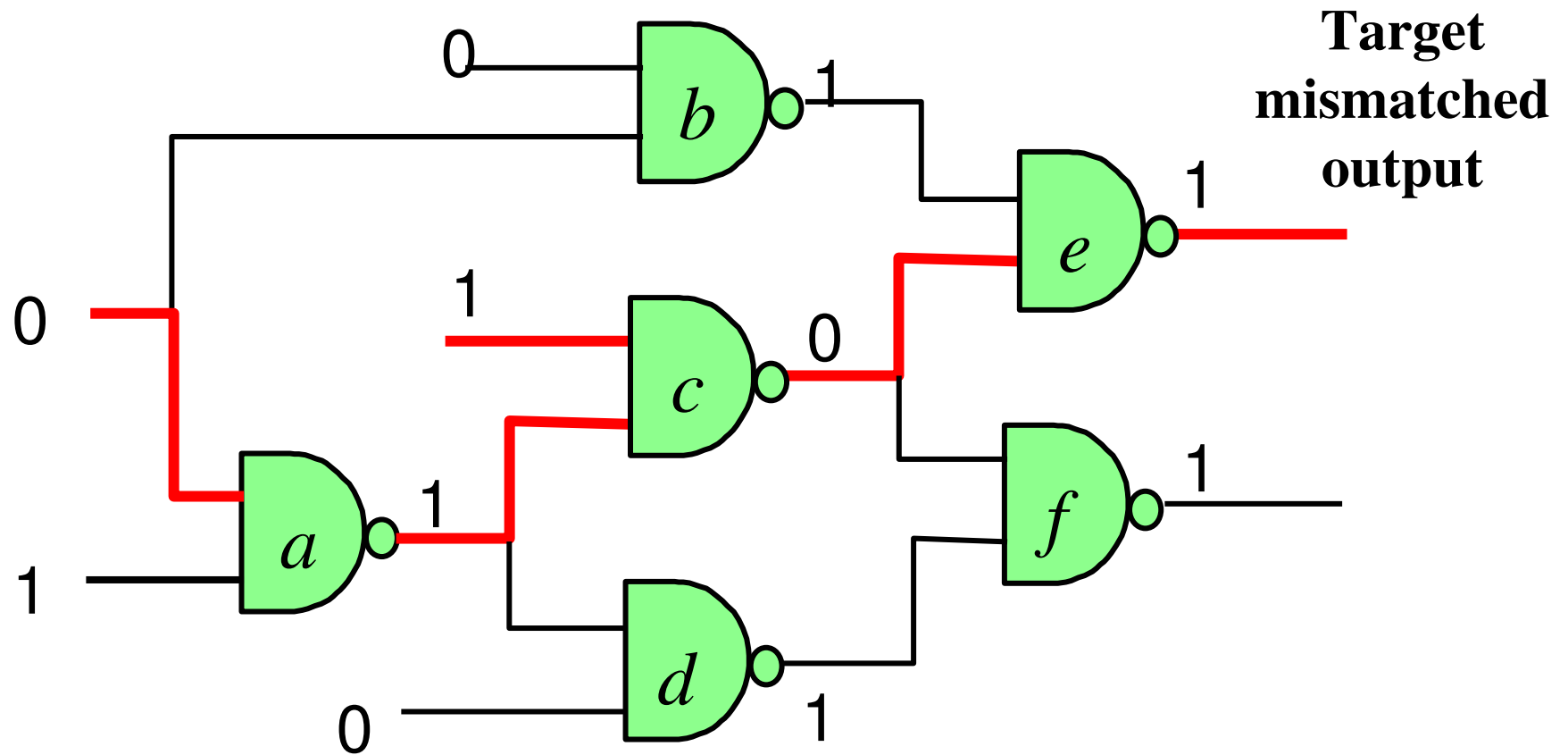All suspicious fault locations are marked in red.




Terminology – Injection

 An injection at a signal f flips its current value which could create value-change events downstream.



O: correct output
X: failing output

 


A mismatched output could be fixed by the injection!


Terminology – Curable Output

□ Diagnosis Criterion

 - A signal is more suspicious if it has more curable outputs



O : correct output
 X : failing output

 


An injection at f fixes two mismatched outputs
→ Thus, f has two curable outputs !

Terminology – Curable Vectors


v is a curable vector by f

→ because an injection at f exists such that it cures all mismatches without creating new one

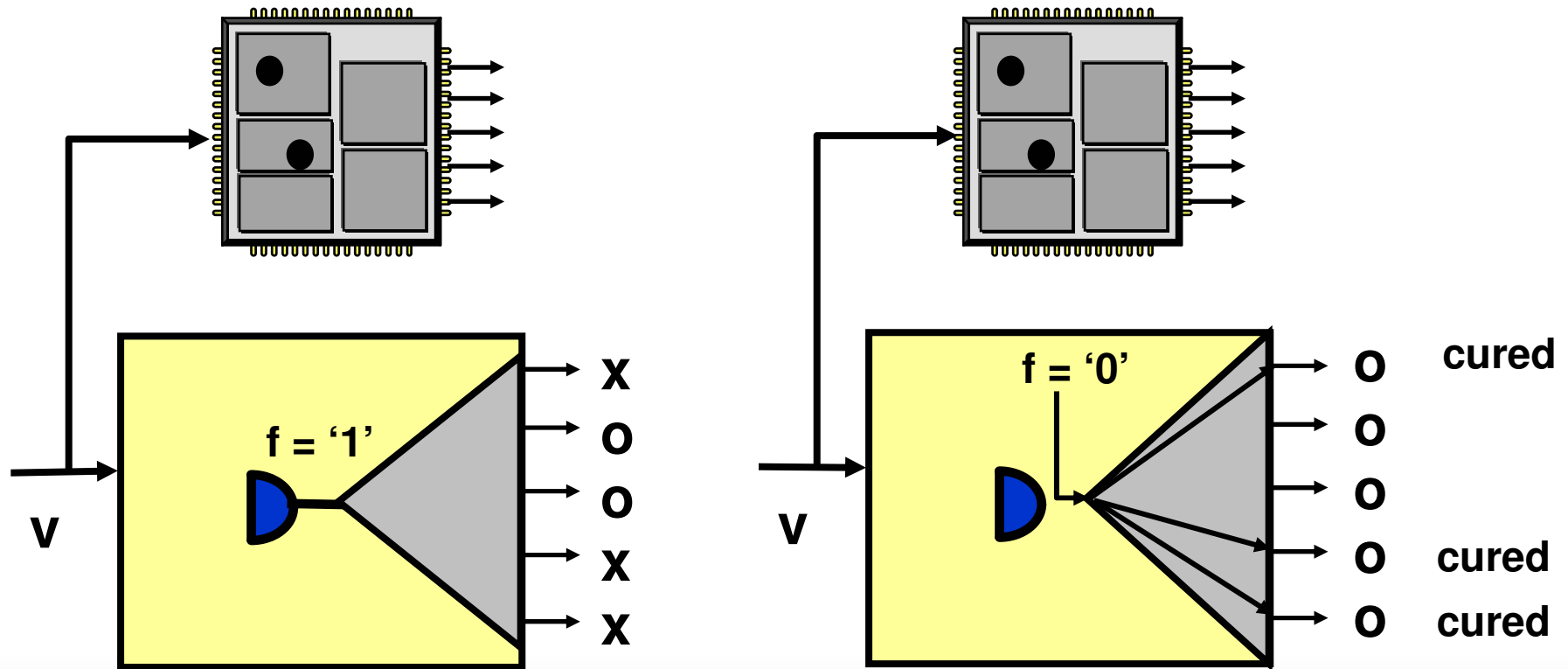
Curable vector is a stronger diagnosis indicator than curable output !



Example of Curable Vector

 

(a) Failing Chip

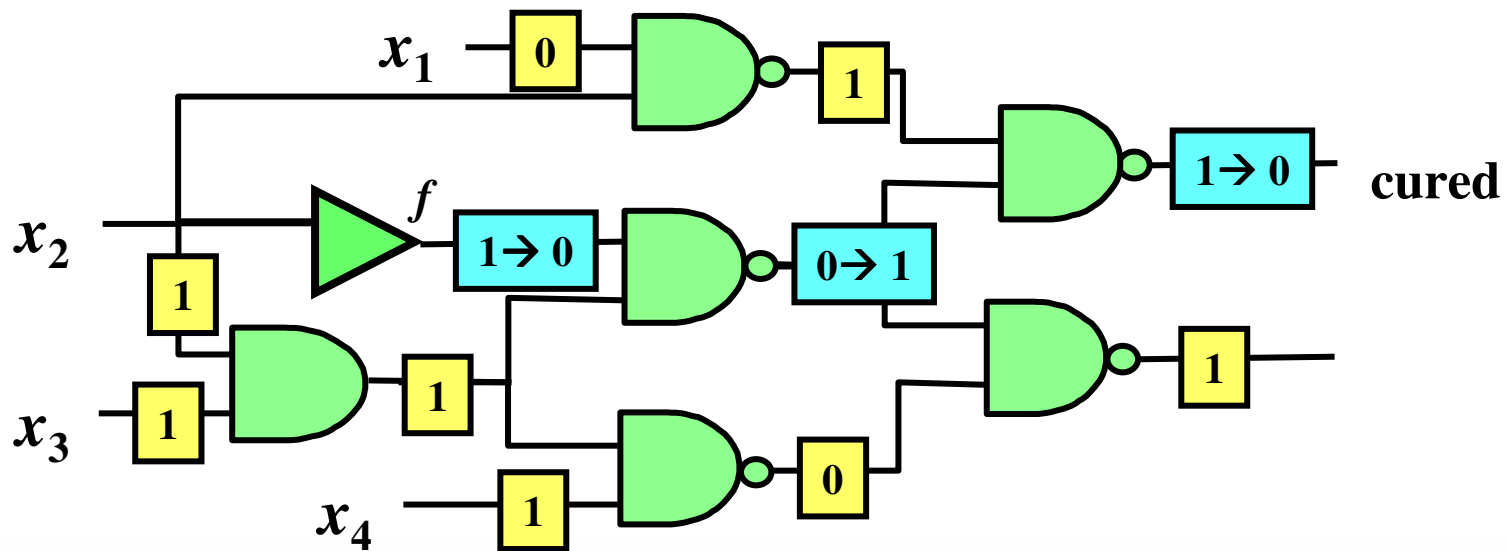

(b) Circuit Under Diagnosis

Why Curable Vector ?

❑ Information theory


- A less probable event contains more information
- Curable output is an easy-to-satisfy criterion, high aliasing
- Curable vector is a hard-to-satisfy criterion, low aliasing

❑ Not all failing input vectors are equal !


❑ Niche input vector

- Is an failing input vector that activates only one fault
- Likely to be a curable vector of certain signals
- Few, but tells more about the real fault locations

Inject-and-Evaluate Paradigm

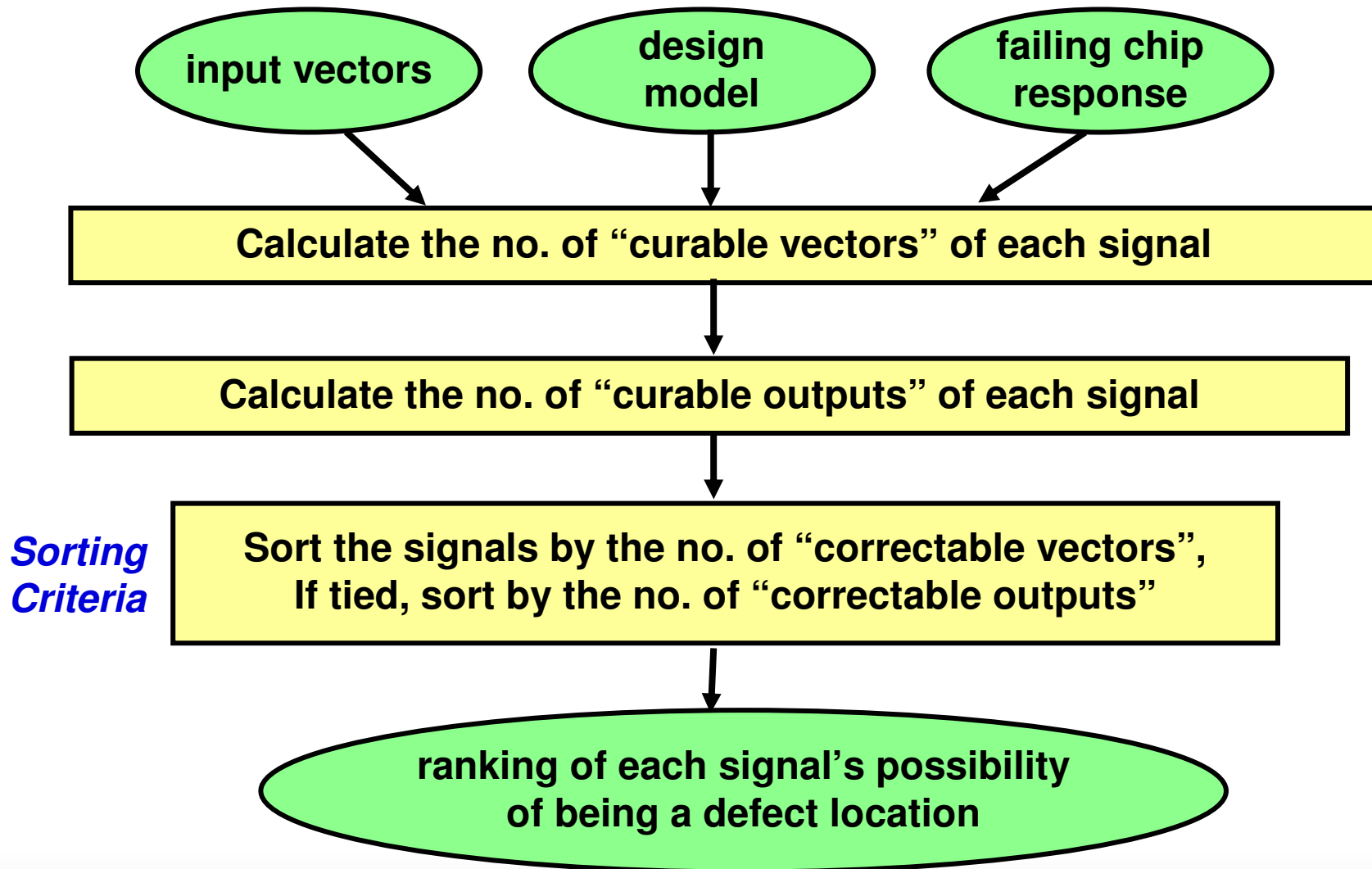

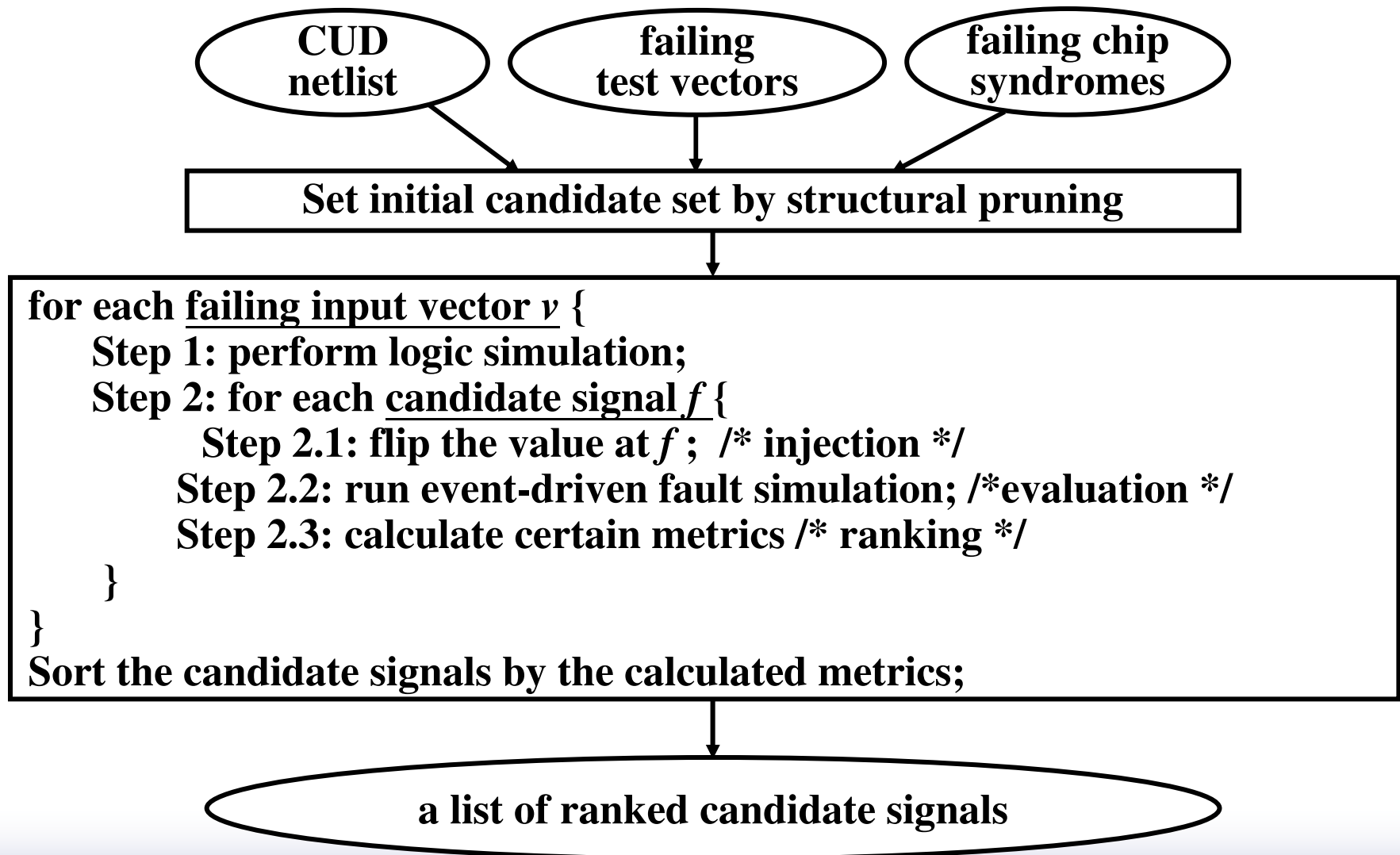
Detailed Computation – Inject-and-Evaluate Paradigm




Reward-and-Penalty Heuristic

Rank1: curable vector count

 Rank2 = (curable output count – 0.5 * new mismatched output count)




(a) Failing Chip.

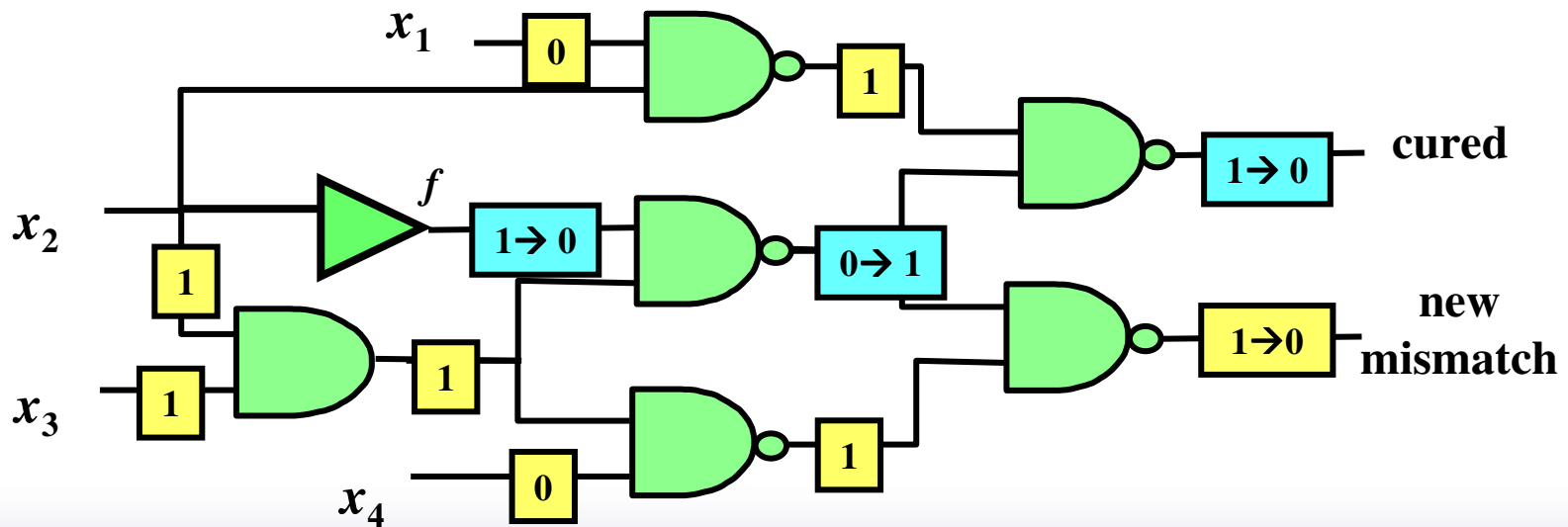

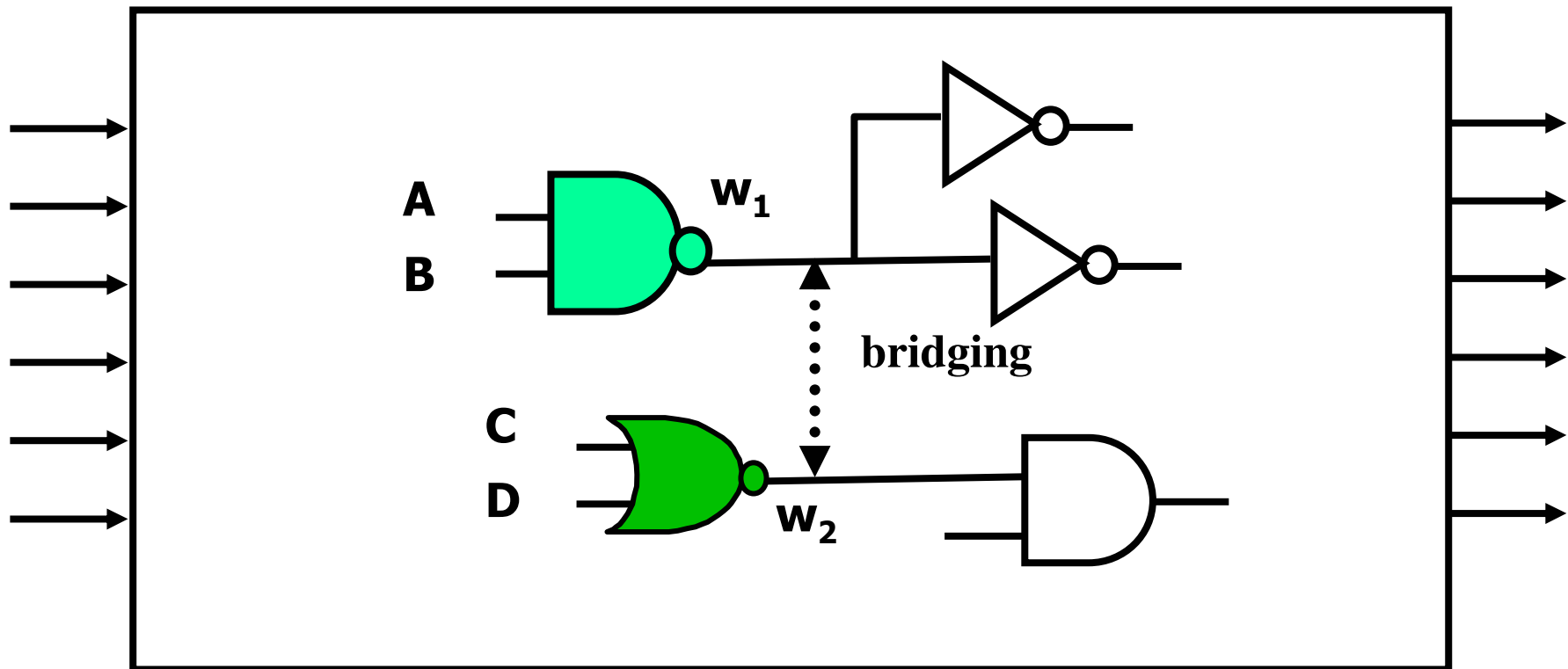(b) Circuit Under Diagnosis.

Targeting Bridging Faults


Even in a realistic bridging fault, there is only one victim at any time. This victim will expose his location by owning some curable vectors.



SLAT Paradigm

Ref: *SLAT* (Single Location At a Time) paradigm [Bartenstein 2001]

Note: A SLAT vector is a curable vector

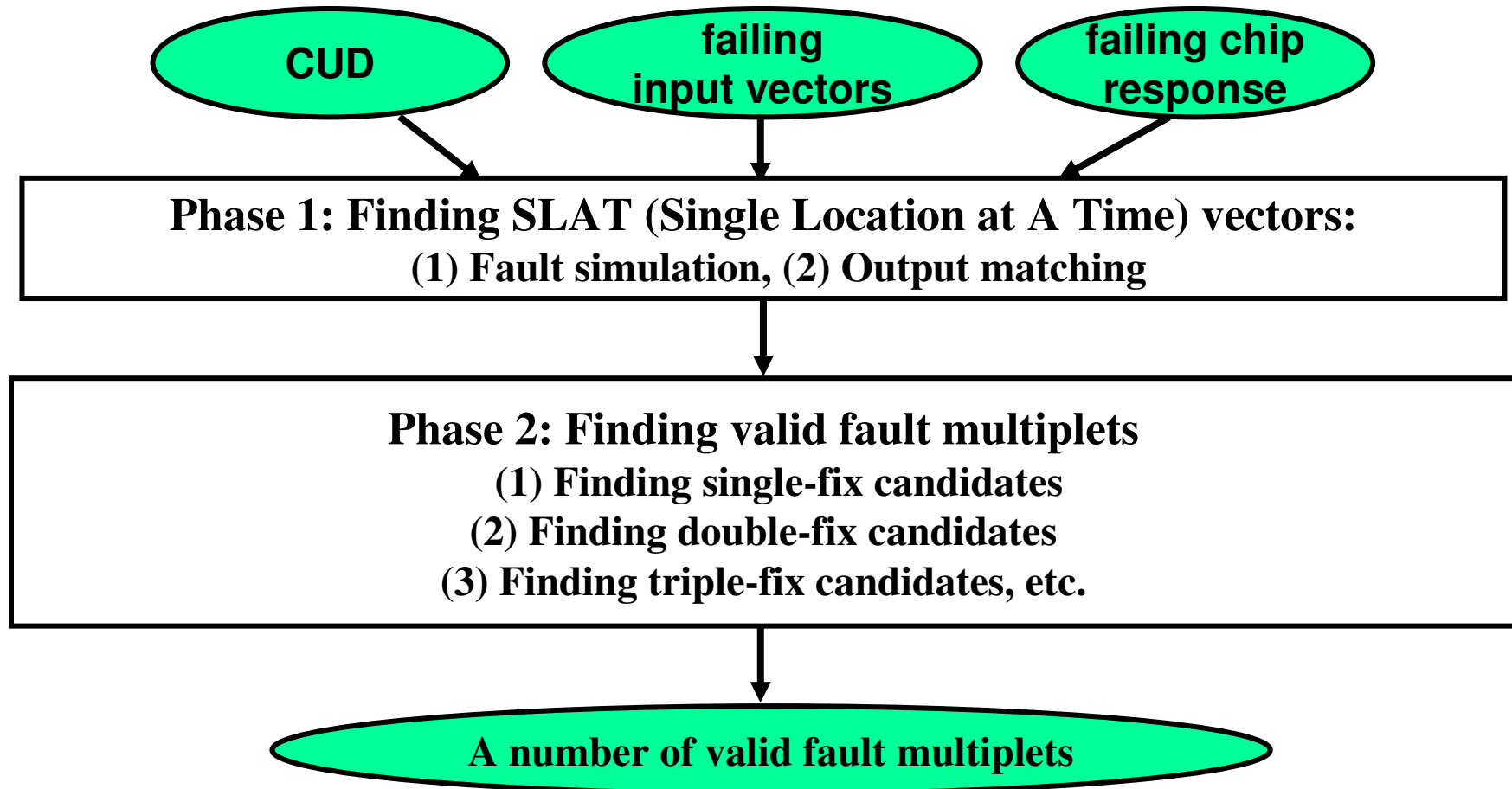


Example: SLAT Paradigm

Failing Input Vectors	Signals in the CUD						
	f_1	f_2	f_3	f_4	f_5	f_6	f_7
V_1	*				*		
V_2	*	*	*				
V_3			*	*			*
V_4					*	*	
V_5		*			*		
V_6		*			*		
V_7	*		*				
V_8			*				*
V_9			*		*		
V_{10}					*		*


A mark * means the corresponding vector is a SLAT vector of the corresponding signal.

$(f_3 \text{ and } f_5)$ is a valid fault multiplet

Outline

- ❑ Introduction
- ❑ Combinational Logic Diagnosis
 - Cause-Effect Analysis
 - Effect-Cause Analysis
 - ▪ **Chip-Level Strategy**
 - **Diagnostic Test Pattern Generation**
- ❑ Scan Chain Diagnosis
- ❑ Logic BIST Diagnosis
- ❑ Conclusion

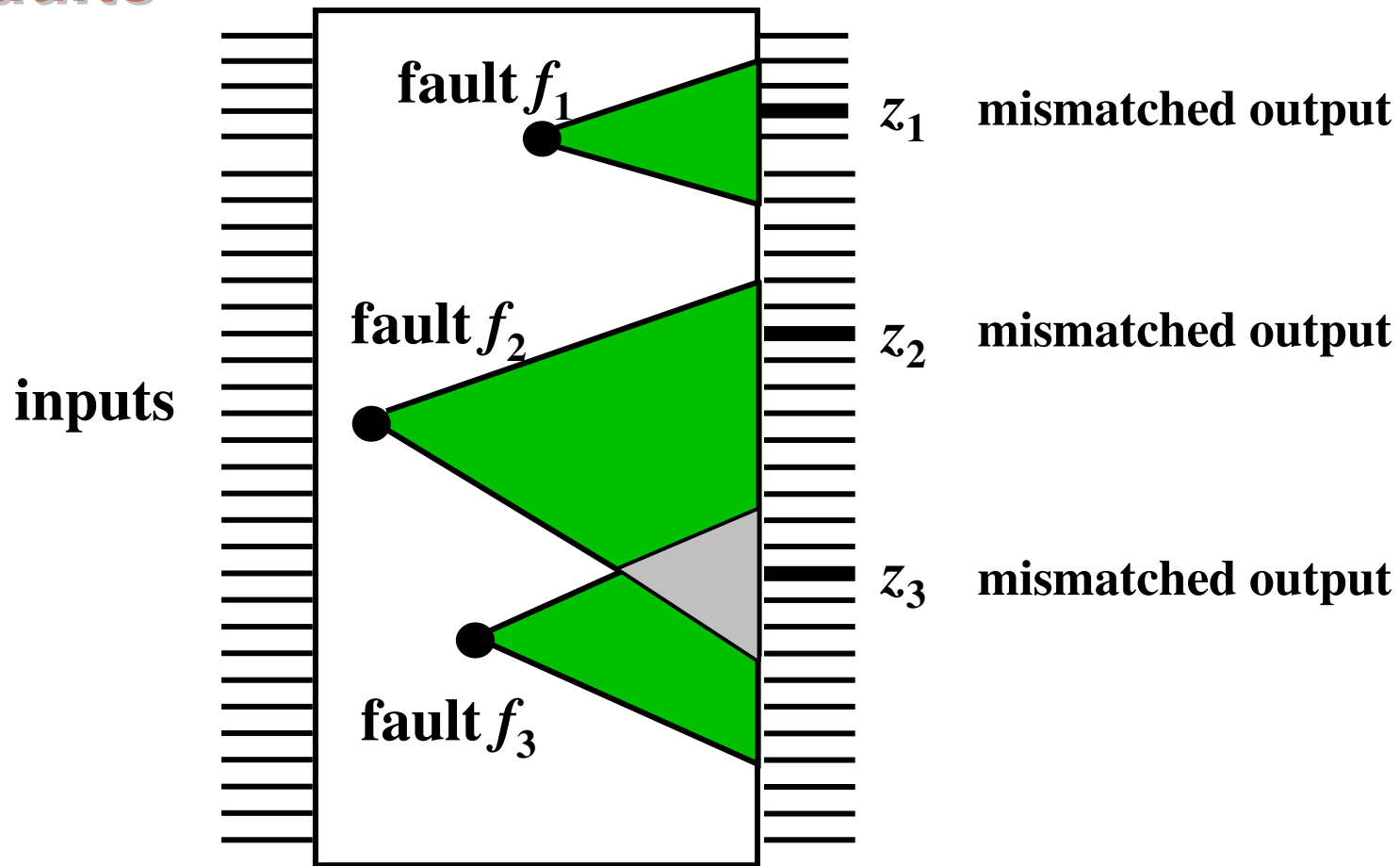
Structurally Dependent and Independent Faults




Fault f_1 is an independent fault.

Faults f_2 and f_3 are dependent faults.


Dependency Graph

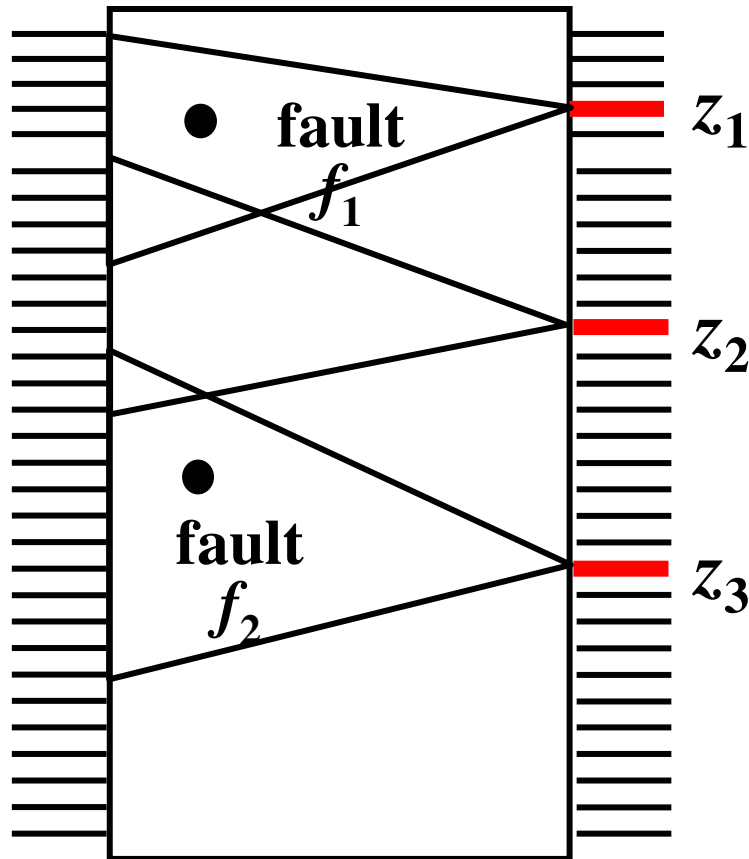

 *Direct divide-and-Conquer
does not work well !*



dependency graph

 

one connected component

Two independent faults, f_1 and f_2 , lead to one diagnosis block.


Main Strategy: Detach-Divide-and-then-Conquer

- **Phase 1: Isolate Independent Faults**
 - Search for prime candidates
 - Use word-level information
- **Phase 2: Locate Dependent Faults As Well**
 - Perform partitioning
 - Aim at finding one fault in each block

Prime Candidates

A signal f is a prime candidate if

 - (1) All failing input vectors are partially curable by f
- (2) Curable-Output-Set(f) is not covered by any other's




Fake Prime Candidates

- **Structurally Independent Faults**
 - are often prime candidates
- **Fake Prime Candidates**
 - are prime candidates that are **NOT** really faults - aliasing

 Example: Dependent Double Faults f1 & f2

May create fake prime candidates {f1, f2, f3}.



Word-Level Registers and Outputs

Signals in a design are often defined in words.

This property can be used to differentiate fake prime candidates from the real ones.


Word-Level Output: O1

Word-Level Registers: R1, R2, State


```
module    design( O1, ...)  
    output[31:0]  O1;  
    reg[31:0]     R1, R2;  
    reg[5:0]      State  
    ...  
endmodule
```

Word-Level Prime Candidates

 Note: Z and R are two word-level output groups.



 Original prime candidates: $\{f_1, f_2\}$
Word-level prime candidates $\{f_1, f_2\}$




Assumed original prime candidates: $\{f_3, f_4, f_5\}$
 $\{f_4, f_5\}$ will be identified as fake
 → *Final Word-level prime candidates $\{f_3\}$*

Efficiency of Using Word-Level Info.

- ❑ **Without word-level Information**
 - **2.4 real faults out of 72.3 candidates**
- ❑ **With word-level Information**
 - **1.23 real faults out of 3.65 candidates**



# of candidates	Original	After Filtering	Filtering Ratio
Prime Candidates	2.375	1.23	48.2 %
Fake Prime Candidates	69.96	2.42	96.5 %

Overall Flow

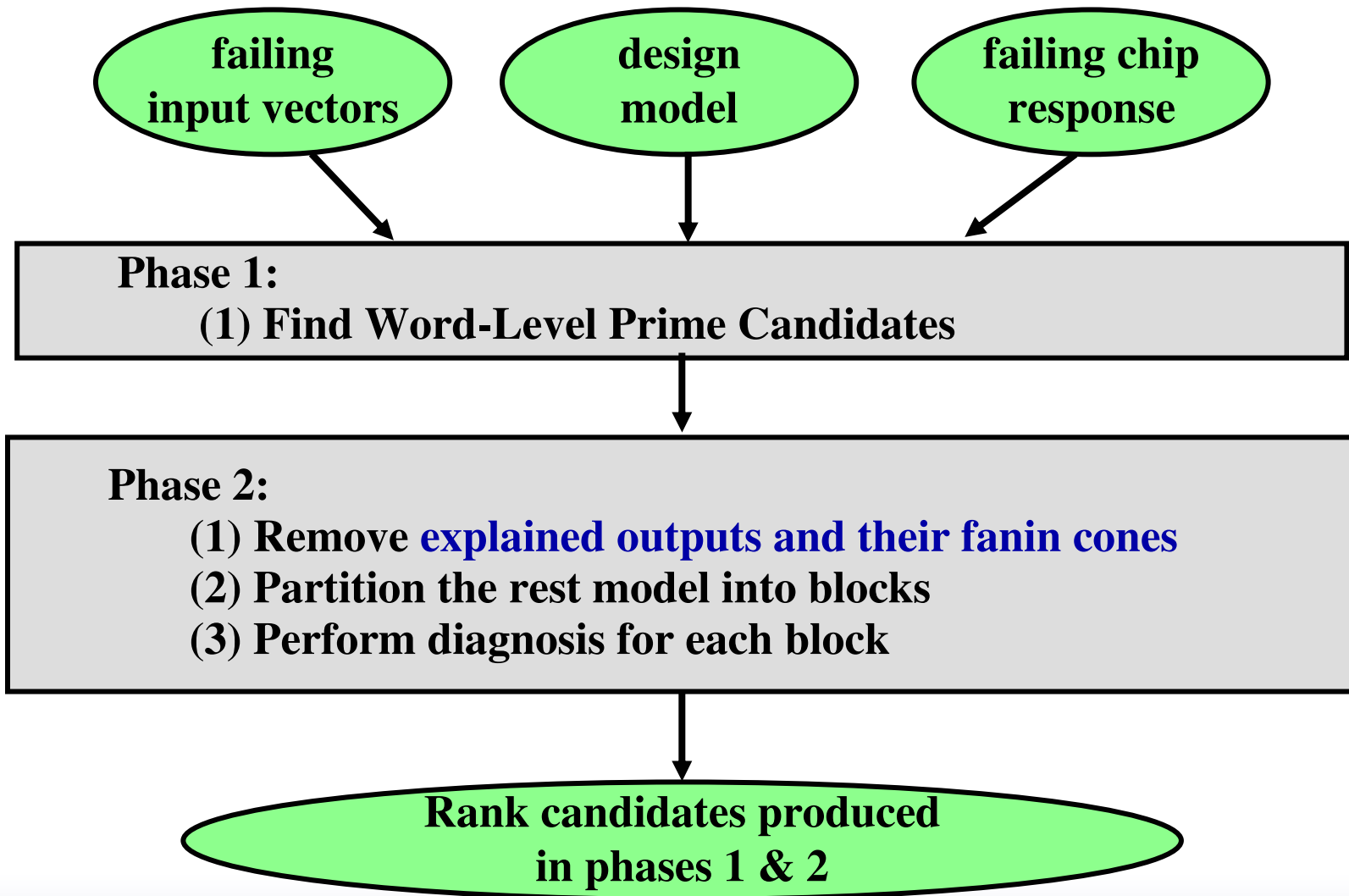


Grouping Using Dependency Graph



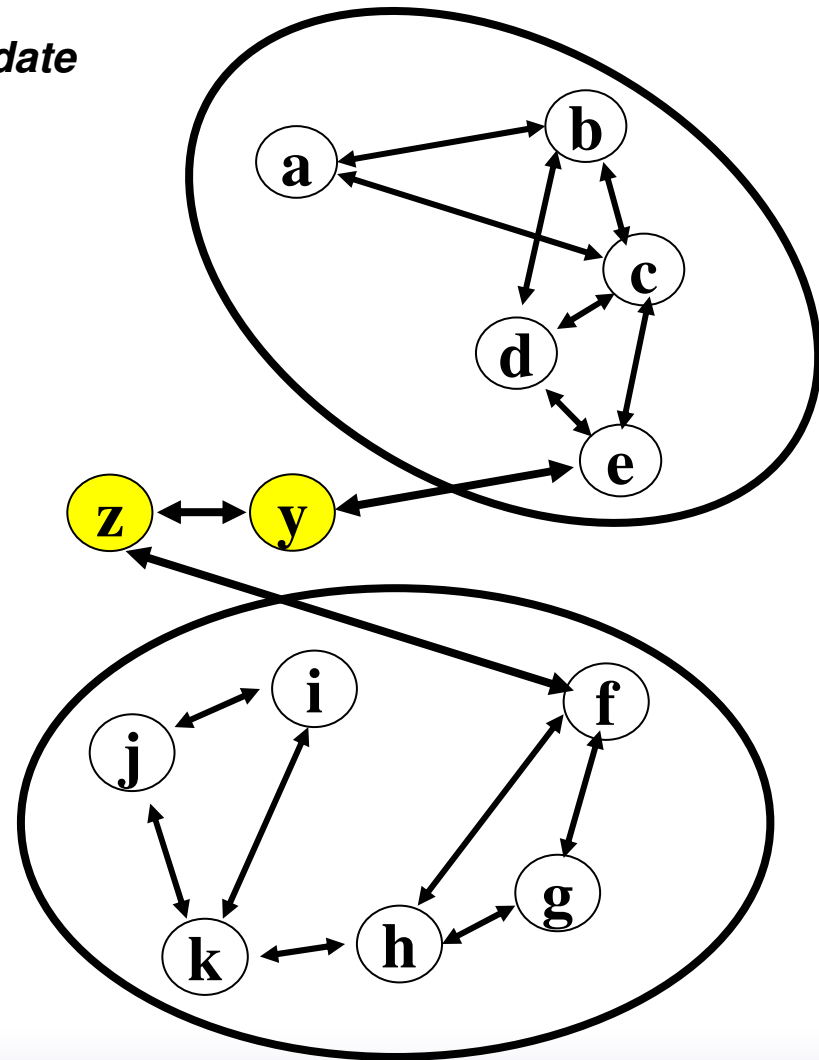
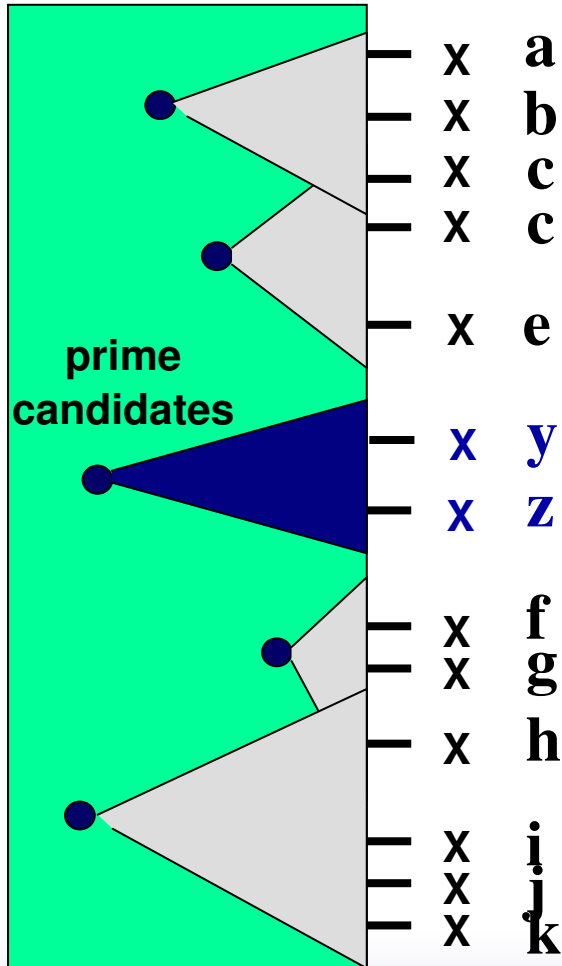
An example with five faults
 One of them is identified as the prime candidate



Removed Explained Faulty Outputs

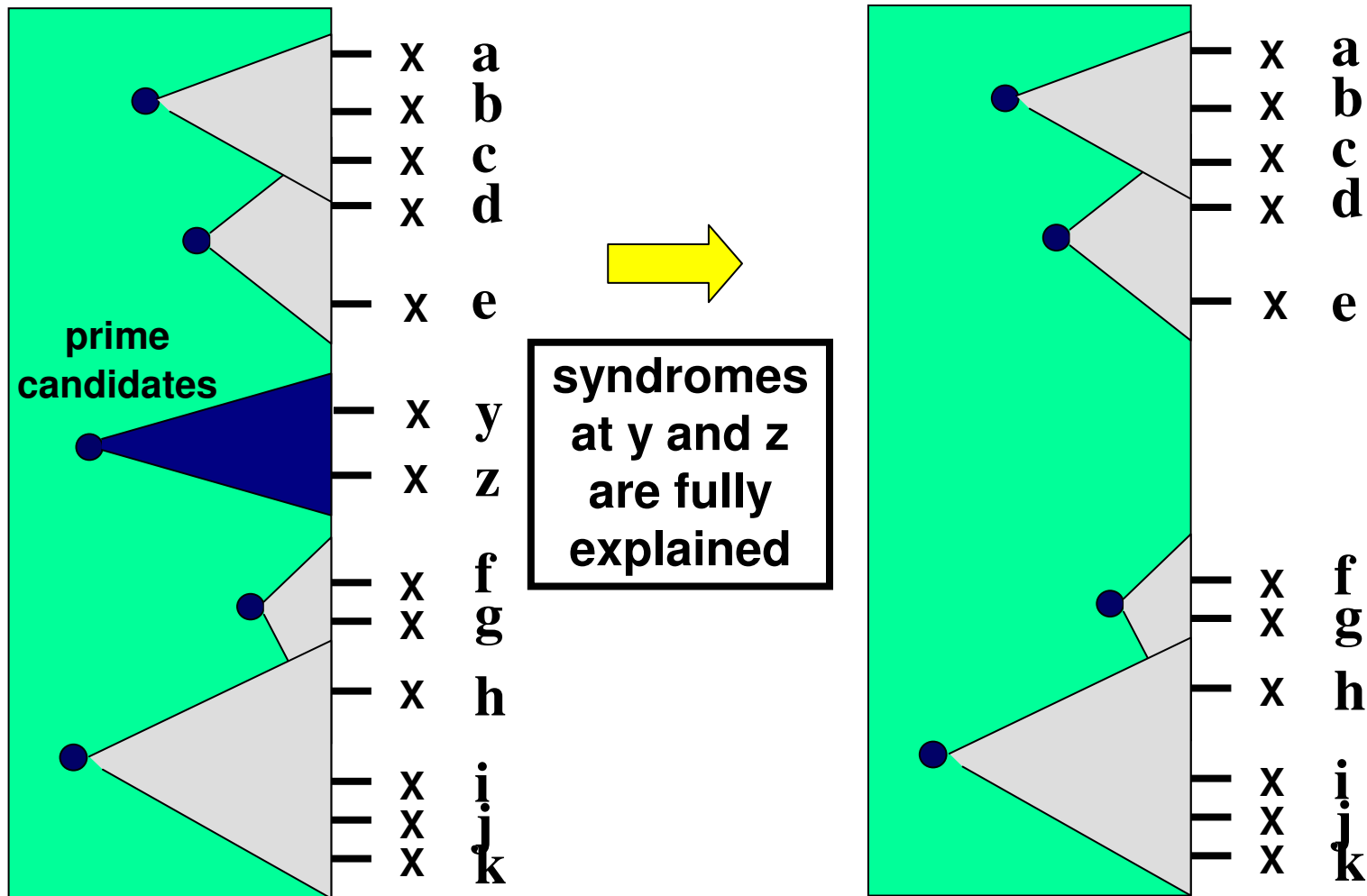

Grouping Example

    


***Two independent diagnosis blocks
Are successfully derived!***

Summary

- ❑ **Strategy**
 - **(1) Search For Word-Level Prime Candidates**
 - **(2) Identify Independent Faults First**
 - **(3) Locate Dependent Faults As Well**
- ❑ **Effectiveness**
 - **identify 2.98 faults in 5 signal inspections**
 - **find 3.8 faults in 10 signal inspections**


Diagnostic Test Pattern Generation

 DTPG helps to increase diagnostic resolution



fault-free circuit

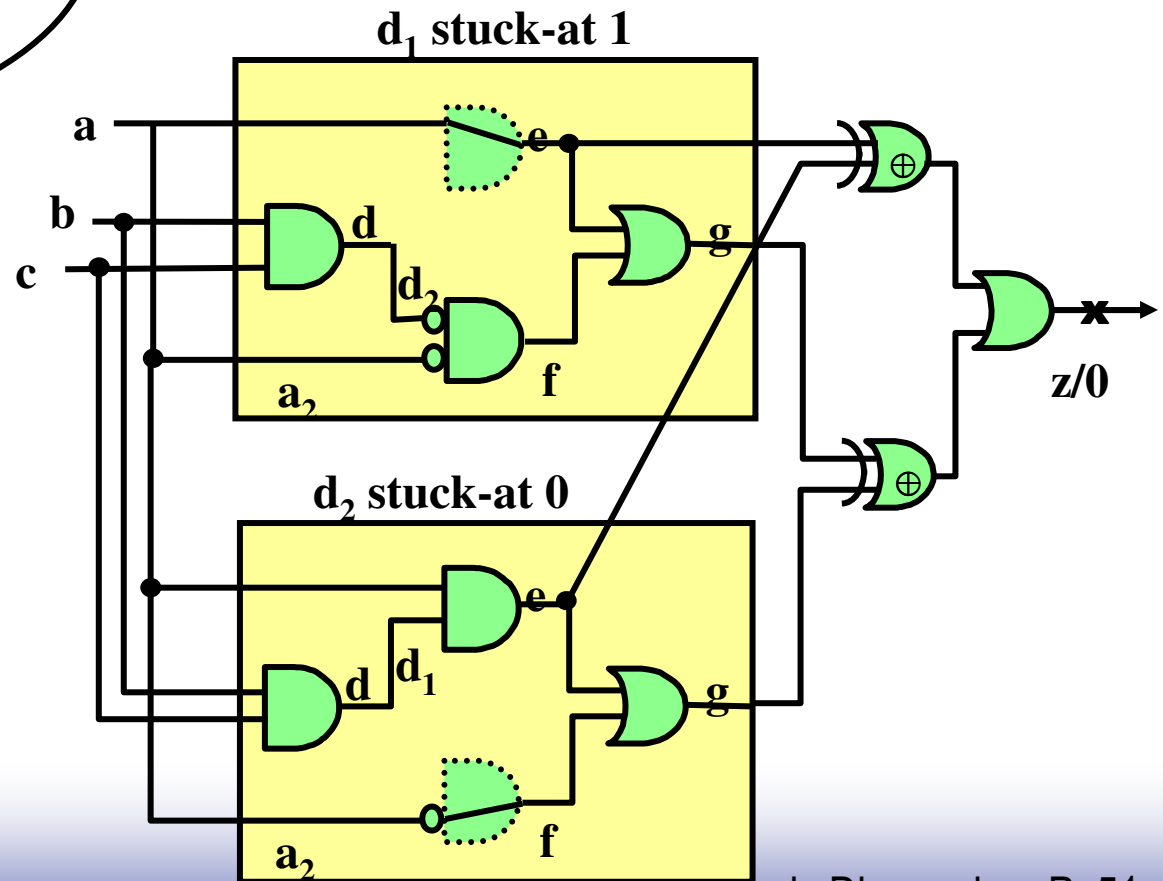
Model for differentiating vector generation




Outline

- Introduction
- Combinational Logic Diagnosis
- □ **Scan Chain Diagnosis**
 - Preliminaries
 - Hardware-Assisted Method
 - Signal-Profiling Based Method
- Logic BIST Diagnosis
- Conclusion

Scan Test and Diagnosis

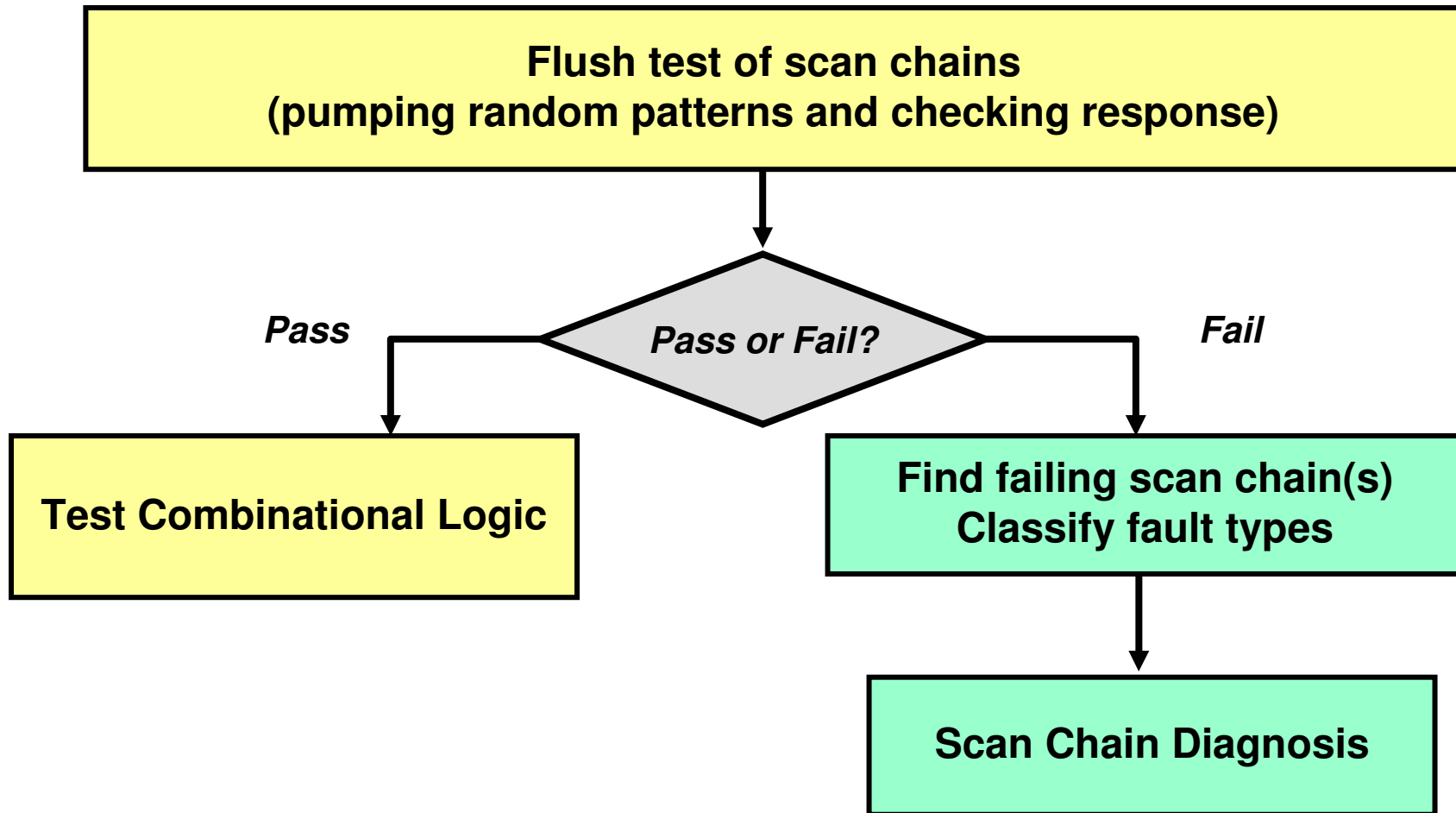


Commonly Used Fault Types in Scan Chains

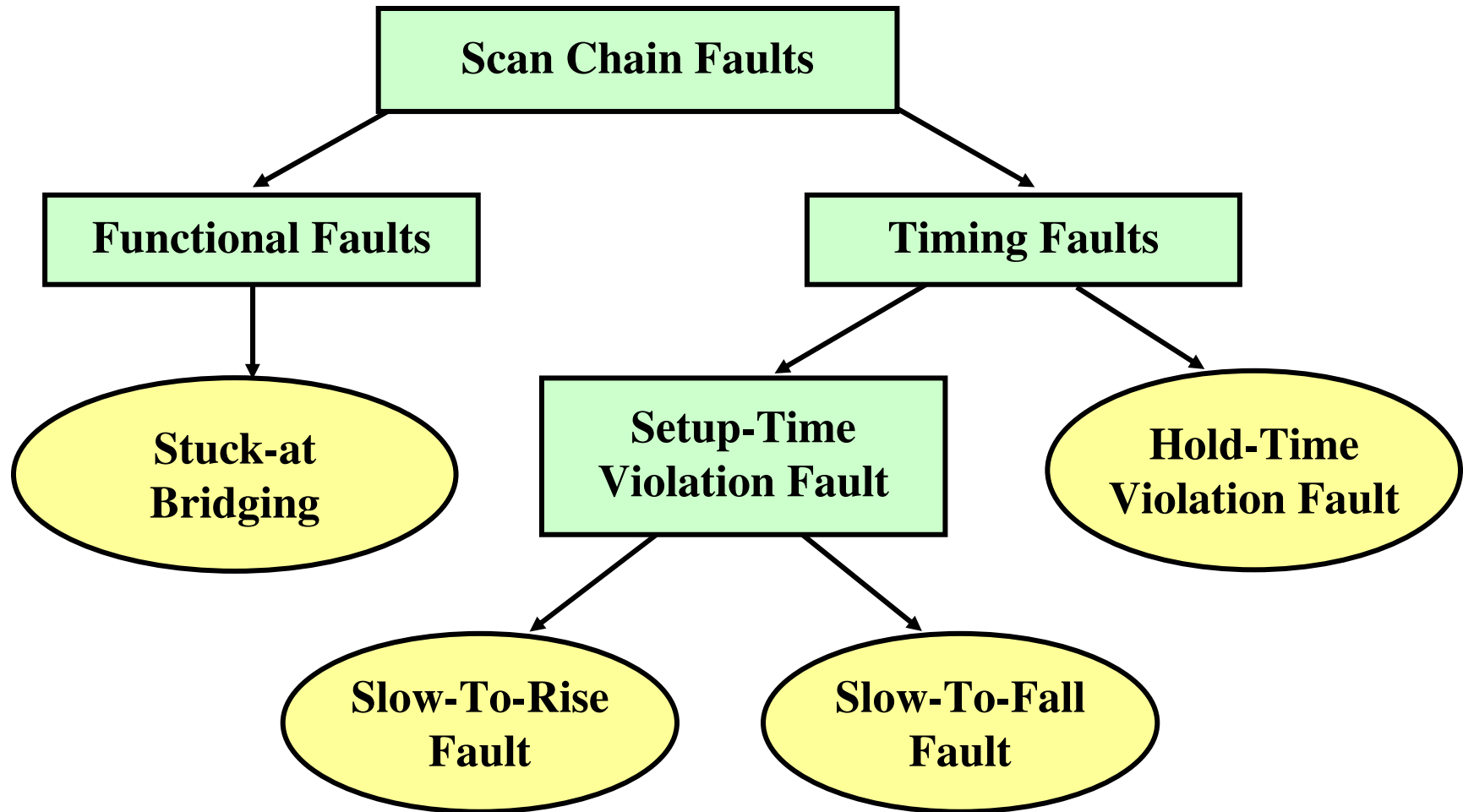


Each fault could be permanent or intermittent.

A Stuck-At Fault In the Chain

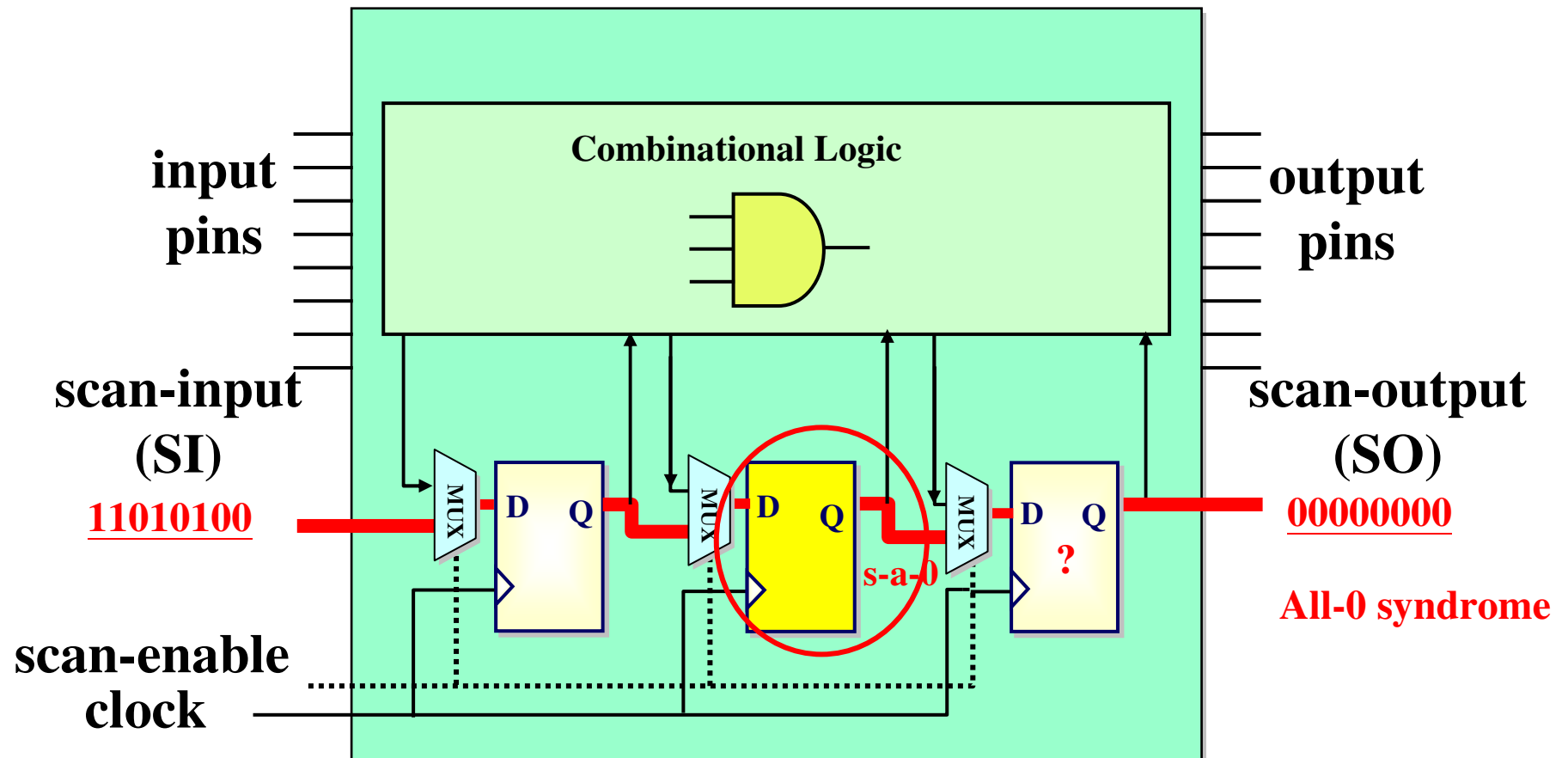
Effect: A **killer** of the scan-test sequence



A Realistic Bridging Fault Model

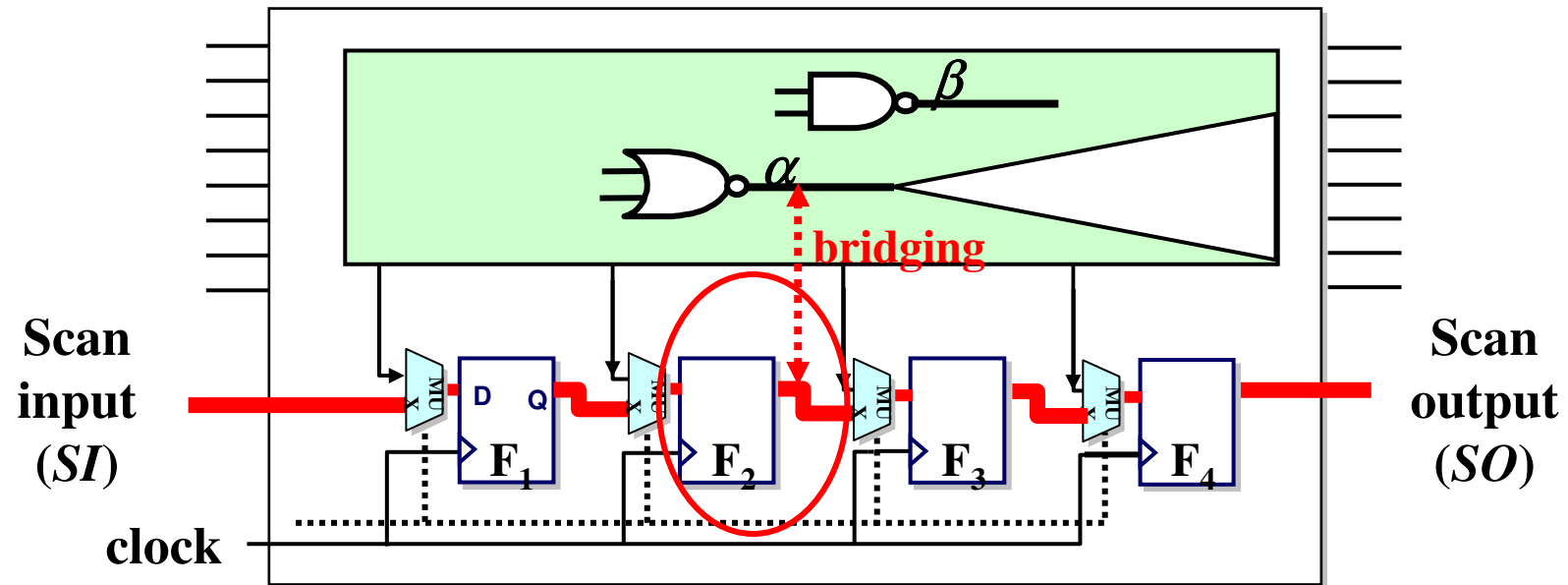

 
(a) Bridging between a flip-flop and a logic cell.




(b) Our bridging fault model.

Potential Hold-Time Fault?

(Negative Edge-Triggered Flip-Flop)

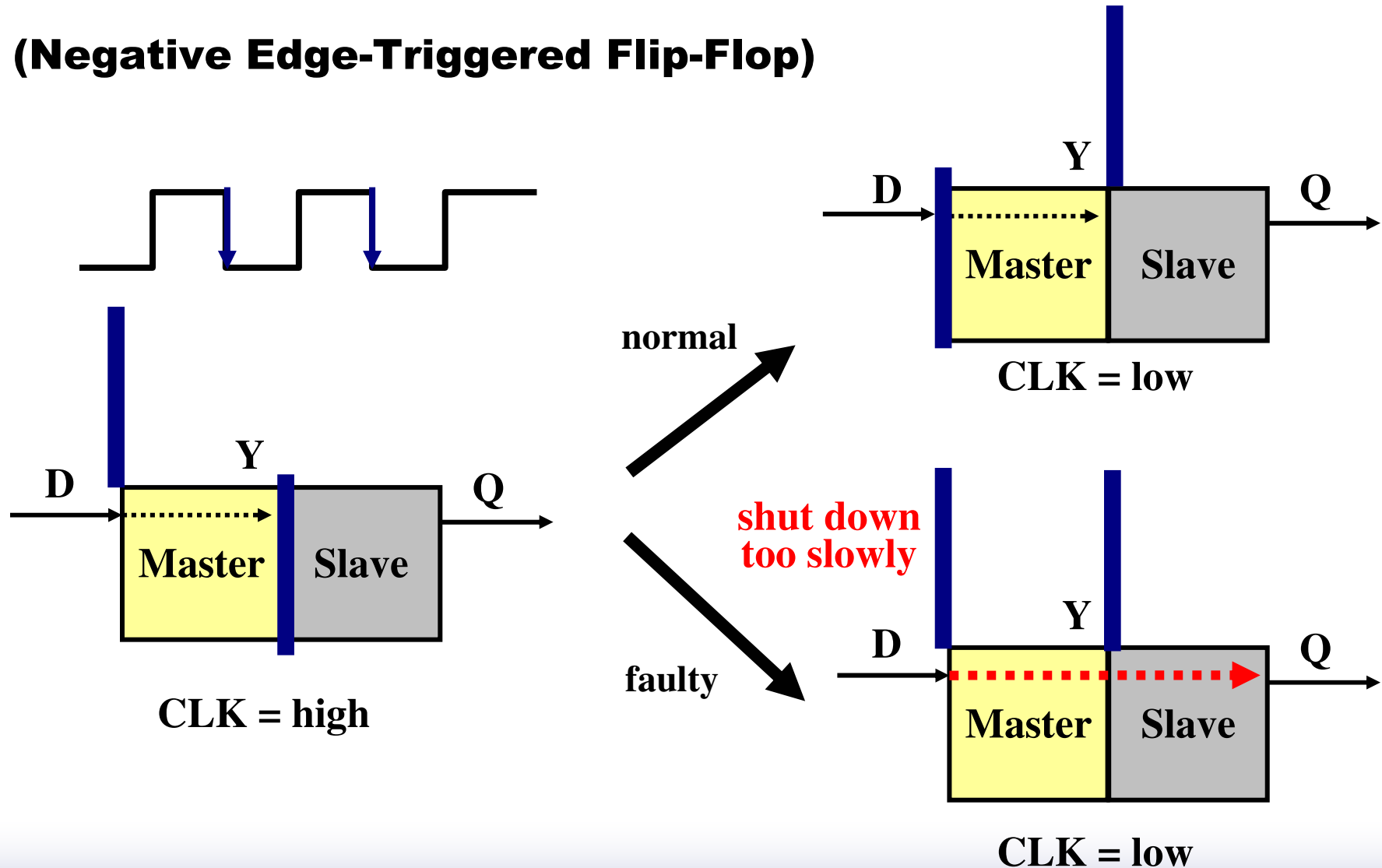

Example: Faulty Syndrome of a Scan Chain

 


Fault Type	Scan-In Pattern	Observed Syndrome
Stuck-at-0	1100110011001100	<u>0000000000000000</u>
Stuck-at-1	1100110011001100	<u>1111111111111111</u>
Slow-to-Rise	1100110011001100	<u>1</u> 000 <u>1</u> 000 <u>1</u> 000 <u>1</u> 000
Slow-to-Fall	1100110011001100	1101110111011100

The rightmost bit goes into the scan first


The rightmost bit gets out of the scan first

A underlined bit in the observed image is failing.

 Augmentation of a Flip-Flop for Easy Diagnosis




(a) A normal scan flip-flop.

 

(b) A modified scan flip-flop for easy inversion.


Fault Location via Inversion Operation

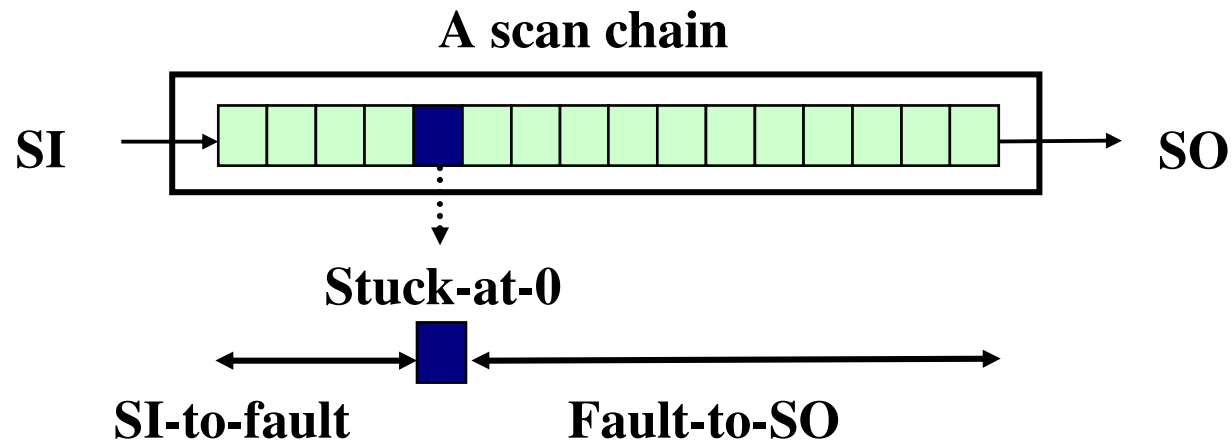

- (1) Original bitstream pattern = (111111111111111)
- (2) After scan-in: snapshot image = (1111000000000000)
- (3) After inversion: snapshot image = (0000011111111111)
- (4) After scan-out: observed image = (0000011111111111)


The fault location is at the edge between 0's and 1's

Scan Chain Diagnosis Flow

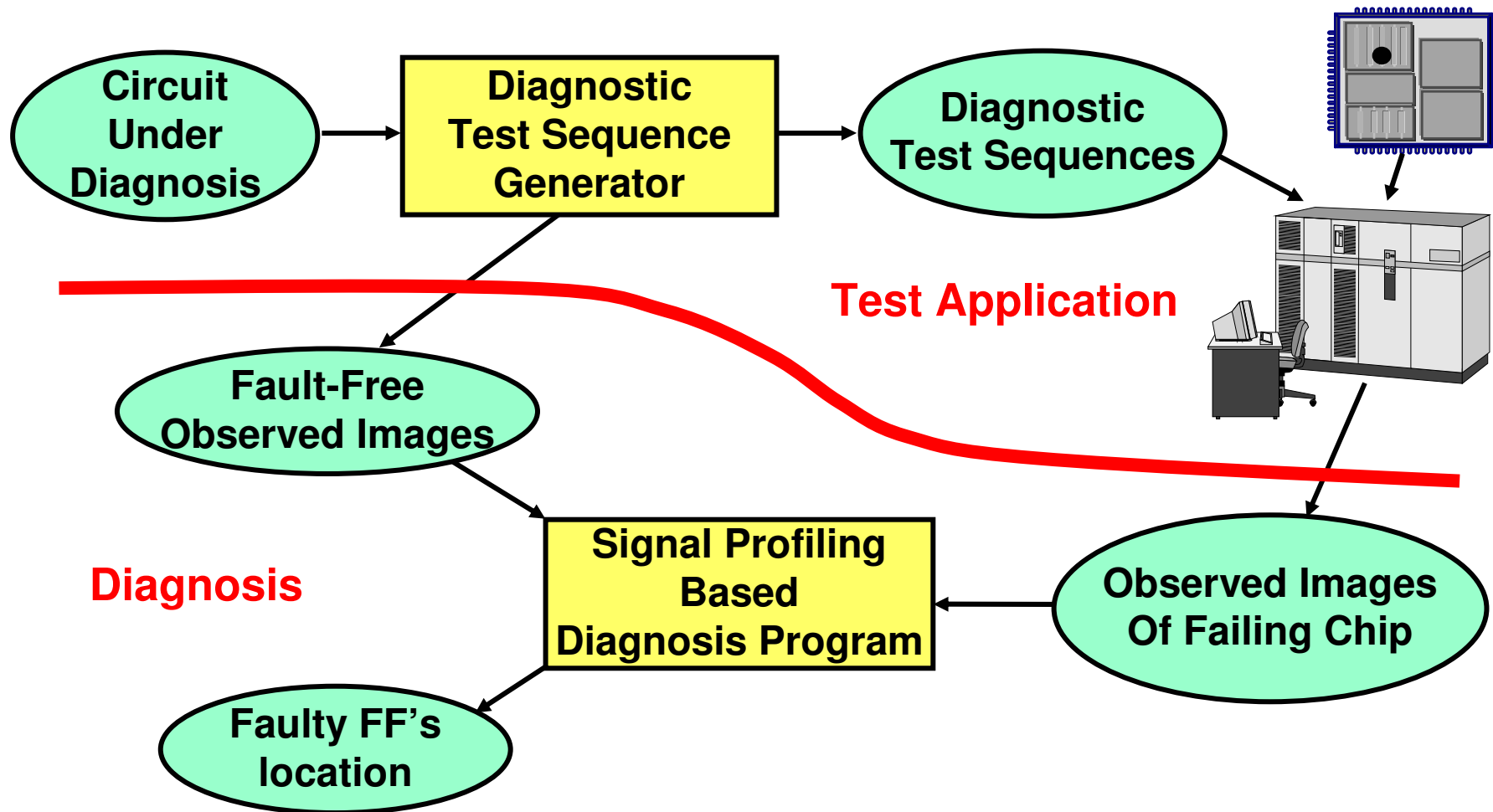

Definition: Snapshot Image

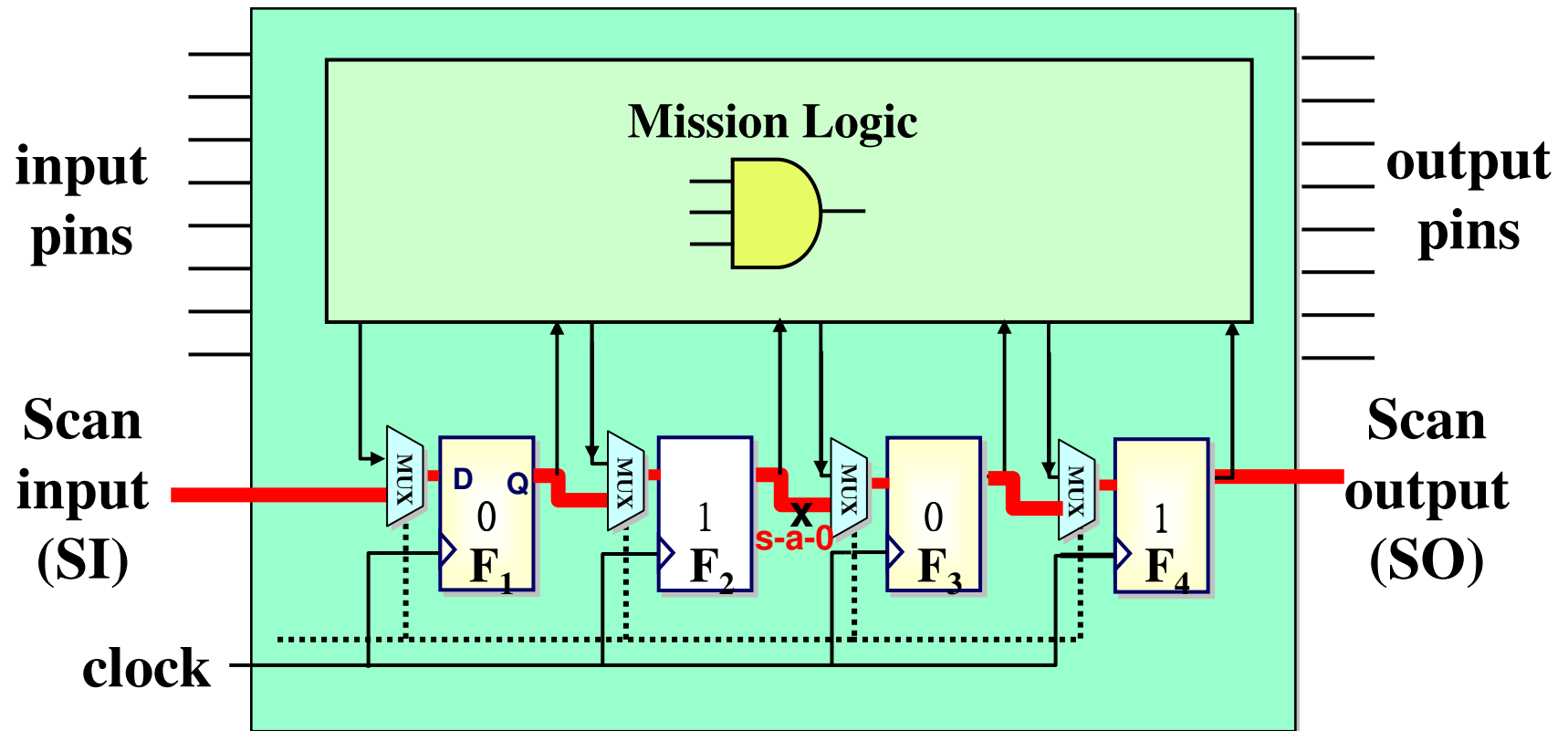
Def: A snapshot image is the combination of flip-flop values at certain time instance



Snapshot image: $\{(F_1, F_2, F_3, F_4) \mid (0, 1, 0, 1)\}$

Definition: Observed Image

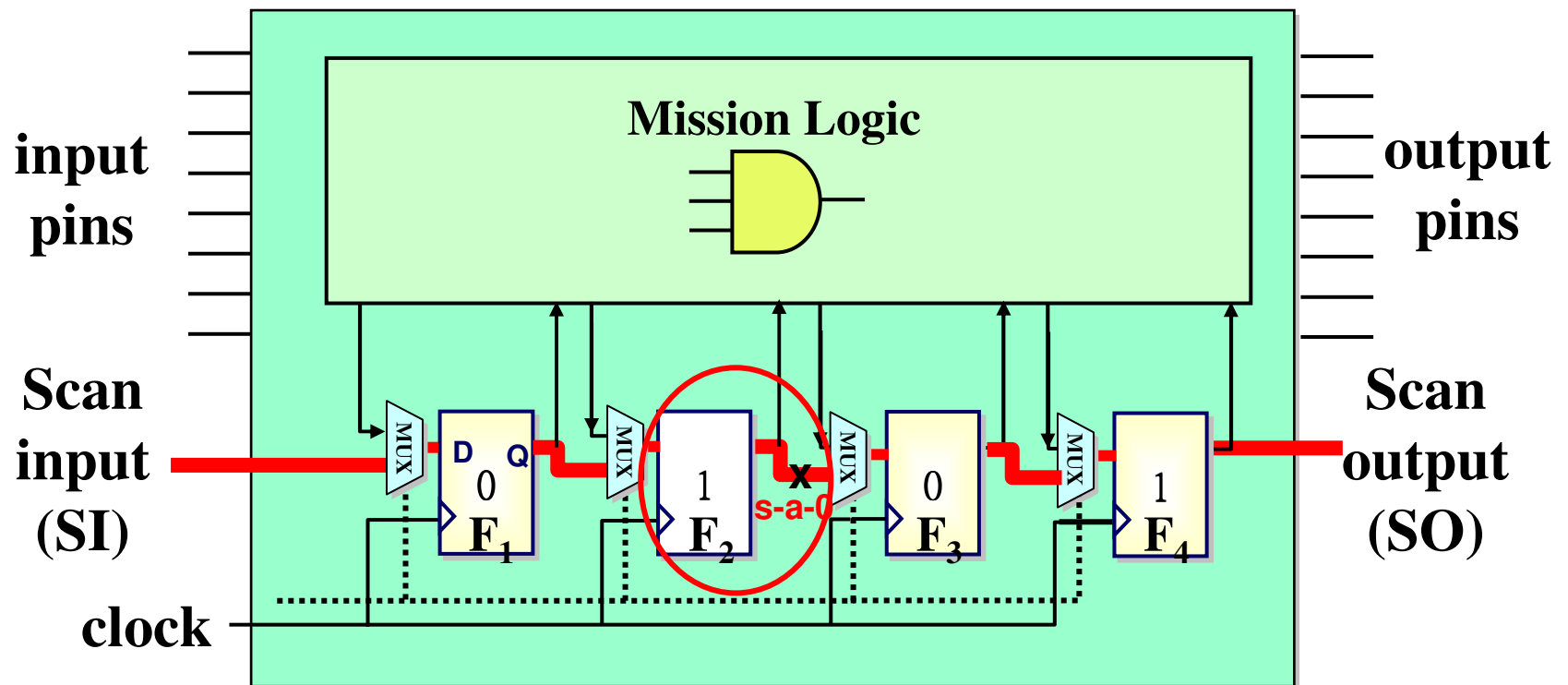Def: An observed image is the scanned-out version of a snapshot image.




Snapshot image: $\{(F_1, F_2, F_3, F_4) \mid (0, 1, 0, 1)\}$

Observed image: $\{(F_1, F_2, F_3, F_4) \mid (0, 0, 0, 1)\}$



Modified Inject-and-Evaluate Paradigm

Step 1: Scan-in an ATPG pattern

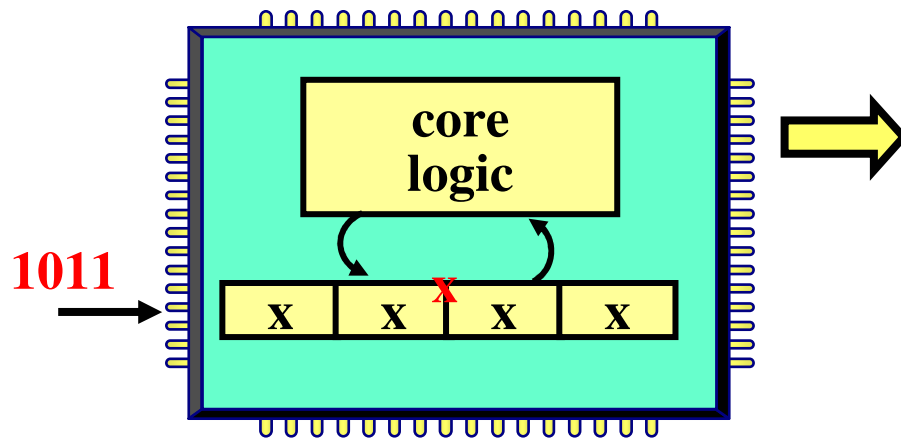

A stuck-at-0 fault is assumed at the output of the 2nd FF from SI


Step 2: Capture the response to FF's

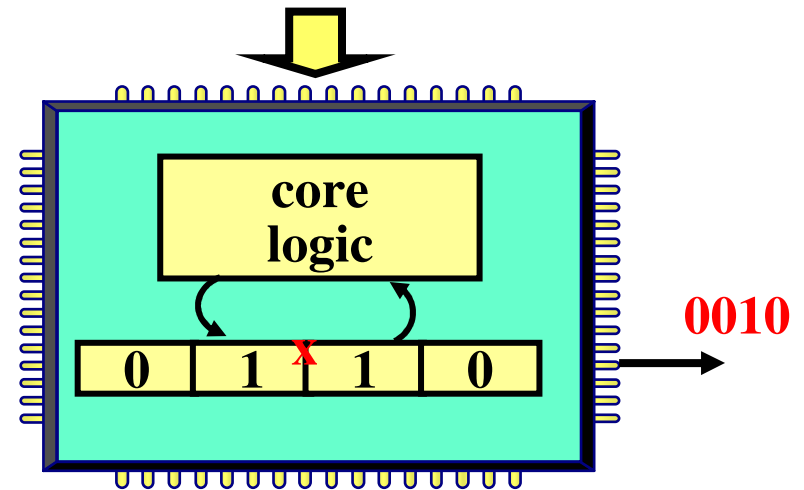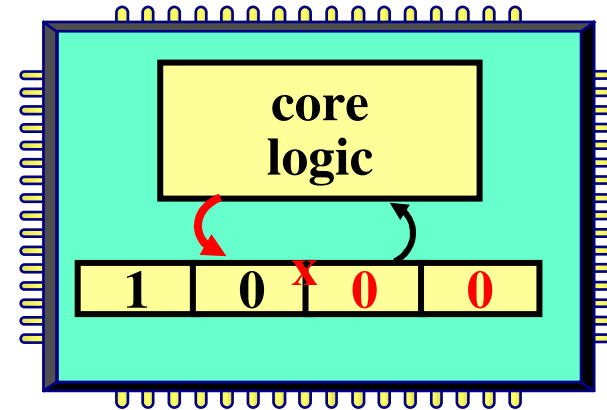

Step 3: Scan-out and compare

Test Application: Run-and-Scan

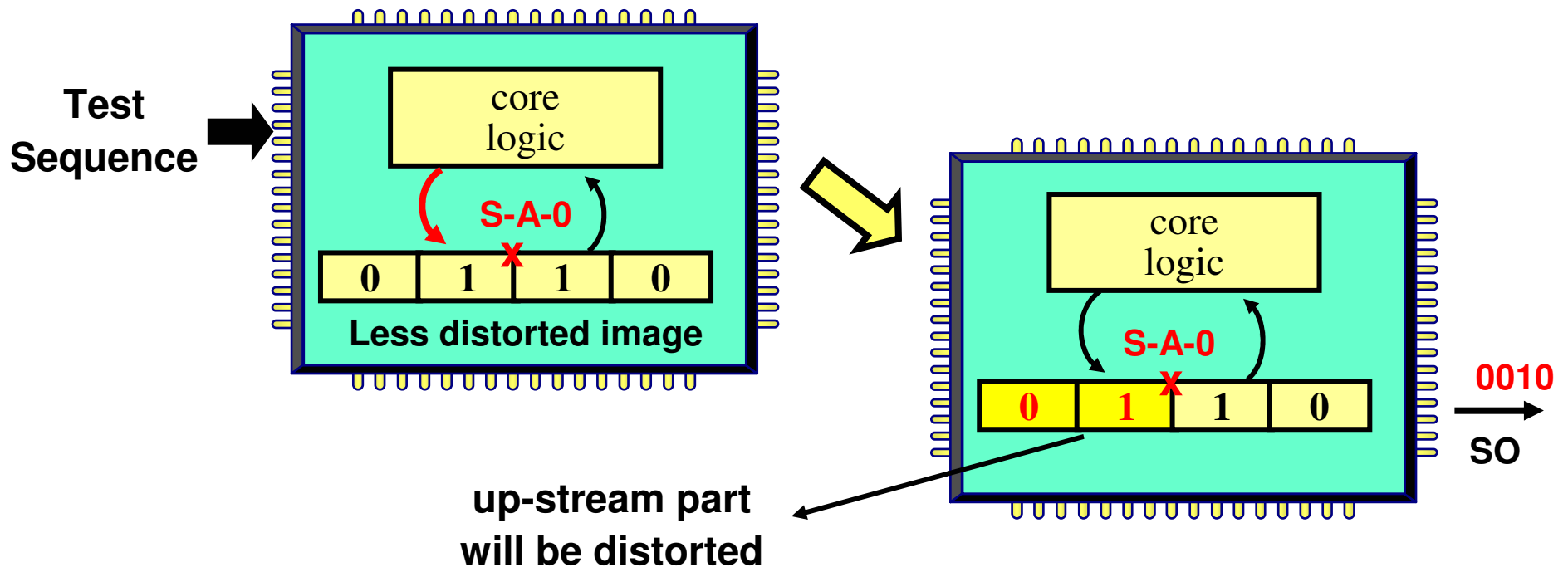Step 1: Apply a test sequence from PI's
→ Setting up a snapshot image at FF's




Step 2: Scan-out an observed image

The fault location is embedded in the observed image


Signal Profiling

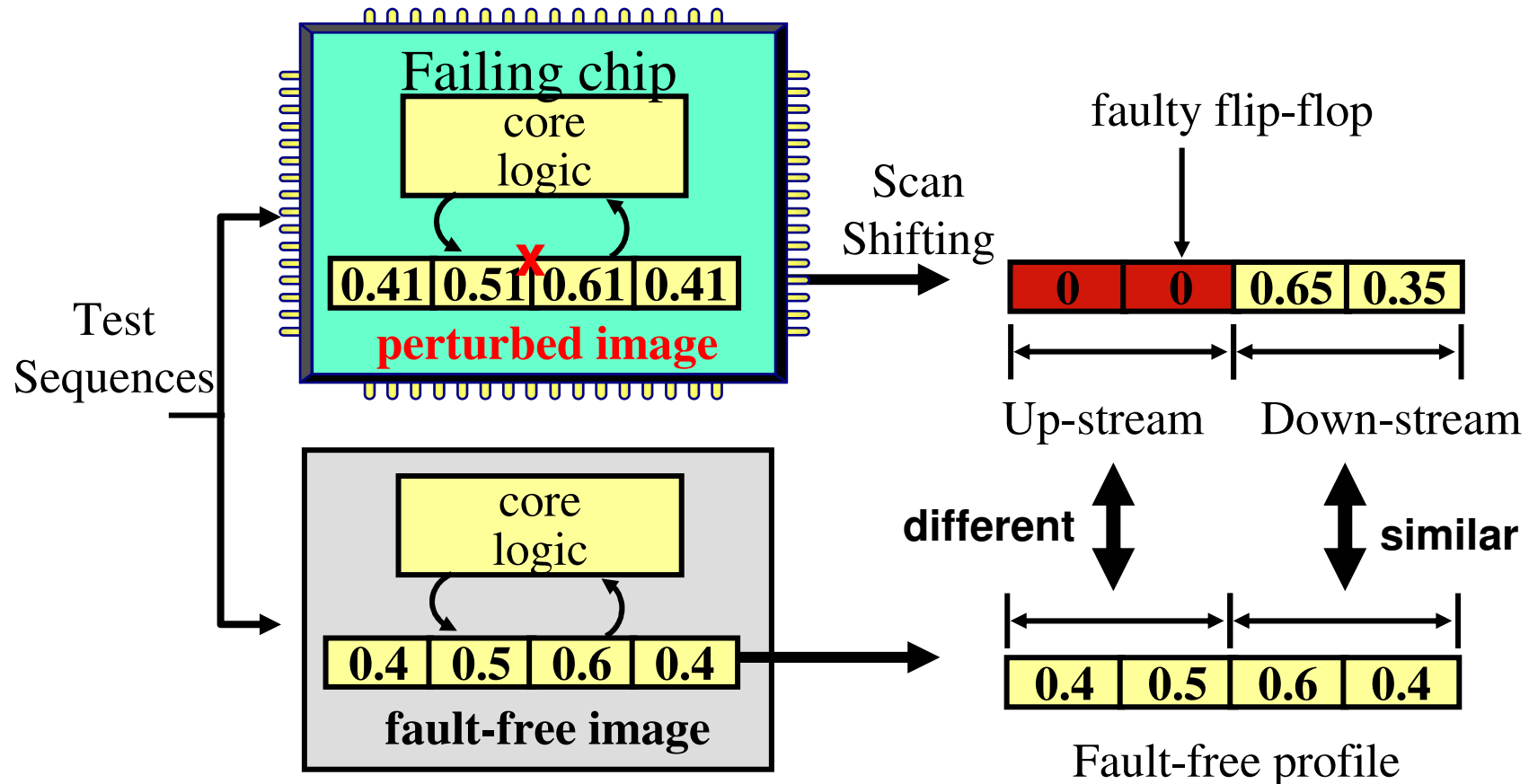A **profile** is the **distribution of certain statistics of the flip-flops**.




**Comparing failing profile with the fault-free profile
→ Could reveal the fault location**


Profile Analysis

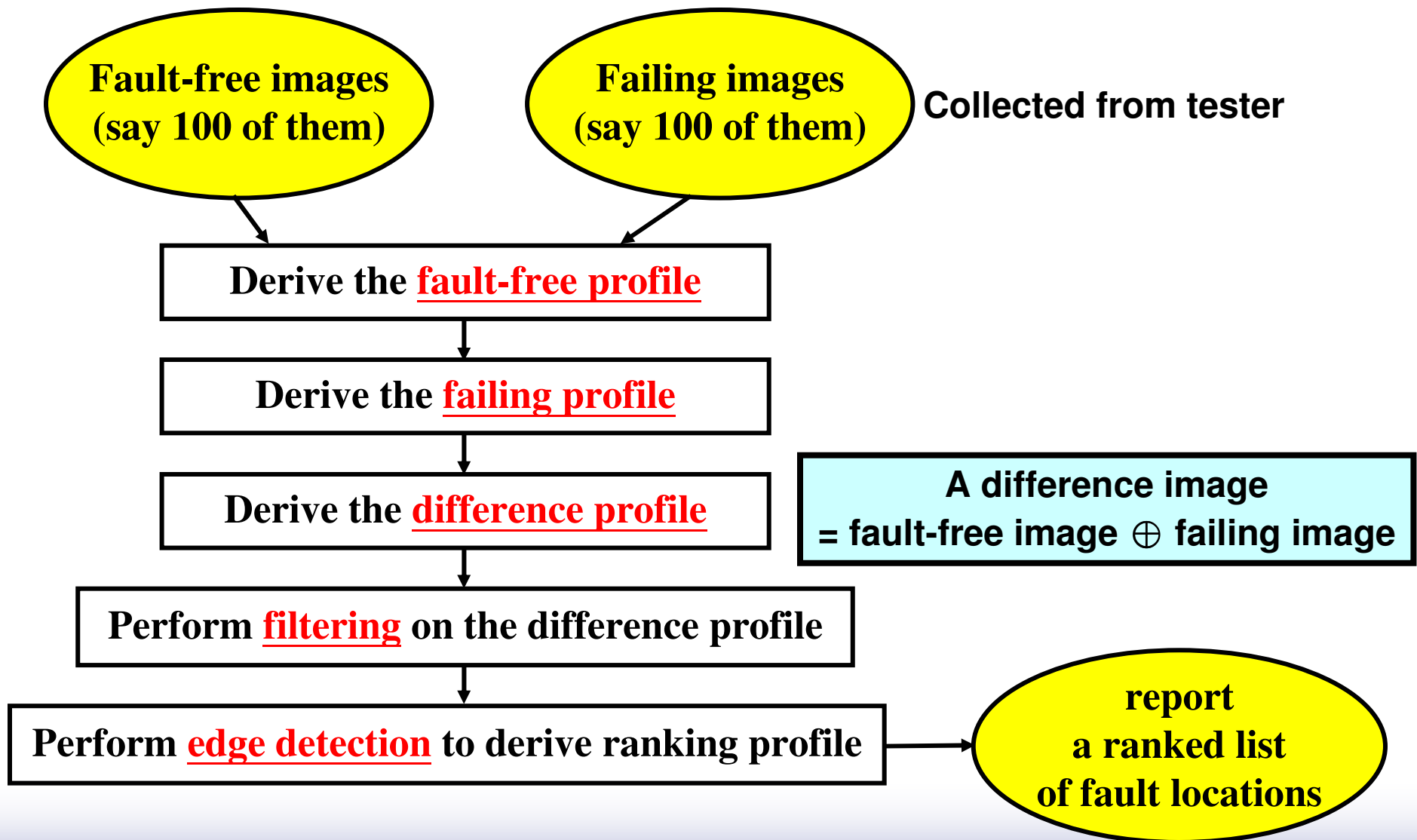

Example: Filtering & Edge Detection

 

Filtering & Edge Detection

 

Computation of Average-Sum Filtering

- (Average-sum filtering) Assume that the difference profile is given and denoted as $D[i]$, where i is the index of a flip-flop. We use the following formula to compute a smoothed difference profile, $SD[i]$:

$$SD[i] = 0.2*(D[i-2]+ D[i-1]+ D[i]+ D[i+1]+ D[i+2])$$

Computation of Edge Detection

- ❑ The true location of the faulty flip-flop is likely to be the *left-boundary of the transition region in the difference profile*. To detect this boundary, we can use a simple *edge detection formula* defined below.
- ❑ (Edge detection) On the smoothed difference profile $SD[i]$, the following formula can be used to compute the faulty frequency of each flip-flop as a suspicious profile.

$$suspicion [i] = [-1, -1, -1, 1, 1, 1] \cdot \begin{bmatrix} |SD[i] - SD[i - 3]| \\ |SD[i] - SD[i - 2]| \\ |SD[i] - SD[i - 1]| \\ SD[i] - SD[i + 1] \\ SD[i] - SD[i + 2] \\ SD[i] - SD[i + 3] \end{bmatrix}$$


Summary of Scan Chain Diagnosis

- ❑ **Hardware Assisted**
 - Extra logic on the scan chain
 - Good for stuck-at fault
- ❑ **Fault Simulation Based**
 - To find a faulty circuit matching the syndromes [Kundu 1993] [Cheney 2000] [Stanley 2000]
 - Tightening heuristic → upper & lower bound [Guo 2001][Y. Huang 2005]
 - Use single-excitation pattern for better resolution [Li 2005]
- ❑ **Profiling-Based Method**
 - Locate the fault directly from the difference profiles obtained by run-and-scan test
 - Applicable to bridging faults
 - Use signal processing techniques such as filtering and edge detection

Outline

- ❑ Introduction
- ❑ Combinational Logic Diagnosis
- ❑ Scan Chain Diagnosis
- ➔ ❑ **Logic BIST Diagnosis**
 - **Overview**
 - **Interval-Based Method**
 - **Masking-Based Method**
- ❑ Conclusion

A Logic BIST Architecture

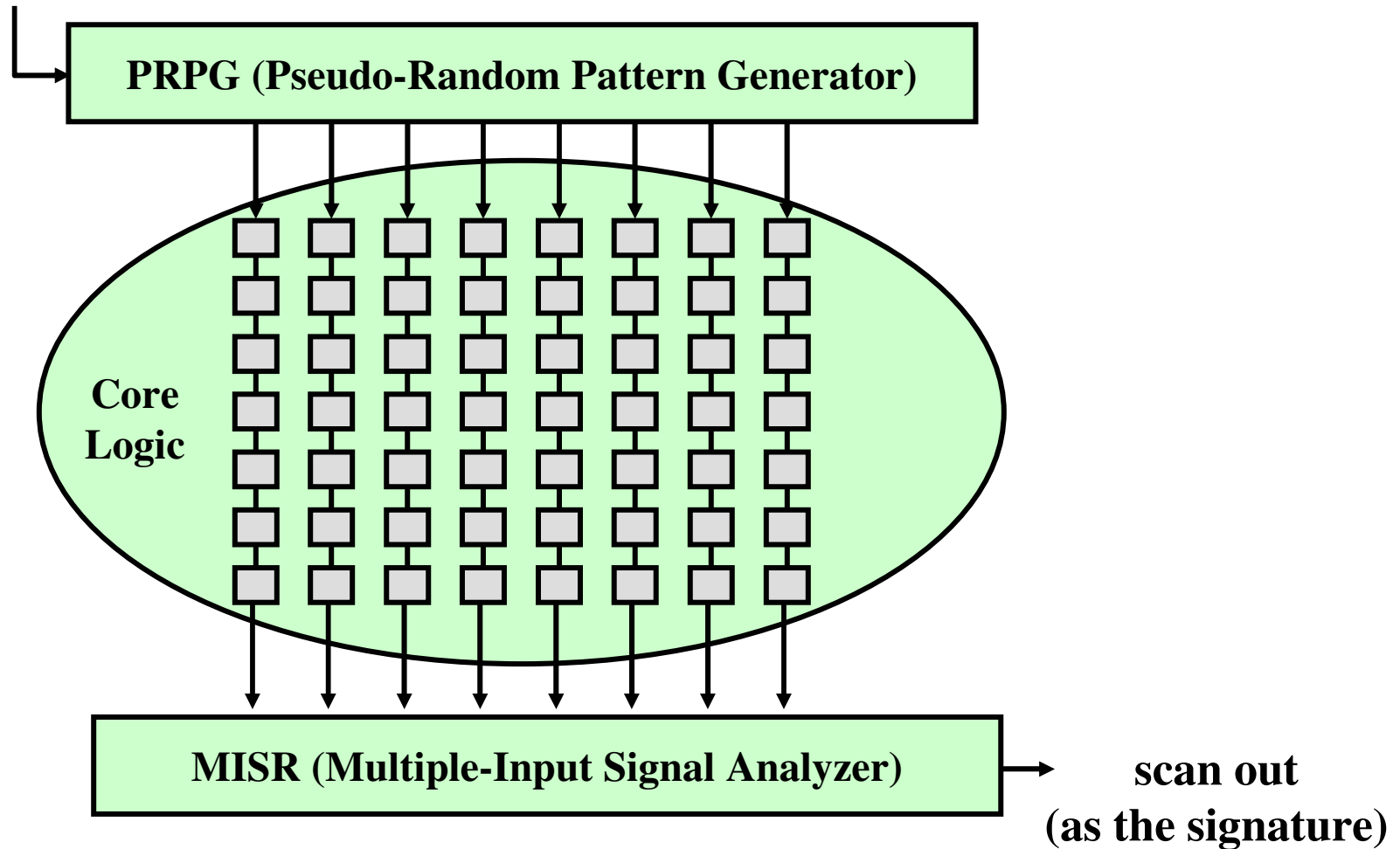


All flip-flops are assumed to be observable through scan chains.


Diagnosis for BISTed Logic

- **Diagnosis in a BIST environment requires**
 - **determining from compacted output responses which test vectors have produced a faulty response (*time information*)**
 - **determining from compacted output responses which scan cells have captured errors (*space information*)**
- **The true fault location inside the logic**
 - **Can then be inferred from the above space and time information using previously discussed combinational logic diagnosis**

 Binary Search To Locate 1st Failing Vector




Interval Unloading-Based Diagnosis

 

**A signature is scanned out to the tester
for comparison at the end of each interval**


Deterministic Masking-Based Diagnosis

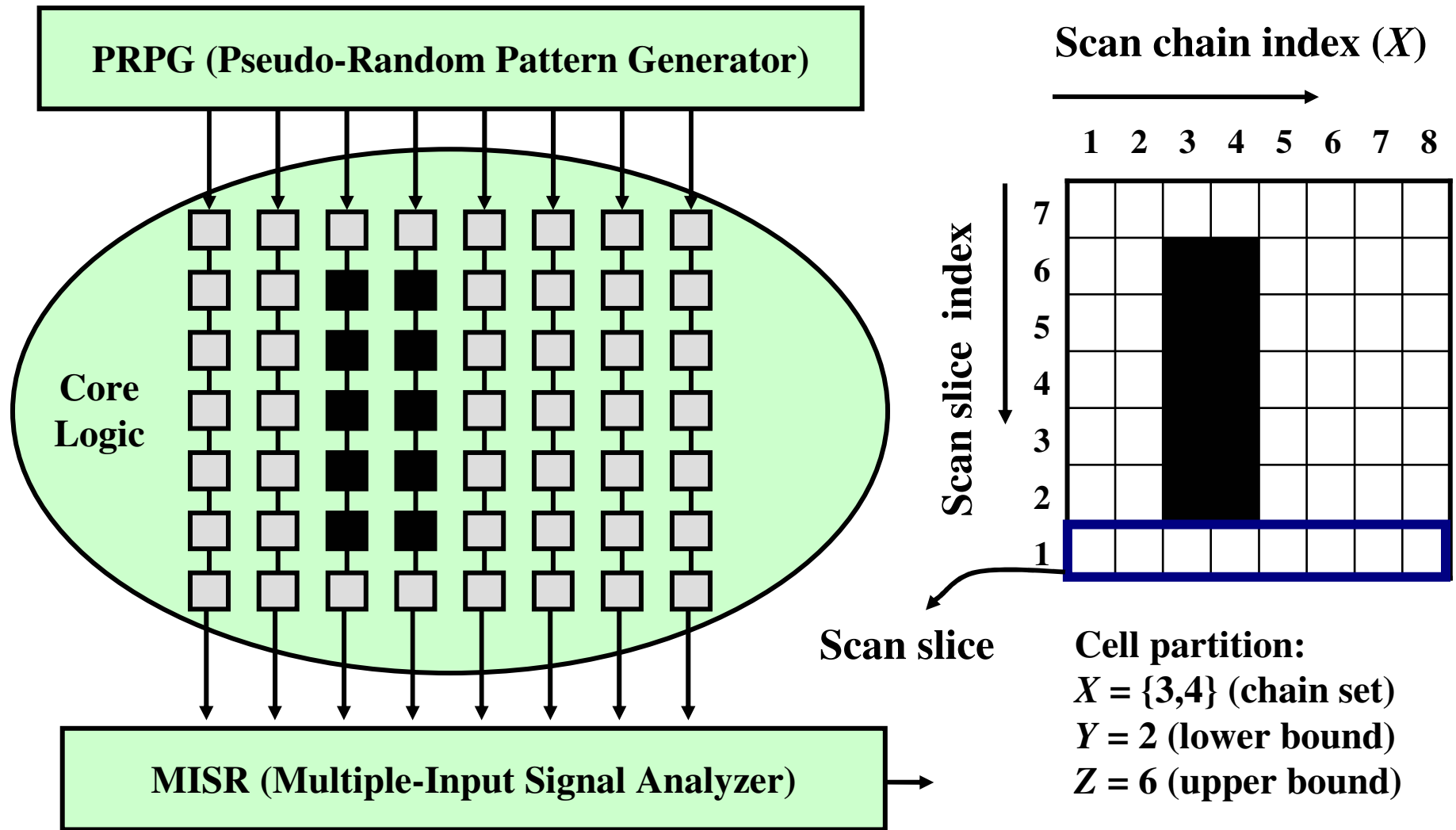


(a) STUMP-based BIST architecture

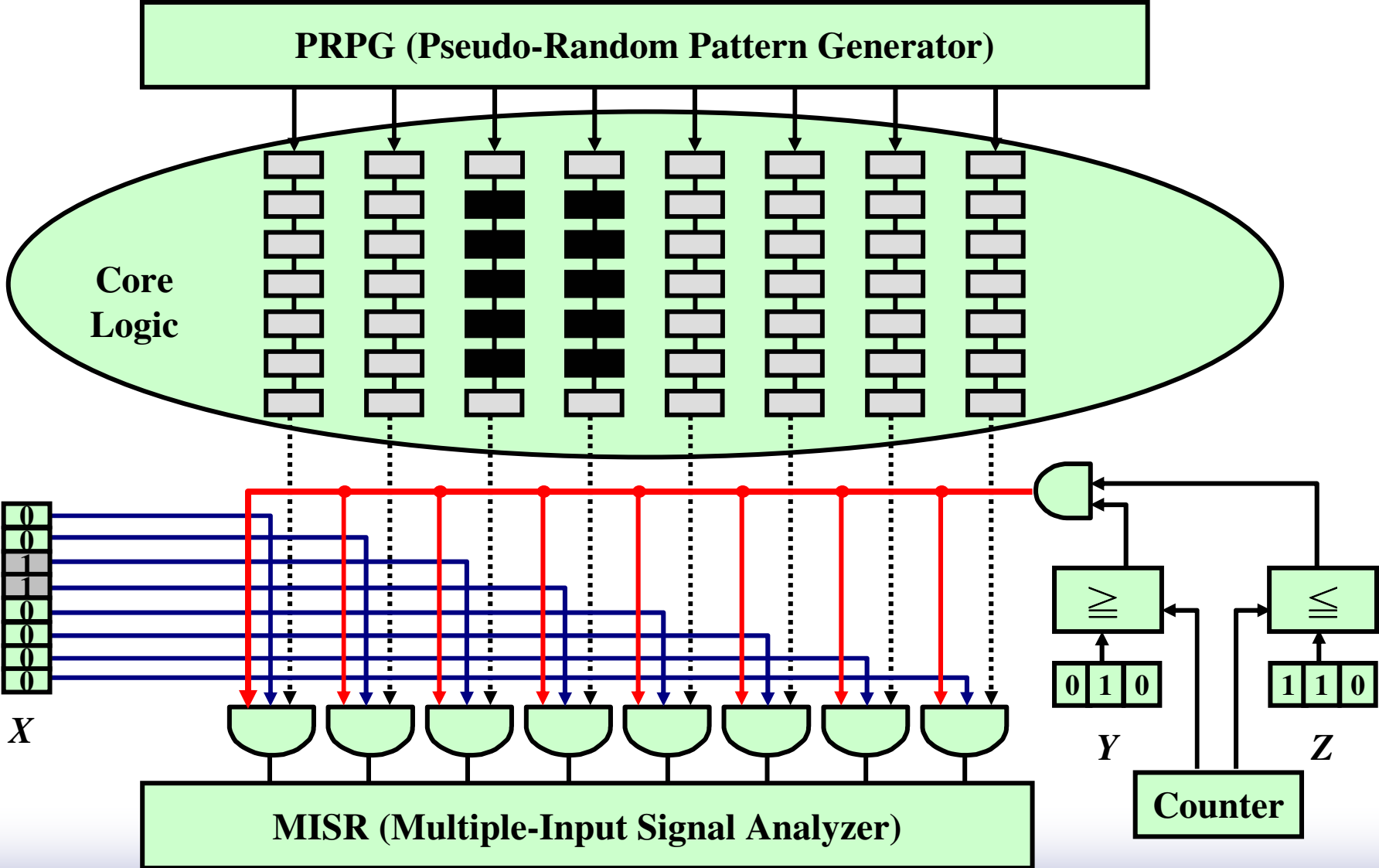(b) Scan cell matrix


Circuitry to Support Deterministic Masking



A Search for Scan Cells Capturing Errors

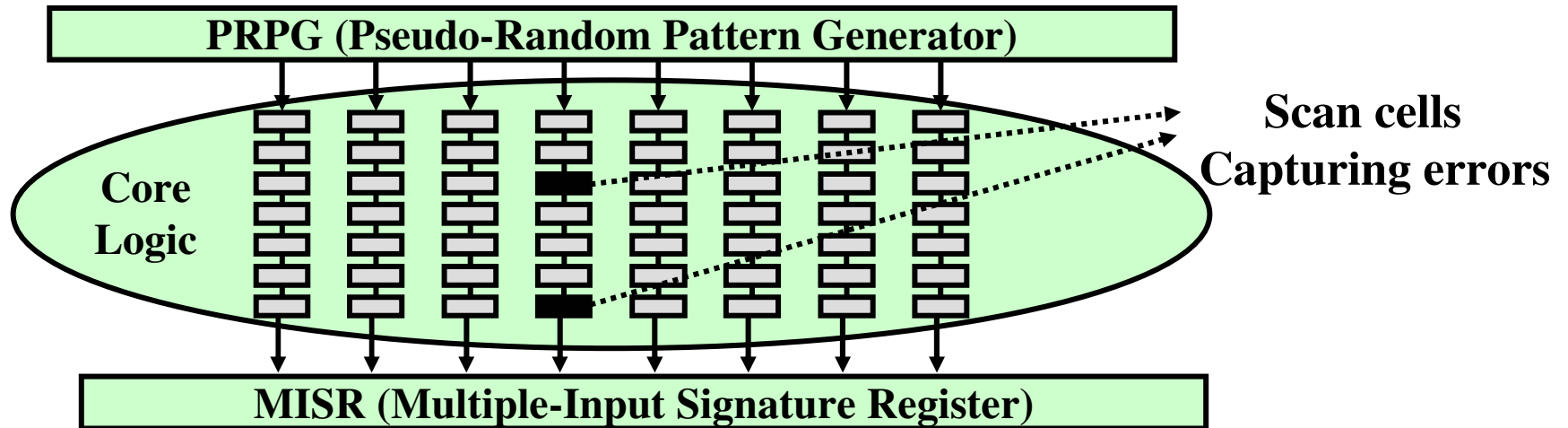

 (a) Scan cells capturing errors in the fourth scan chain



(b) The search tree

Conclusions

- ❑ **Logic diagnosis for combinational logic**
 - Has been mature
 - Good for not just stuck-at faults, but also bridging faults
- ❑ **Scan chain diagnosis**
 - Making good progress ...
 - Fault-simulation-based, or signal-profiling based
- ❑ **Diagnosis of scan-based logic BIST**
 - Hardware support is often required
 - Interval-unloading, or masking-based
- ❑ **Future challenges**
 - Performance (speed) debug
 - Diagnosis for logic with on-chip test compression and decompression
 - Diagnosis for parametric yield loss due to nanometer effects