

# *Chapter 11*

## Analog and Mixed-Signal Testing

## *What is this chapter about?*

- Introduces AMS circuits, failure modes and fault models.
- Addresses analog testing, including DC and AC parametric testing.
- Discusses mixed-signal circuits, ADC and DAC, and their testing approaches.
- Studies IEEE Std. 1149.4, the standard for mixed-signal test buses

# ***Chapter 11***


## ***Analog and Mixed-Signal Testing***

- Introduction
- Analog Circuit Testing
- Mixed-Signal Testing
- IEEE Std. 1149.4 Standard for Mixed-Signal Test Bus
- Concluding Remarks


# *11.1 Introduction*

- ❑ **Analog Circuit Properties**
- ❑ Analog Defect Mechanism and Fault Models

 
# *Analog, Digital, and Mixed-Signal Signals*



Analog

 

Mixed-Signal

 

Digital


# Analog Circuit Properties

- ❑ Continuous Signal
- ❑ Large Range of Circuits
- ❑ Nonlinear Characteristics
- ❑ Feedback Ambiguity
- ❑ Complicated Cause-Effect Relationship
- ❑ Absence of Suitable Fault Model
- ❑ Accurate Measurements Required




# Properties - Continuous Signal

## Digital Signal

 

- Logic 1, Logic 0
- $V_{IH}$ ,  $V_{IL}$ ,  $V_{OH}$ ,  $V_{OL}$
- Rise Time, Fall Time
- Propagation Delay H-L/L-H
- Noise Margin High/Low

## Analog Signal

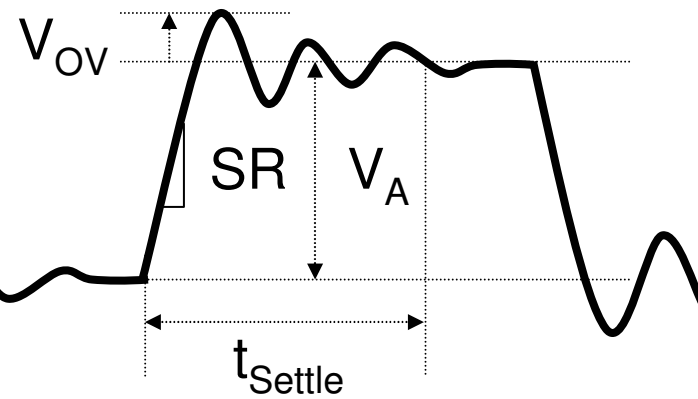

- Voltage/Current
- Slew Rate
- Overshoot
- Damping Factor
- Frequency
- Bandwidth

# *Properties - Large Ranges of Circuits*

## **Digital Circuits**

- Operation
  - Static Logic
  - Dynamic Logic
- Structure
  - Gates
  - PLA
  - Memory



## **Analog Circuits**

- Operation
  - Current Mode
  - Voltage Mode
  - Switching Cap
- Structure
  - Amplifier
  - Multiplier
  - Rectifier
  - Resonator



 
 
# Properties- Nonlinear Characteristics

- Analog circuits are nonlinear in nature
- Nonlinear cause effect



 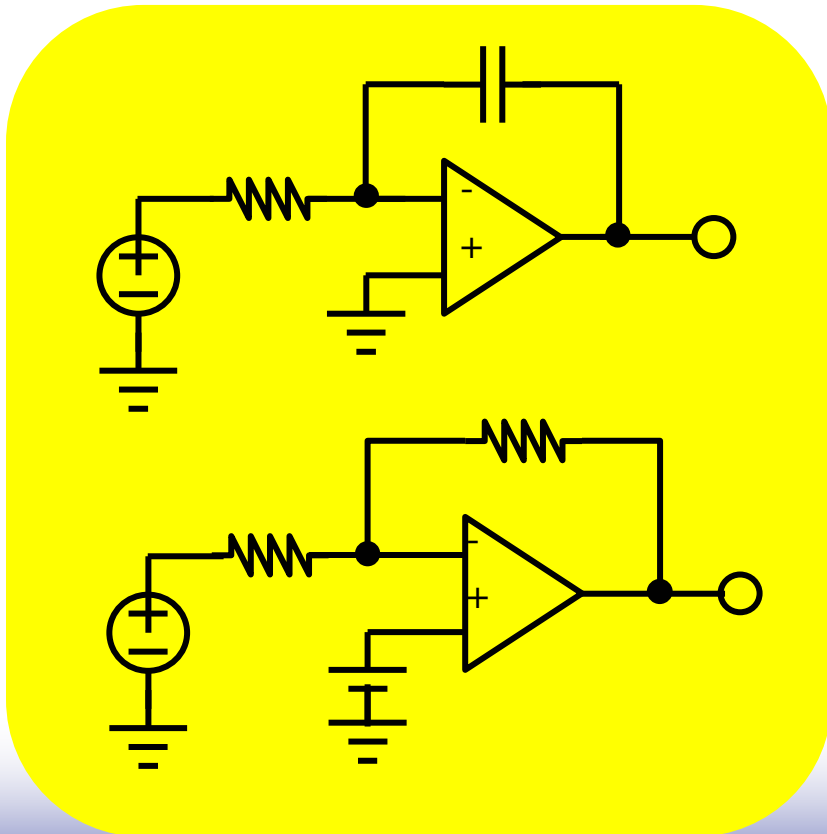
# Properties- Feedback Ambiguities

- Feedback puts circuit parameters together
- Difficult to identify fault location



 
# **Properties- Complicated Cause-Effect Relationship**

- Difficult to determine the cause of error.


 
$$A_V = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$



$$A = \frac{V_o}{V_i} = -\frac{A}{\left(1 + \frac{A}{R_2}\right)R_1}$$

# *Properties* – Absence of Suitable Fault Models

## **Digital Faults**

- Good Logic Fault Model
- Generally Accepted
  - Stuck-at-1, Stuck-at-0
  - Stuck-Open, Stuck-On
  - Short. Open
  - Memory Faults
  - PLA Faults

# *Properties - Absence of Suitable Fault Models*

## Analog Faults

- No Good Fault Model
- Not Generally Accepted
  - Open Short
  - Missing/Extra Devices
  - Parameter Variation
  - Performance Deviation
  - Circuit Structure Related
  - Functional Faults
  - ??????????????

# *Properties* — Accurate Measurements Required

## Digital Instrument

- Oscilloscope
- Function Generator
- Logic Analyzer
- Frequency Counter

# *Properties* – Accurate Measurements Required

## Analog Instrument

- Oscilloscope
- Function Gen
- Freq. Counter
- Spectrum Analyzer
- Network Analyzer
- Impedance Analyzer
- Timing Analyzer
- Communication Analyzer
- RF Instrument
- Optical Instrument
- Microwave Instrument

# *11.1 Introduction*

- Analog Circuit Properties
- **Analog Defect Mechanism and Fault Models**



# *Defect Mechanisms (1)*

## □ **Material Defects**

- cracks
- crystal imperfection
- surface impurities
- ion migration

## □ **Processing Faults**

- oxide thickness
- mobility change
- impurity density
- diffusion depth
- dielectric constants
- metal sheet resistance
- missing contacts
- dust

# ***Defect Mechanisms (2)***


## **□ Time-Dependent Failures**

- dielectric breakdown
- electron migration

## **□ Packaging Failures**


- contact degradation
- seal leakage

# *Analog Fault Model*

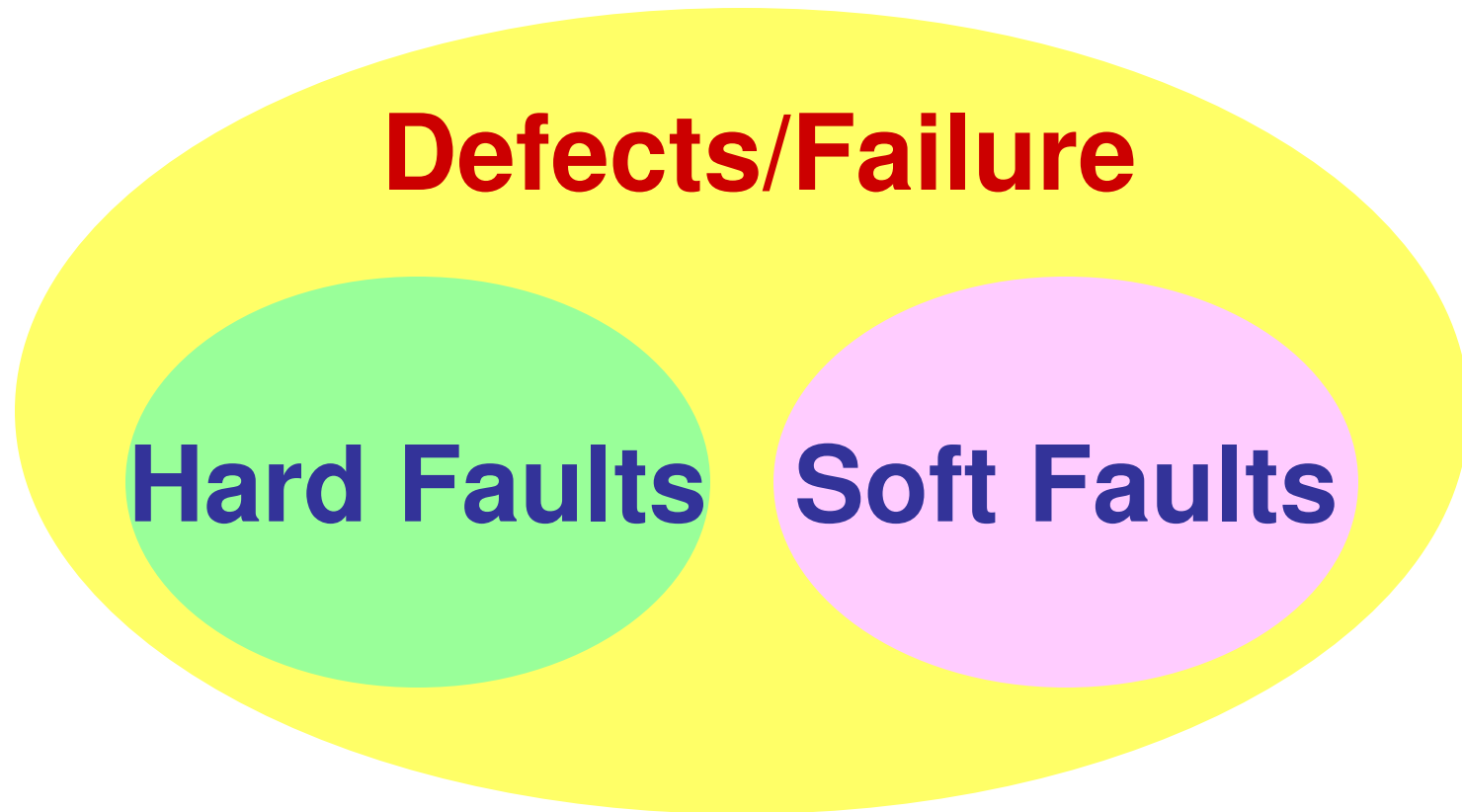

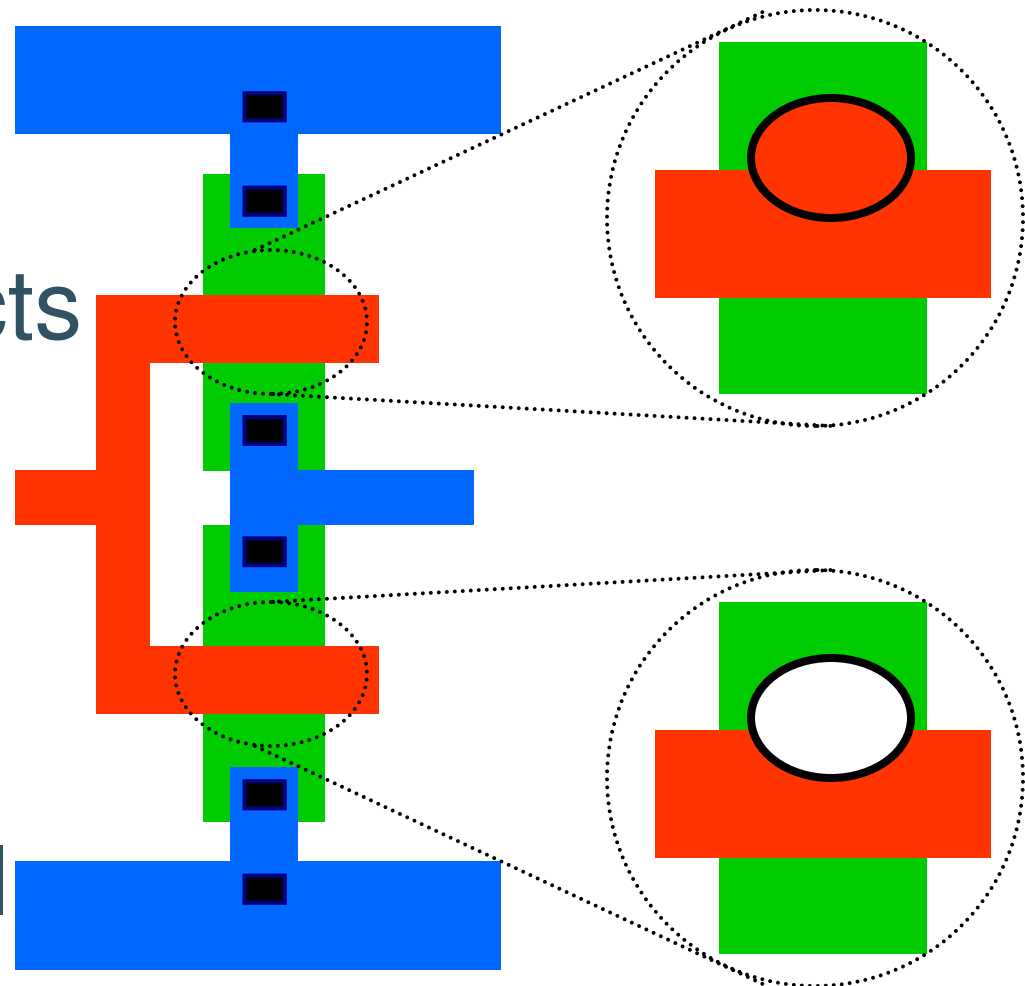
# *Analog Faults - Defect*

- Defects
  - Extra Defects
  - Etching Defects
- Source
  - Dust
  - Lithography
- Layout Oriented
- Statistical Model



 
# Analog Faults - Hard Faults

- Fault Models
  - Open ●
  - Short —
  - Missing Device ■
  - Extra Devices ■
- Faulty Effects
  - Catastrophic Error
  - Module Malfunction
  - System Failure


 
# Analog Faults - Soft Faults

- Parametric Faults
  - $I_o$ :  $100\mu A \rightarrow 50\mu A$
  - $W$ :  $20\mu m \rightarrow 10\mu m$
- Deviation Faults
  - $f_o$ :  $10\text{MHz} \rightarrow 5\text{MHz}$
  - $\text{Gain}$ :  $10000 \rightarrow 2000$
- Sources
  - Mobility
  - Oxide Thickness
  - Impurity Density
  - Diffusion Depth
  - Dielectric Constants
  - Metal Sheet Resistance



# *Analog Fault - Model Mapping*


**Functional Level**

□ Deviation Faults



**Circuit Level**

□ Parametric Faults

 


**Layout Level**

□ Extra Defects


□ Etching Defects

# Analog Faults - Model Mapping

 
 
## Layout to Parametric

- Defect Statistics
  - Randomly insert dusts of random size.
- Parameter Statistics
  - Simulate the effect of dust on transistor parameters







# Analog Faults - Model Mapping
  
## Parametric to Deviation

- Use SPICE simulation and statistics to derive the performance deviation.







# 11.1 Summary

- Studied the analog test properties
  - Nonlinearity, Feedback Ambiguity
  - No good fault model
- Overview the analog test plan
  - Test Code, Binning, Sequence Control
  - Focused Calibrations, DIB Checkers
  - Characterization and Simulation Code
- Analog Fault Model
  - Extra and Etching Defects
  - Parametric and Deviation faults
  - Model Mapping

## ***11.2 Analog Circuit Testing***

- ❑ **Analog Test Approaches**
- ❑ Analog Test Waveforms
- ❑ DC Parametric Testing
- ❑ AC Parametric Testing

# Analog Testing

 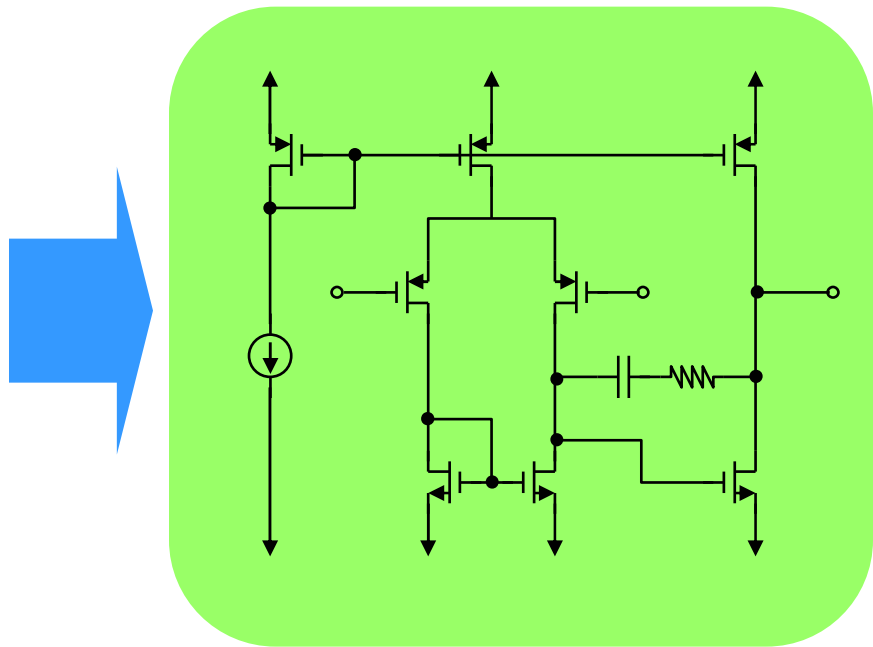  

**Spec  
Oriented**

**Waveform  
Oriented**

# Specification Oriented Test

## OP777/OP727/OP747—SPECIFICATIONS

### ELECTRICAL CHARACTERISTICS (@ $V_S = 5.0\text{ V}$ , $V_{CM} = 2.5\text{ V}$ , $T_A = 25^\circ\text{C}$ unless otherwise noted.)

| Parameter                            | Symbol                   | Conditions   | Min  | Typ      | Max | Unit                         |
|--------------------------------------|--------------------------|--|------|----------|-----|------------------------------|
| <b>INPUT CHARACTERISTICS</b>         |                          |  |      |          |     |                              |
| Offset Voltage OP777                 | $V_{OS}$                 | $+25^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 20       | 100 | $\mu\text{V}$                |
|                                      |                          | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 50       | 200 | $\mu\text{V}$                |
| Offset Voltage OP727/OP747           |                          | $+25^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 30       | 160 | $\mu\text{V}$                |
|                                      |                          | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 60       | 300 | $\mu\text{V}$                |
| Input Bias Current                   | $I_B$                    | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 5.5      | 11  | nA                           |
| Input Offset Current                 | $I_{OS}$                 | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 0.1      | 2   | nA                           |
| Input Voltage Range                  |                          |  | 0    |          | 4   | V                            |
| Common-Mode Rejection Ratio          | CMRR                     | $V_{CM} = 0\text{ V to }4\text{ V}$                              | 104  | 110      |     | dB                           |
| Large Signal Voltage Gain            | $A_{VO}$                 | $R_L = 10\text{ k}\Omega$ , $V_O = 0.5\text{ V to }4.5\text{ V}$ | 300  | 500      |     | V/mV                         |
| Offset Voltage Drift OP777           | $\Delta V_{OS}/\Delta T$ | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 0.3      | 1.3 | $\mu\text{V}/^\circ\text{C}$ |
| Offset Voltage Drift OP727/OP747     | $\Delta V_{OS}/\Delta T$ | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 0.4      | 1.5 | $\mu\text{V}/^\circ\text{C}$ |
| <b>OUTPUT CHARACTERISTICS</b>        |                          |  |      |          |     |                              |
| Output Voltage High                  | $V_{OH}$                 | $I_L = 1\text{ mA}$ , $-40^\circ\text{C to }+85^\circ\text{C}$   | 4.88 | 4.91     |     | V                            |
| Output Voltage Low                   | $V_{OL}$                 | $I_L = 1\text{ mA}$ , $-40^\circ\text{C to }+85^\circ\text{C}$   |      | 126      | 140 | mV                           |
| Output Circuit                       | $I_{OUT}$                | $V_{DROPOUT} < 1\text{ V}$                                       |      | $\pm 10$ |     | mA                           |
| <b>POWERSUPPLY</b>                   |                          |  |      |          |     |                              |
| Power Supply Rejection Ratio         | PSRR                     | $V_S = 3\text{ V to }30\text{ V}$                                | 120  | 130      |     | dB                           |
| Supply Current/Amplifier OP777       | $I_{SY}$                 | $V_O = 0\text{ V}$   |      | 220      | 270 | $\mu\text{A}$                |
|                                      |                          | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 270      | 320 | $\mu\text{A}$                |
| Supply Current/Amplifier OP727/OP747 |                          | $V_O = 0\text{ V}$   |      | 235      | 290 | $\mu\text{A}$                |
|                                      |                          | $-40^\circ\text{C} < T_A < +85^\circ\text{C}$                    |      | 290      | 350 | $\mu\text{A}$                |
| <b>DYNAMIC PERFORMANCE</b>           |                          |  |      |          |     |                              |
| Slew Rate                            | SR                       | $R_L = 2\text{ k}\Omega$   |      | 0.2      |     | V/ $\mu\text{s}$             |
| Gain Bandwidth Product               | GBP                      |  |      | 0.7      |     | MHz                          |
| <b>NOISE PERFORMANCE</b>             |                          |  |      |          |     |                              |
| Voltage Noise                        | $e_{n\text{p-p}}$        | 0.1 Hz to 10 Hz  |      | 0.4      |     | $\mu\text{V p-p}$            |
| Voltage Noise Density                | $e_n$                    | $f = 1\text{ kHz}$   |      | 15       |     | $\text{nV}/\sqrt{\text{Hz}}$ |
| Current Noise Density                | $i_n$                    | $f = 1\text{ kHz}$   |      | 0.13     |     | $\text{pA}/\sqrt{\text{Hz}}$ |

#### NOTES

Typical specifications: >50% of units perform equal to or better than the "typical" value.

Specifications subject to change without notice.


Analog Devices, Inc.™

# *Specification Oriented Test*


- Specification Oriented Test
  - Check whether all the specs are met
  - Tedious and inflexible
- Example: Operational Amplifier
  - DC Specifications
    - Input Offset Voltage
    - Input Bias Offset Current
    - Open-Loop Gain
    - Noise
    - Common Rejection Ratio
    - Temperature Drift
  - AC Specifications
    - Bandwidth
    - Harmonic Distortion
    - Slew Rate
    - Settling Time
    - Noise
 
# Waveform Oriented Test

- Waveform Oriented Test
  - Compare waveform to the simulated ones



# Waveform Oriented Test

 

|   |                                      |
|---|--------------------------------------|
| A | DC Bias, Input Offset                |
| B | Slew Rate, Damping Factor            |
| C | Overshoot, Damping Factor, Bandwidth |
| D | Settling Time, DC Gain               |




# *Analog Testing - Comparison*

- Specification Oriented Test
  - Require more test runs and time
  - Require accurate instrument
  - Specifications are guaranteed
  - ***Low defect level***
  
- Waveform Oriented Test
  - Less test runs and test time
  - More forgiving on instrument
  - Specifications are not guaranteed
  - ***Low cost***


## *11.2 Analog Circuit Testing*

- Analog Test Approaches
- **Analog Test Waveforms**
- DC Parametric Testing
- AC Parametric Testing


# *Analog Test Waveforms*

 


**Sine**

 


**Square (Step)**

 


**Ramp**

 


**Triangular**

 

**Chirp (Sweep Sine)**

 


**Arbitrary**

 

**Modulated**
 
# Waveform - Step

- For transient response testing
- Application: Filter, OPs, VCO, etc
- Difficult to generate good steps




$$\theta = \pm 45^{\circ} \sim \pm 60^{\circ}$$

$$f = \frac{1}{(4 \sim 3)T_r}$$


$$f = \frac{1}{3.5T_r}$$
 
# Waveform - Step


- Step change in voltage: Transient testing
- Step change in frequency: PLL testing
- Step change in amplitude: AGC testing



Voltage Step

 



Frequency Step

 



Amplitude Step

# Waveform - Ramp

## □ Triangular Wave Generation

  


## □ Sawtooth Wave Generation

  




 
# Waveform - Chirp

- Also called Sweep Sine
- Generation: Triangular to VCO
- Application: Frequency response plotting


   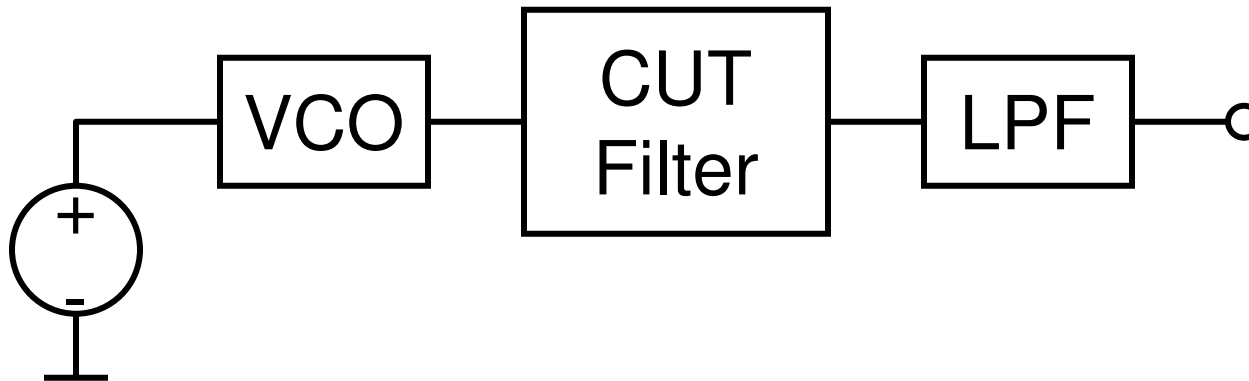
# Waveform - Chirp



- Application: Frequency response plotting




  
# *Waveform - Arbitrary*

- Synthesized by DACs
- Combinations of all kinds of waveform



# *Waveform - Modulated/Synthesized*

- Modulated/Synthesized Waveforms
  - Communication System Testing
    - GSM, CDMA, 1394, USB2, etc.
  - Modulation
    - AM, FM, PCM, PWM, QAM, PSK, QPSK
- Generated by dedicated instrument

## *11.2 Analog Circuit Testing*



- Analog Test Approaches
- Analog Test Waveforms
- **DC Parametric Testing**
- AC Parametric Testing

# ***DC Parametric Testing***

|                                       |   |
|---------------------------------------|---|
| <b>Rated output current</b>           | <b>Rated output voltage</b>             |
| <b>Open-loop gain</b>                 | <b>Slewing rate</b>                     |
| <b>Unity gain full power response</b> | <b>Unity gain small signal response</b> |
| <b>Overload recovery</b>              | <b>Input bias current</b>               |
| <b>Input offset voltage</b>           | <b>Input offset current</b>             |
| <b>Input noise</b>                    | <b>Input impedance</b>                  |
| <b>Supply voltage sensitivity</b>     | <b>Common mode rejection</b>            |
| <b>Maximum voltage between inputs</b> | <b>Maximum common mode voltage</b>      |
| <b>Temperature drift</b>              | <b>Source: [Sata 1967]</b>              |
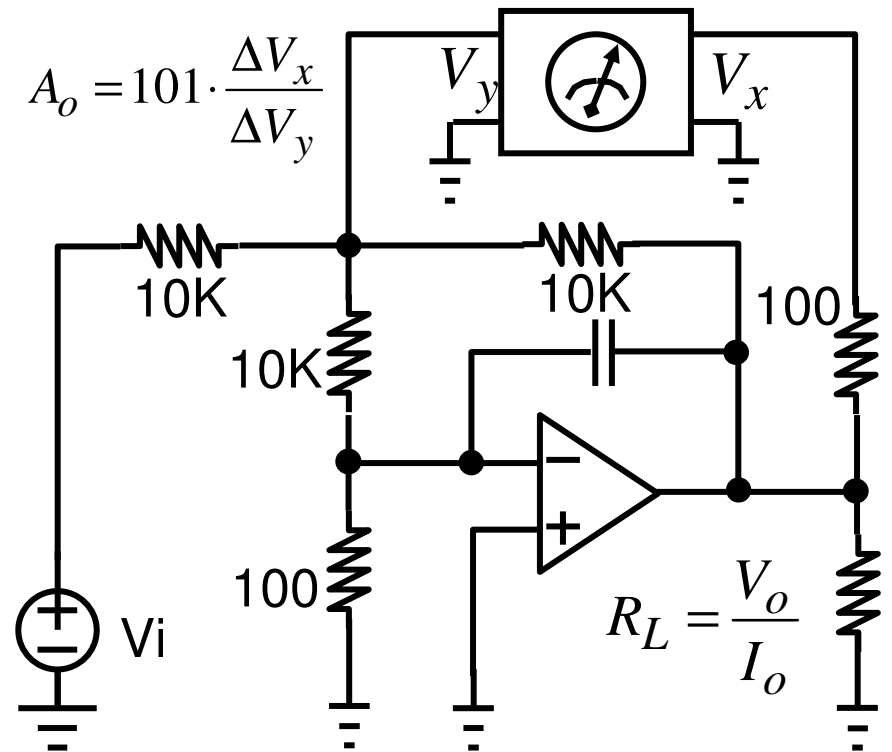 
# DC Test – Open-Loop Gain Measurement


$$A_o = 101 \cdot \frac{\Delta V_x}{\Delta V_y}$$




# DC Test – Unit Gain Bandwidth Measurement

$$f_t = A_o \cdot f_{3dB}$$

$$V_i \leq \frac{SR}{2\pi f_t}$$

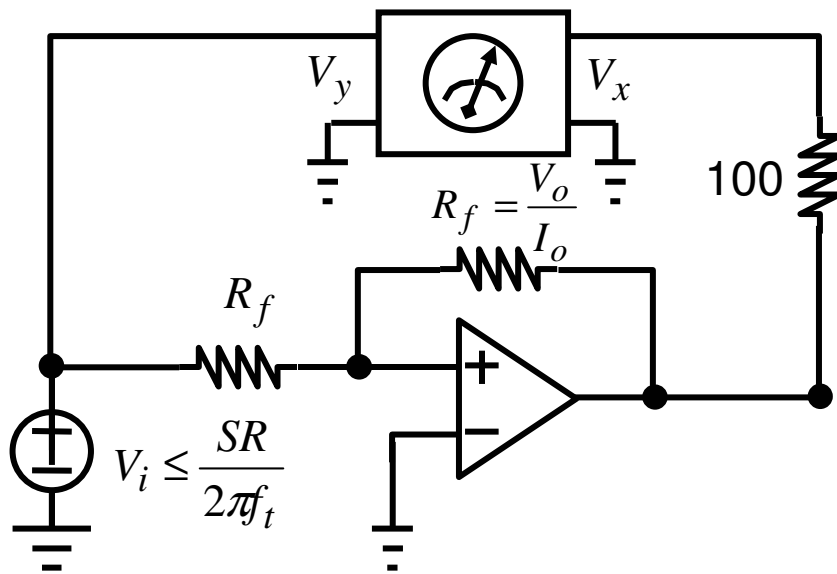


**Inverting Configuration**

 

**Noninverting Configuration**

# DC Test – Common Mode Rejection Ratio

 


$$V_{CM \cdot i} = \frac{\Delta V_o}{A_o} = \Delta V_o / \frac{R2}{R1}$$

$$CMRR = 20 \log \left( A_o / \frac{\Delta V_o}{\Delta V_{CM}} \right)$$
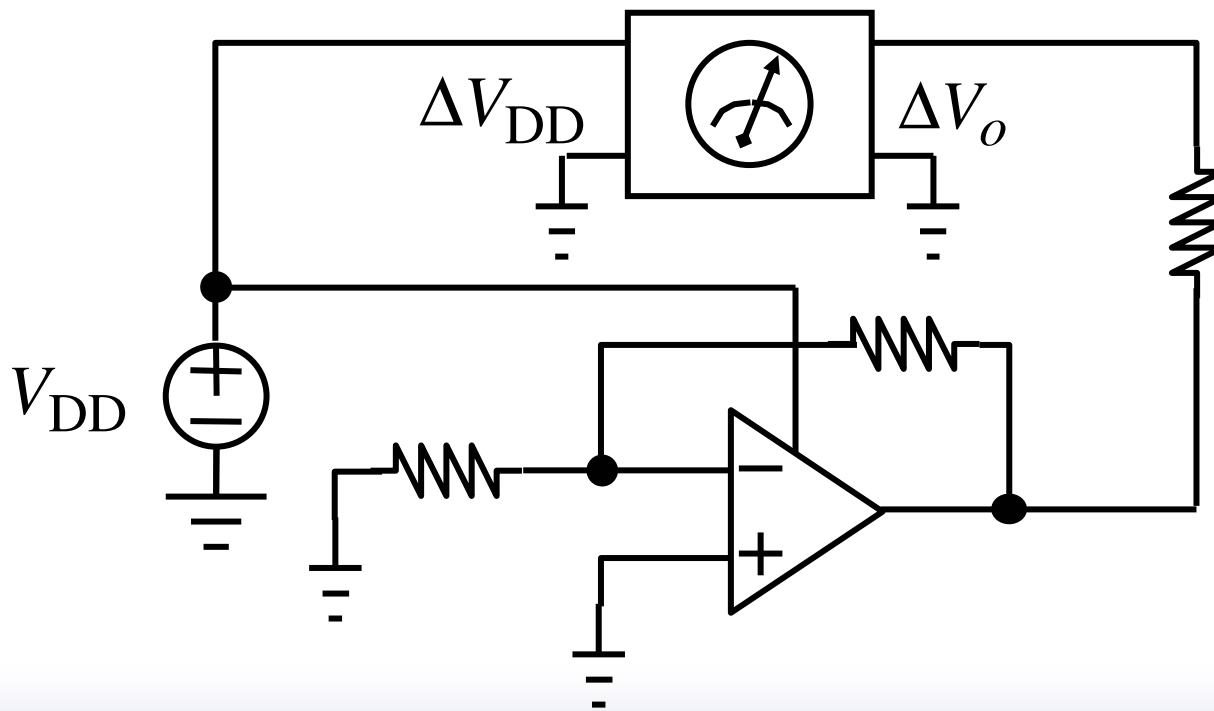
# DC Test – Power Supply Rejection Ratio

$$PSRR = 20\log\left(A_o / \frac{\Delta V_o}{\Delta V_{DD}}\right)$$






## *11.2 Analog Circuit Testing*

- Analog Test Approaches
- Analog Test Waveforms
- DC Parametric Testing
- **AC Parametric Testing**

# Analog AC Testing
 
## □ Test Types

- Gain
- Phase
- Distortion
- Signal Rejection
- Noise




## □ Test Setup





- AGW: Arbitrary Waveform Generator (DAC)
- Digitizer: Sample and convert to digital (ADC)
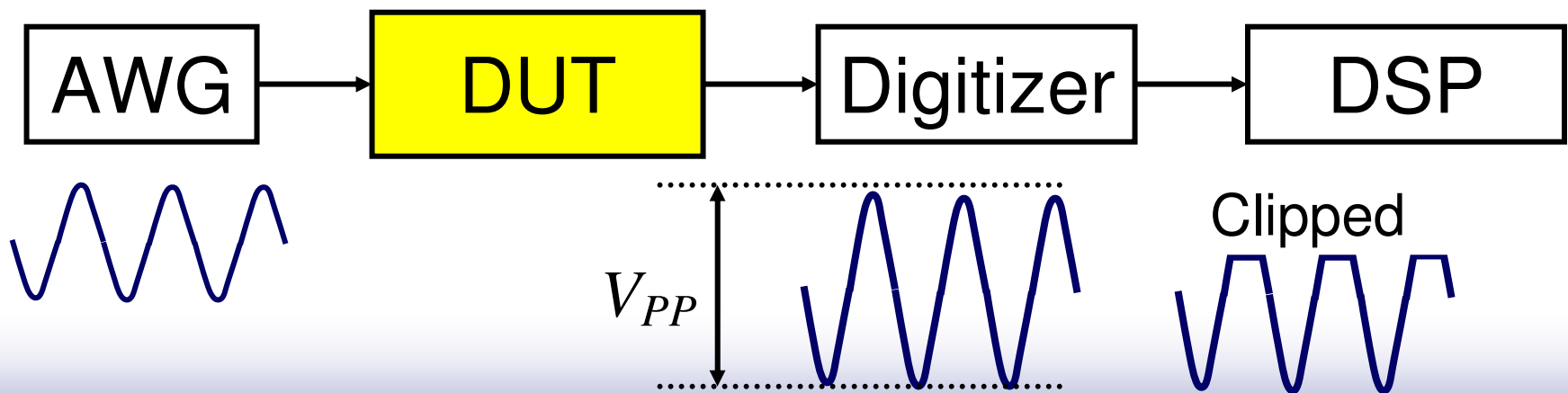
# AC – Maximal Output Amplitude

- ❑ Input sine wave (1KHz) with fixed amplitude
- ❑ Digitize the output waveform
- ❑ DSP (FFT) to eliminate distortion and noise.
- ❑ Check the fundamental amplitude.
- ❑ Detect first order defects in a circuit.
- ❑ Voltage in dBV or dBm



# AC - Frequency Response

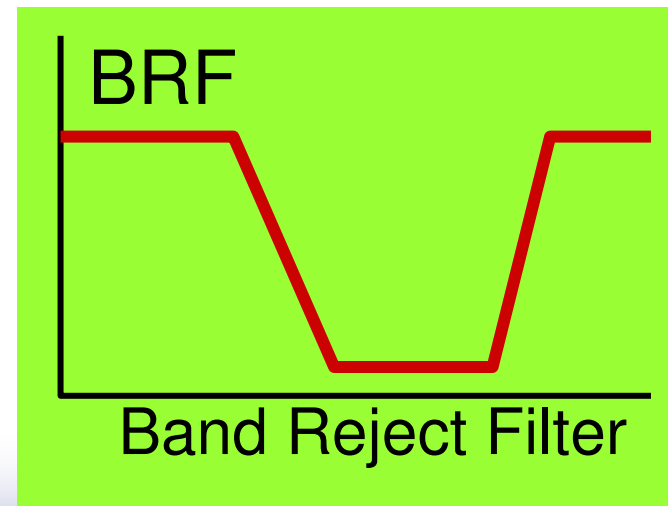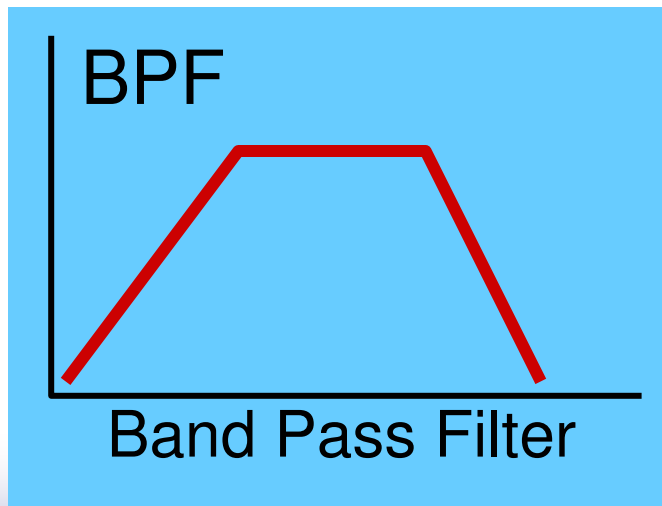  


# AC - Frequency Response

 
## Bode Plot

$$A(j\omega) = \frac{10^2 \left(1 + \frac{j\omega}{10^6}\right)}{\left(1 + \frac{j\omega}{10^2}\right) \left(1 + \frac{j\omega}{10^4}\right)}$$


- Open Loop Gain  $10^2$
- Pole 1:  $10^2$
- Pole 2:  $10^4$
- Zero:  $10^6$



# AC - Frequency Response

 


# AC - Frequency Response

 

# AC - Frequency Response

Frequencies of special interests

 



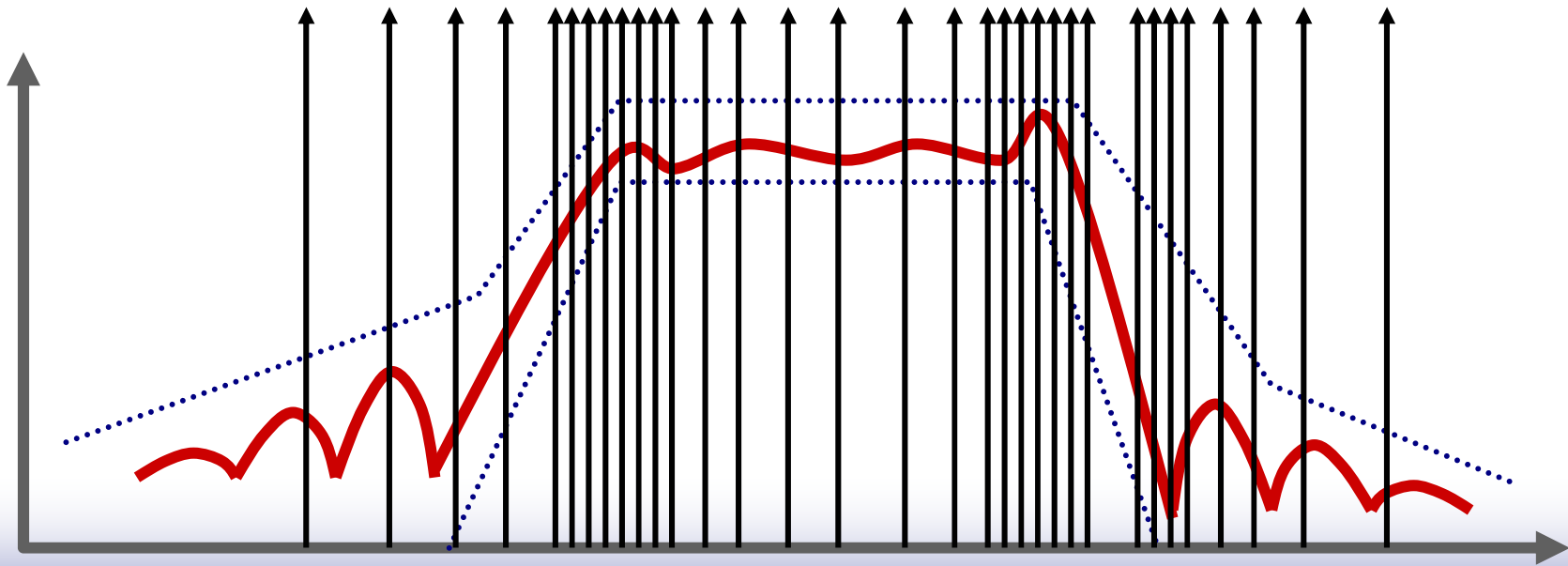
# AC - Frequency Response

- Multi-tone Test Waveform


$$A(t) = \sum_{i=1}^{i=k} A_i \sin(\omega_i t + \phi_i)$$


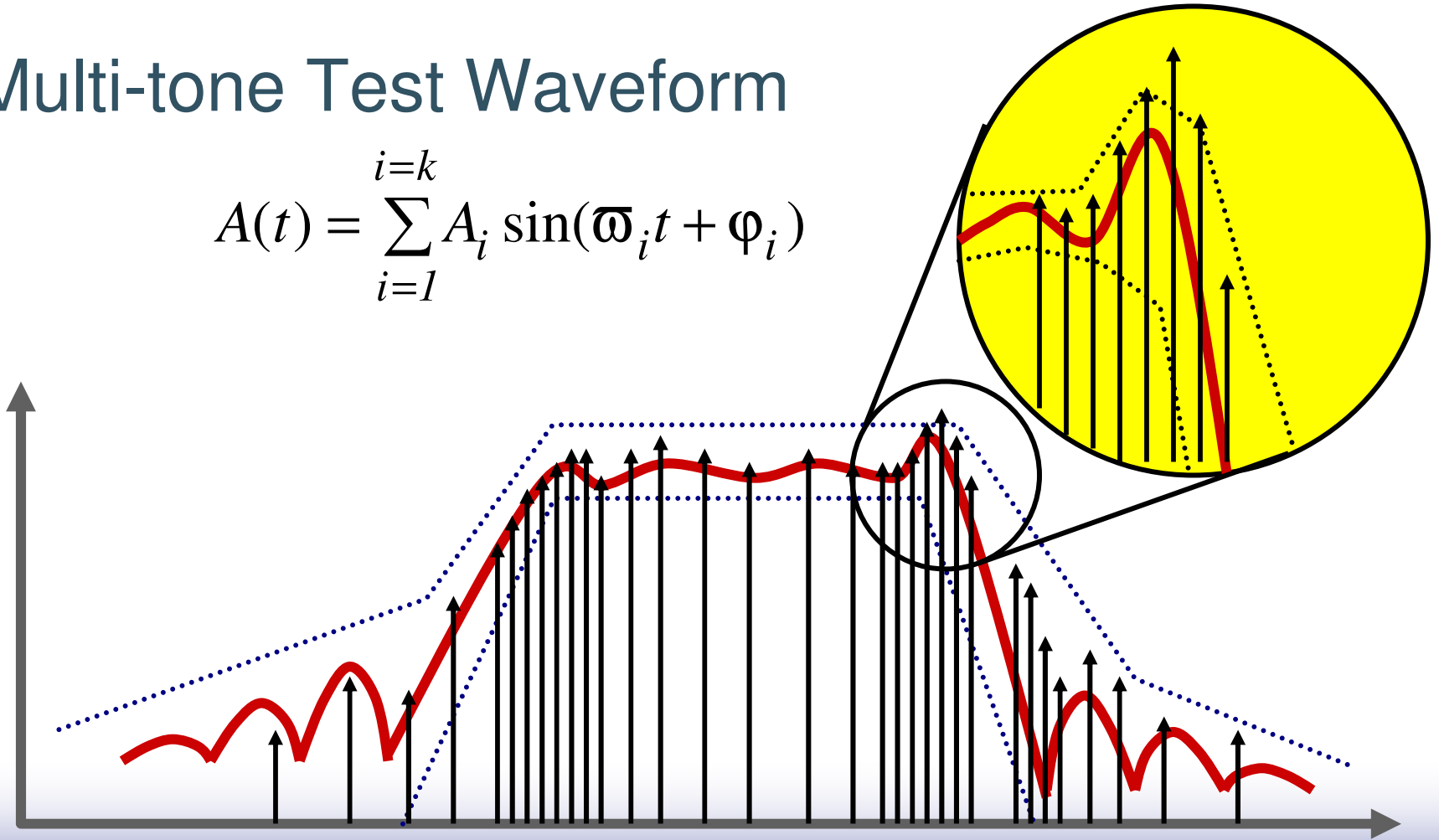
# AC - Frequency Response

- Multi-tone Test Waveform

$$A(t) = \sum_{i=1}^{i=k} A_i \sin(\omega_i t + \phi_i)$$





# AC – Noise and Distortion

- **Distortion**
  - Harmonic Distortion
  - Intermodulation Distortion
  - Crossover
- **Cause**
  - Nonlinearity of the circuit
  - Clip (saturation)
  - Mismatch of the devices
  
# AC – Noise and Distortion

- Apply sinusoidal waveform
- Do Fourier transform on response waveform
- Obtain F domain properties mathematically.




# AC – Noise and Distortion

$$THD = 10 \log \frac{F^2}{\sum H_i^2} = 100 \times \frac{F^2}{\sum H_i^2} \%$$


$$SNR = 10 \log \frac{F^2}{\sum N_i^2}$$
 
$$SNDR = 10 \log \frac{F^2}{\sum H_i^2 + \sum N_i^2}$$


 
# AC – Intermodulation Distortion

$$v(t) = A_1 \sin 2\pi f_1 t + A_2 \sin 2\pi f_2 t$$



## 11.2 Summary


- Studied the analog test approaches
  - Specification oriented testing
  - Waveform oriented testing
- Outlined the analog test waveforms
  - Sine, step, triangular, chirp, arbitrary, modulated
- Discussed DC parametric testing
  - Open-loop gain, unit gain bandwidth
  - CMRR, PSRR
- Discussed AC parametric testing
  - Use AWG, Digitizer, and DSP
  - Frequency response, Noise, and Distortion

## ***11.3 Mixed-Signal Testing***

- ❑ **Introduction to Analog-Digital Conversion**
- ❑ ADC and DAC Circuit Structure
- ❑ ADC/DAC Specification and Fault Models
- ❑ IEEE Std. 1057
- ❑ Time-Domain ADC Testing
- ❑ Frequency-Domain ADC Testing




# AD Model - Quantization

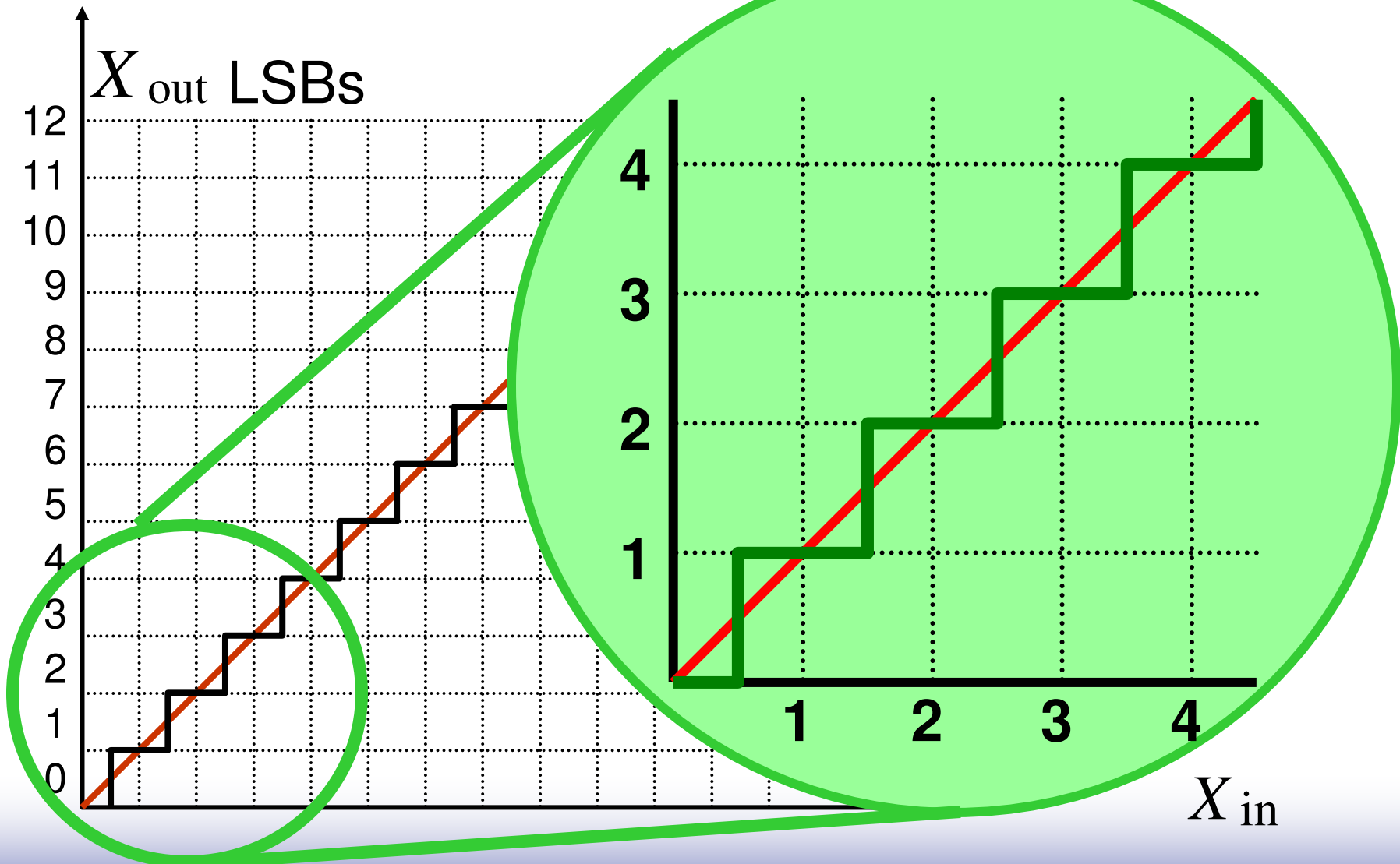

 
# Quantization – Noise Model

- Quantization error is sawtooth-like.
- Uniform distribute between  $(-q/2, q/2)$  ( $q=LSB$ ).


 
# Quantization – Noise Model

- The error contains a lot of jumps.
- Error spectral is much wider than the original signal.
- The bandwidth of the quantization is proportional to the slope of the signal and inversely proportional to the quantum size  $q$ .




# Quantization - Noise Model

- A sine wave is quantized by a B-bit ADC. How large is the SNR.

$$2V_p = 2^n q$$

$$P_S = \frac{V_p^2}{2}$$
 
$$P_N = \left( \frac{q/2}{\sqrt{3}} \right)^2 = \frac{q^2}{12}$$



# Quantization - Noise Model

$$SNR = 10 \log \frac{P_s}{P_N} = 10 \log \left( \frac{\frac{V_p^2}{2}}{\frac{q^2}{12}} \right) = 10 \log(6 \cdot 4^{n-1})$$


$$\underline{SNR = (1.76 + 6n)dB}$$

$$\text{For } n=10, \quad SNR = 61.8dB$$

## ***11.3 Mixed-Signal Testing***


- Introduction to Analog-Digital Conversion
- **ADC and DAC Circuit Structure**
- ADC/DAC Specification and Fault Models
- IEEE Std. 1057
- Time-Domain ADC Testing
- Frequency-Domain ADC Testing

# ADC Architecture - Gain Stage

 

- ❑ **Gain:** Provide offset and full scale conversion
- ❑ **Filter:** Reject off-band noise (anti-aliasing filter)
- ❑ **MUX:** Provide multiple channel access
- ❑ **S/H:** Provide steady signal for A-to-D conversion
- ❑ **ADC:** Actual analog to digital conversion


# ADC Architecture - Gain Stage

 

- ❑ Function: Provides gain and offset
- ❑ Achieve the maximal A/D resolution by scaling the input signal to match the full A/D input range.
- ❑ Drawbacks:
  - Introduces noise, nonlinearity, drift
  - Expense of tight-tolerance
  - Require calibration




# ADC Architecture - Filter Stage

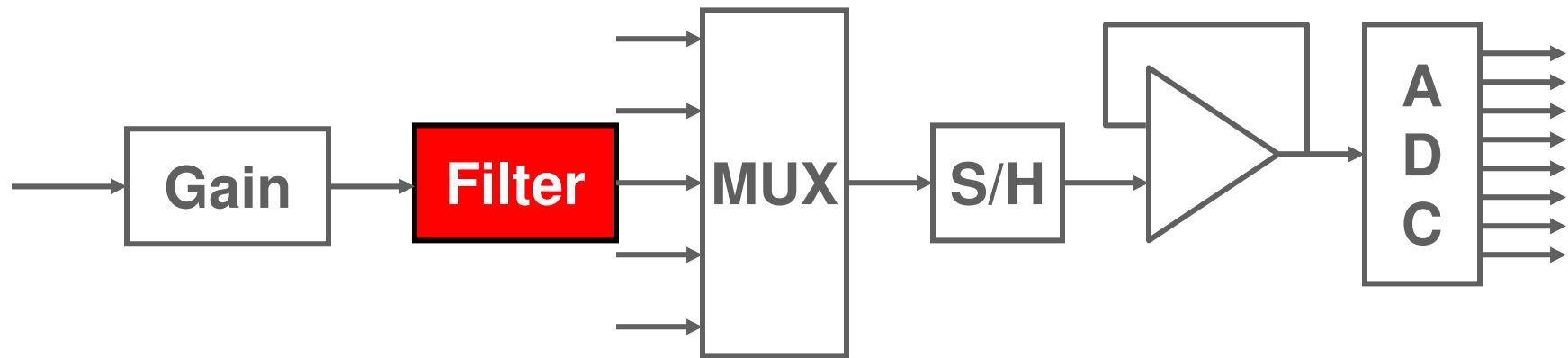


- ❑ Function: Attenuate the out-of-band noise to prevent aliasing
- ❑ Filter Position
  - Before the MUX (1 per channel) : maximize speed in switching channels.
  - After the MUX: minimize mismatching among channels.

# ADC Architecture - Filter Stage

## □ Anti-Aliasing Filter

 


# ADC Architecture - MUX Stage

 

- ❑ Function: Provides multiple access
- ❑ Crosstalk:
  - The most severe problem
  - Frequency dependent
  - Can be minimized by placing amplifier before the MUX.
- ❑ Load Issues
  - Avoid too many fanins.
  - Use hierarchical structure.

# ADC Architecture - S/H Stage

 


## □ Function:

- Provides steady signal
- Provides signal synchronization,


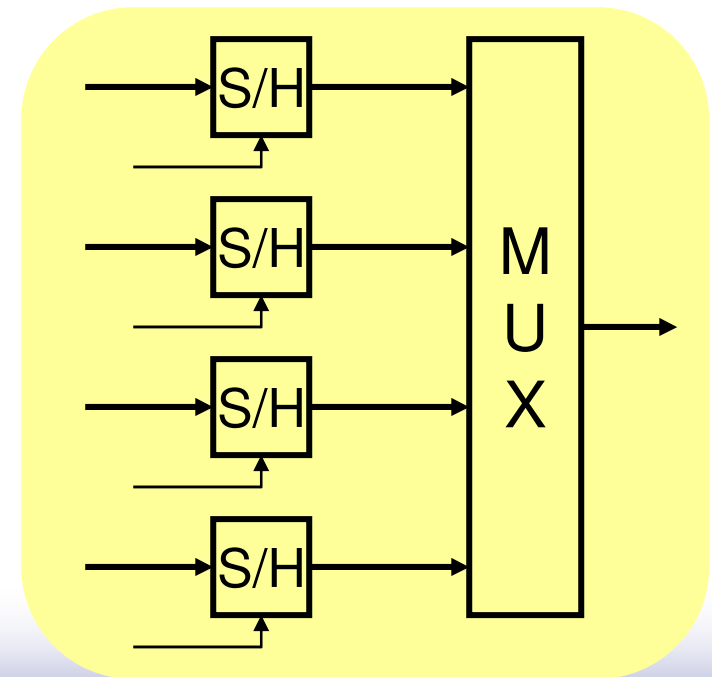
## □ S/H position:

- After the MUX for cost reason
- Before MUX for synchronization and crosstalk reduction.



 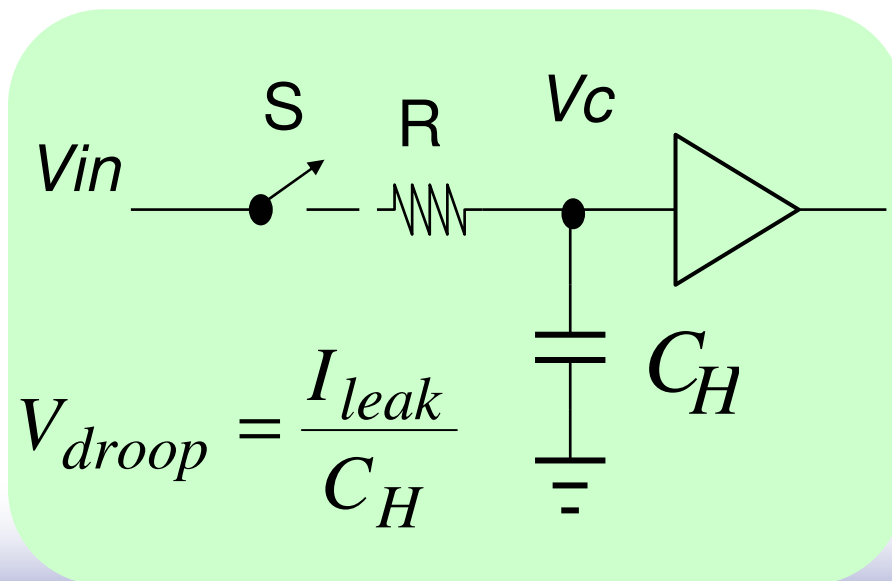
# ADC Architecture - S/H Check List

- ❑ **Aperture Time:** The time aperture ( $t_3$ )
- ❑ **Acquisition Time:** The total time for the S/H to acquire a full-scale step input signal. ( $t_3 - t_1$ )
- ❑ **Aperture Jitter:** The uncertainty of aperture time due to noise or jitter in clock. ( $t_4 - t_2$ )



# ADC Architecture - ADC Stage

 


□ Executes analog to digital conversion

□ Check List:


- Bit length
- Accuracy
- Conversion Rate
- System Error Budget
- Input Signal Range
- Total System Cost Target
- Input Impedance
- AC or DC Inputs BW

# DAC Example - R-2R Ladder

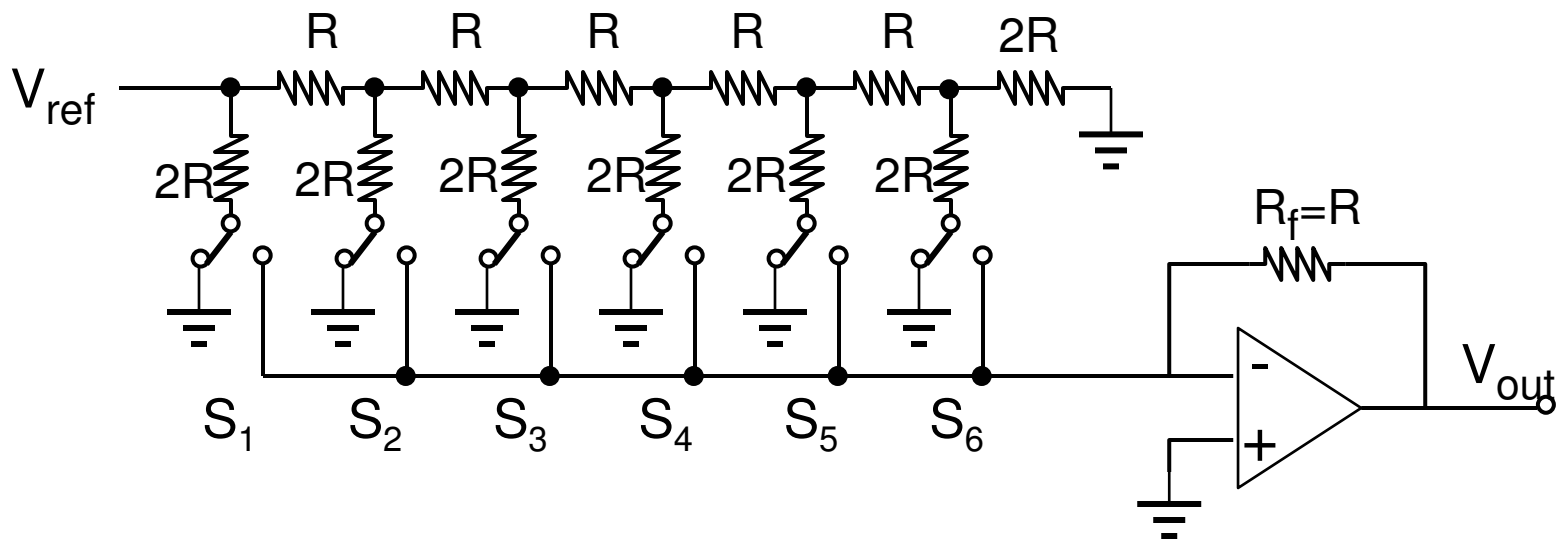

$$V_o = S_5 \cdot \frac{V_{ref}}{2^1} + S_4 \cdot \frac{V_{ref}}{2^2} + S_3 \cdot \frac{V_{ref}}{2^3} + S_2 \cdot \frac{V_{ref}}{2^4} + S_1 \cdot \frac{V_{ref}}{2^5} + S_0 \cdot \frac{V_{ref}}{2^6}$$
$$= (S_5 \cdot 2^5 + S_4 \cdot 2^4 + S_3 \cdot 2^3 + S_2 \cdot 2^2 + S_1 \cdot 2^1 + S_0 \cdot 2^0) \cdot \frac{V_{ref}}{2^6}$$

# ADC Example – Pipelined ADC

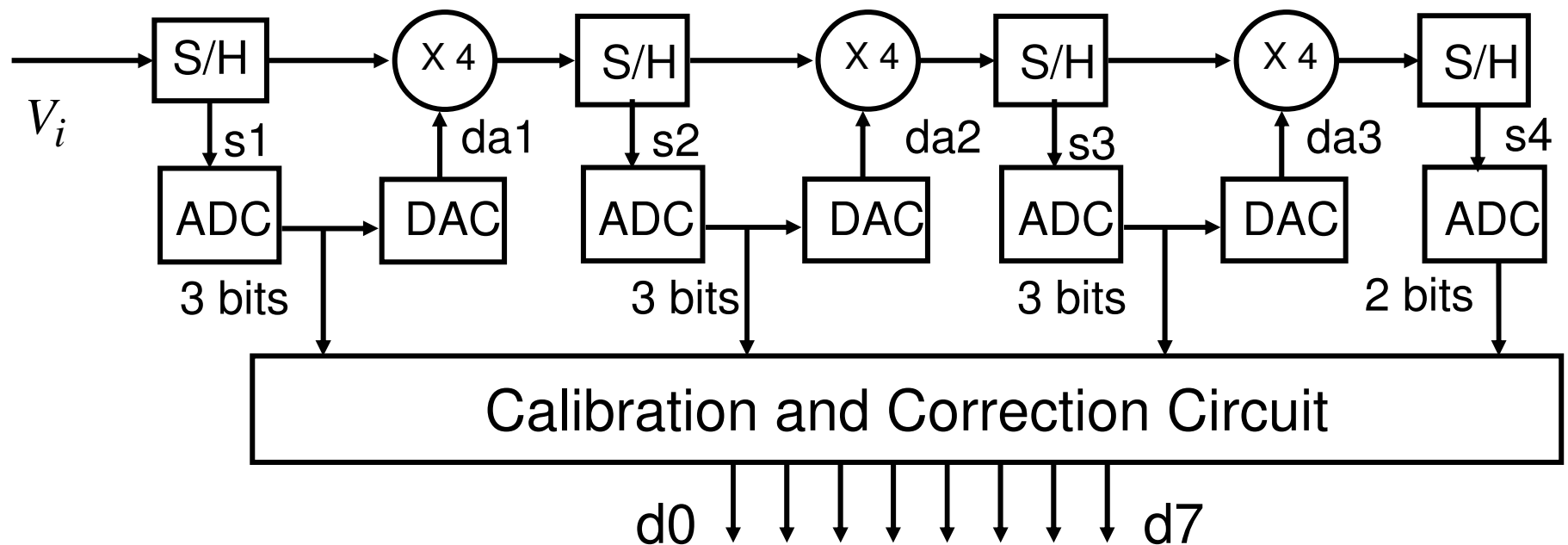



# ADC – Bits v.s. Throughput

| ADC         | Bit-Length  | Throughput   |
|-------------|-------------|--------------|
| Flash       | ~ 6 bits    | 100 M ~      |
| Pipelined   | 8 ~ 16 bits | 10 ~ 100 MHz |
| Sigma-Delta | 14 ~ bits   | ~ 10 M       |

# ADC – Selection Matrix

|       |         |                      |                     |                    |                  |              |
|-------|---------|----------------------|---------------------|--------------------|------------------|--------------|
| 17+   | ●       | ●                    | ●                   | ●                  |                  |              |
| 14-16 | ●       | ●                    | ●                   | ●                  |                  |              |
| 12-13 |         | ●                    | ●                   | ●                  | ●                | ●            |
| 10-11 |         | ●                    | ●                   | ●                  | ●                | ●            |
| 8-9   |         |                      | ●                   | ●                  | ●                | ●            |
| <8    |         |                      |                     |                    | ●                |              |
| Bits  | <10kbps | 10Kbps to<br>100Kbps | 100Kbps<br>to 1Mbps | 1Mbps to<br>10Mbps | 10 to<br>100Mbps | 100Mbps<br>+ |

*From Analog Devices Inc.*

# ADC – Example AD775

## AD775–SPECIFICATIONS ( $T_A = +25^\circ\text{C}$ with $AV_{DD}, DV_{DD} = +5\text{ V}$ , $AV_{SS}, DV_{SS} = 0\text{ V}$ , $V_{RT} = 2.6\text{ V}$ , $V_{RB} = +0.6\text{ V}$ , CLOCK = 20 MHz unless otherwise noted)

| Parameter                                       | Min   | AD775J<br>Typ | Max       | Units            |
|---|-------|---------------|-----------|------------------|
| RESOLUTION                                      | 8     |               |           | Bits             |
| DC ACCURACY                                     |       |               |           |                  |
| Integral Nonlinearity (INL)                     |       | +0.5          | 1.3       | LSB              |
| Differential Nonlinearity (DNL)                 |       | $\pm 0.3$     | $\pm 0.5$ | LSB              |
| No Missing Codes                                |       | GUARANTEED    |           |                  |
| Offset  |       |               |           |                  |
| To Top of Ladder $V_{RT}$                       | -10   | -35           | -60       | mV               |
| To Bottom of Ladder $V_{RB}$                    | 0     | +15           | +45       | mV               |
| VIDEO ACCURACY <sup>1</sup>                     |       |               |           |                  |
| Differential Gain Error                         |       | 1.0           |           | %                |
| Differential Phase Error                        |       | 0.5           |           | Degrees          |
| ANALOG INPUT                                    |       |               |           |                  |
| Input Range ( $V_{RT}-V_{RB}$ )                 |       | 2.0           |           | V p-p            |
| Input Capacitance                               |       | 11            |           | pF               |
| AC SPECIFICATIONS <sup>2</sup>                  |       |               |           |                  |
| Signal-to-Noise and Distortion (S/(N + D))      |       |               |           |                  |
| $f_{IN} = 1\text{ MHz}$                         |       | 47            |           | dB               |
| $f_{IN} = 5\text{ MHz}$                         |       | 41            |           | dB               |
| Total Harmonic Distortion (THD)                 |       |               |           |                  |
| $f_{IN} = 1\text{ MHz}$                         |       | -51           |           | dB               |
| $f_{IN} = 5\text{ MHz}$                         |       | -42           |           | dB               |
| REFERENCE INPUT                                 |       |               |           |                  |
| Reference Input Resistance ( $R_{REF}$ )        | 230   | 300           | 450       | $\Omega$         |
| Case 1: $V_{RT} = V_{RTS}$ , $V_{RB} = V_{RBS}$ |       |               |           |                  |
| Reference Bottom Voltage ( $V_{RB}$ )           | 0.60  | 0.64          | 0.68      | V                |
| Reference Span ( $V_{RT}-V_{RB}$ )              | 1.96  | 2.09          | 2.21      | V                |
| Reference Ladder Current ( $I_{REF}$ )          | 4.4   | 7.0           | 9.6       | mA               |
| Case 2: $V_{RT} = V_{RTS}$ , $V_{RB} = AV_{SS}$ |       |               |           |                  |
| Reference Span ( $V_{RT}-V_{RB}$ )              | 2.25  | 2.39          | 2.53      | V                |
| Reference Ladder Current ( $I_{REF}$ )          | 5     | 8             | 11        | mA               |
| POWER SUPPLIES                                  |       |               |           |                  |
| Operating Voltages                              |       |               |           |                  |
| $AV_{DD}$                                       | +4.75 |               | +5.25     | Volts            |
| $DV_{DD}$                                       | +4.75 |               | +5.25     | Volts            |
| Operating Current                               |       |               |           |                  |
| $I_{AV_{DD}}$                                   |       | 9.5           |           | mA               |
| $I_{DV_{DD}}$                                   |       | 2.5           |           | mA               |
| $I_{AV_{DD}} + I_{DV_{DD}}$                     |       | 12            | 17        | mA               |
| POWER CONSUMPTION                               |       | 60            | 85        | mW               |
| TEMPERATURE RANGE                               |       |               |           |                  |
| Operating                                       | -20   |               | +75       | $^\circ\text{C}$ |

### NOTES

<sup>1</sup>NISTC 40 IRE modulation ramp, CLOCK = 14.3 MSPS.

<sup>2</sup> $f_{IN}$  amplitude = 0.3 dB full scale.


Specifications subject to change without notice. See Definition of Specifications for additional information.

## ***11.3 Mixed-Signal Testing***

- Introduction to Analog-Digital Conversion
- ADC and DAC Circuit Structure
- **ADC/DAC Specification and Fault Models**
- IEEE Std. 1057
- Time-Domain ADC Testing
- Frequency-Domain ADC Testing

 
# ADC – Offset Error

- **Offset:** constant component of the error that is independent of the inputs



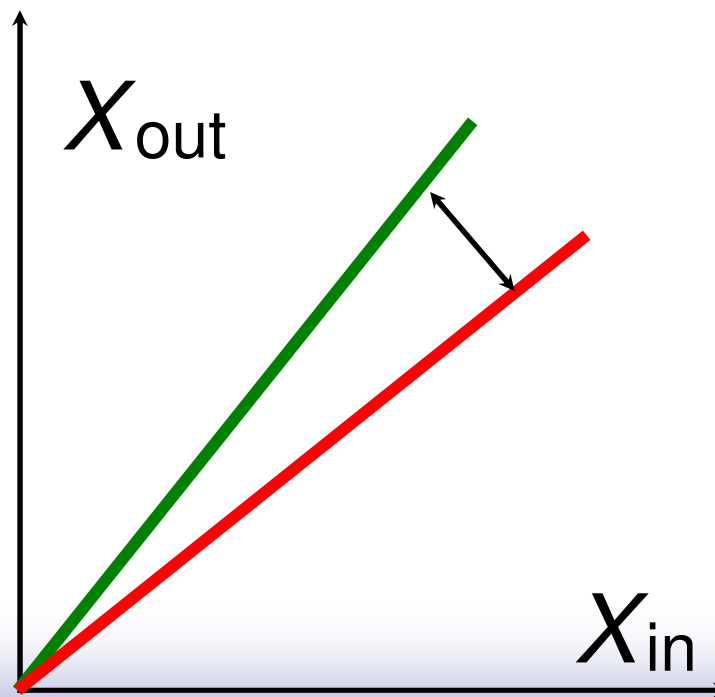
# ADC – Gain Error

- **Gain Error:** difference between the actual transfer ratio and the ideal ratio
- Also called Calibration Error



 
# ADC – Nonlinearity Error

- **Nonlinearity error:** The deviation of the output quantity from a specified linear reference


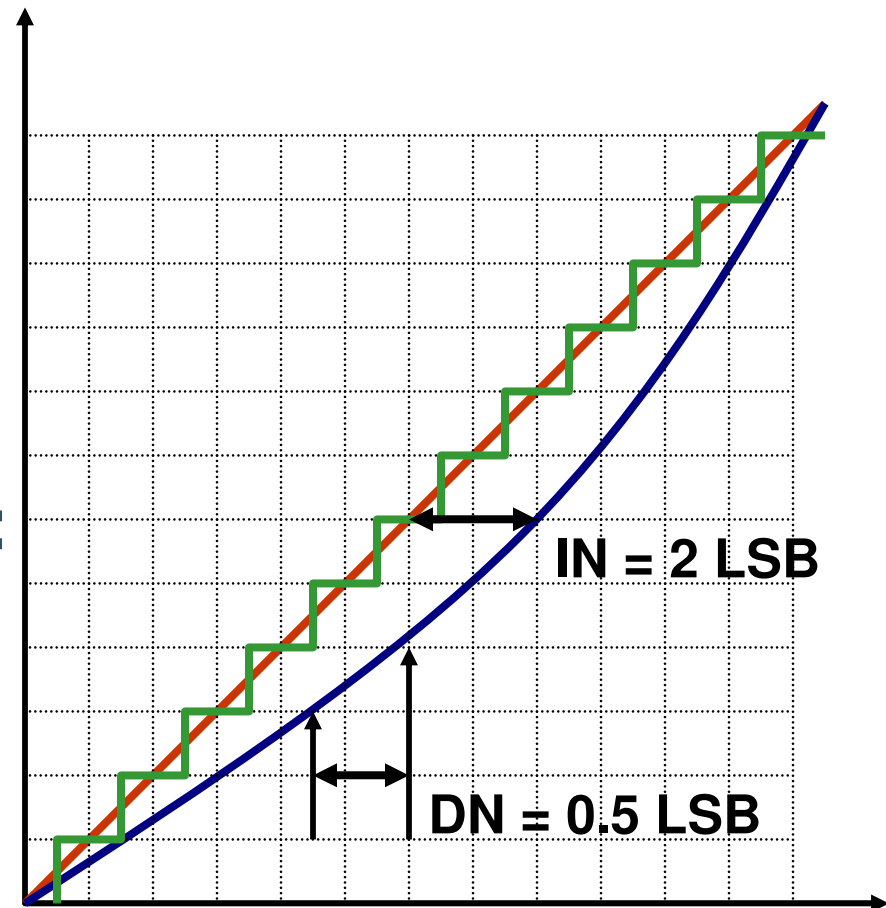
# ADC – Nonlinearity Error


- **Integral Nonlinearity:**  
Worst-case deviation from the ideal transfer characteristic curve
- **Differential Nonlinearity:**  
Difference between the actual transfer ratio and the ideal ratio





 
## *ADC – Temperature-Dependent Error*

- **Temperature-Dependent Error:** Due to the change in ambient temperature or temperature variation due to self-heating (temperature stability, temperature coefficient)



 
# ADC – Load-Dependent Error

- **Load Error:** Loading error is due to the effect of a load impedance upon the converter or signal source driving it.



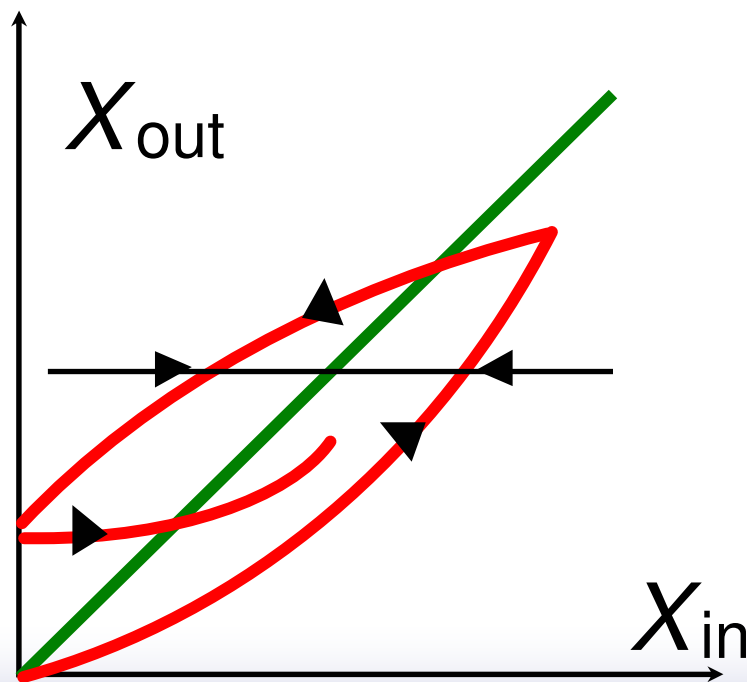
# ADC – Hysteresis Error

- **Hysteresis Error:** The difference between the increasing and decreasing input values that produce the same output



 
# ADC – Resolution Error

- **Resolution Error:** The error due to the inability to respond to change of a variable smaller than a given increment




# ADC – Missing Code Error

*Ideal Input Waveform*

 

*Quantized with missing Code*

 

*Quantization Error*



## ***11.3 Mixed-Signal Testing***

- Introduction to Analog-Digital Conversion
- ADC and DAC Circuit Structure
- ADC/DAC Specification and Fault Models
- **IEEE Std. 1057**
- Time-Domain ADC Testing
- Frequency-Domain ADC Testing

# *IEEE 1057 Standard*

## □ Scope

- Covers electronic digitizing waveform recorders, waveform analyzers and digitizing oscilloscopes with digital outputs.
- Applies to, but is not restricted to, general-purpose waveform recorders and analyzers.

# *IEEE 1057 Standard*

## □ Purpose

- Provides common methods for testing and terminology for describing the performance of waveform recorders.
- Benefits users and manufacturers of such devices.
- Presents many performance features, sources of error, and test methods.



# ***IEEE 1057*** – General Information

|  |
|--|
| Model Number   |
| Dimensions and weight                                    |
| Power Requirement  |
| Environmental conditions (tem., humidity, EMC/EMI, etc.) |
| Any special or peculiar characteristics                  |
| Available options and accessories                        |
| Exception to the above parameters where applicable       |
| Calibration interval                                     |

# ***IEEE 1057*** – Minimum Specification

|                           |                     |
|---------------------------|---------------------|
| Number of digitizing bits | Input impedance     |
| Sample rates              | Analog bandwidth    |
| Memory length             | Input signal ranges |

# IEEE 1057 – Additional Specifications

|                                  |                                      |
|----------------------------------|--------------------------------------|
| Gain                             | Fixed error in sample time           |
| Offset                           | Trigger delay and jitter             |
| Differential nonlinearity        | Trigger sensitivity                  |
| Integral nonlinearity            | Trigger minimum rate of change       |
| Harmonic distortion              | Trigger hysteresis band              |
| Spurious response                | Trigger coupling to signal           |
| Maximal static error             | Crosstalk                            |
| Signal to noise ratio            | Monotonicity                         |
| Effective bits                   | Hysteresis                           |
| Peak error                       | Over voltage recovery                |
| Random noise                     | Word error rate                      |
| Frequency response               | Cycle time                           |
| Settling time                    | Common mode rejection ratio          |
| Slew limit                       | Differential input impedance         |
| Overshoot and precursors         | Maximum operating common             |
| Aperture uncertainty             | mode signal level                    |
| Long-term stability              | Transition duration of step response |
| Maximum common mode signal level |                                      |


# IEEE 1057 – Test Methods

|  |                                  |
|--|----------------------------------|
| General methods  | Triggering                       |
| Input impedance  | Crosstalk                        |
| Gain and offset  | Monotonicity                     |
| Noise  | Hysteresis                       |
| Analog bandwidth                                       | Overvoltage Recovery             |
| Frequency response                                     | Word Error Rate                  |
| Step Response parameters                               | Cycle Time                       |
| Time base errors                                       | Differential Input Specification |
| Linearity, harmonic distortion, and spurious responses |                                  |

## ***11.3 Mixed-Signal Testing***

- Introduction to Analog-Digital Conversion
- ADC and DAC Circuit Structure
- ADC/DAC Specification and Fault Models
- IEEE Std. 1057
- **Time-Domain ADC Testing**
- Frequency-Domain ADC Testing


# Histogram – Code Bins

 

# Test Methods - Code Transition Level
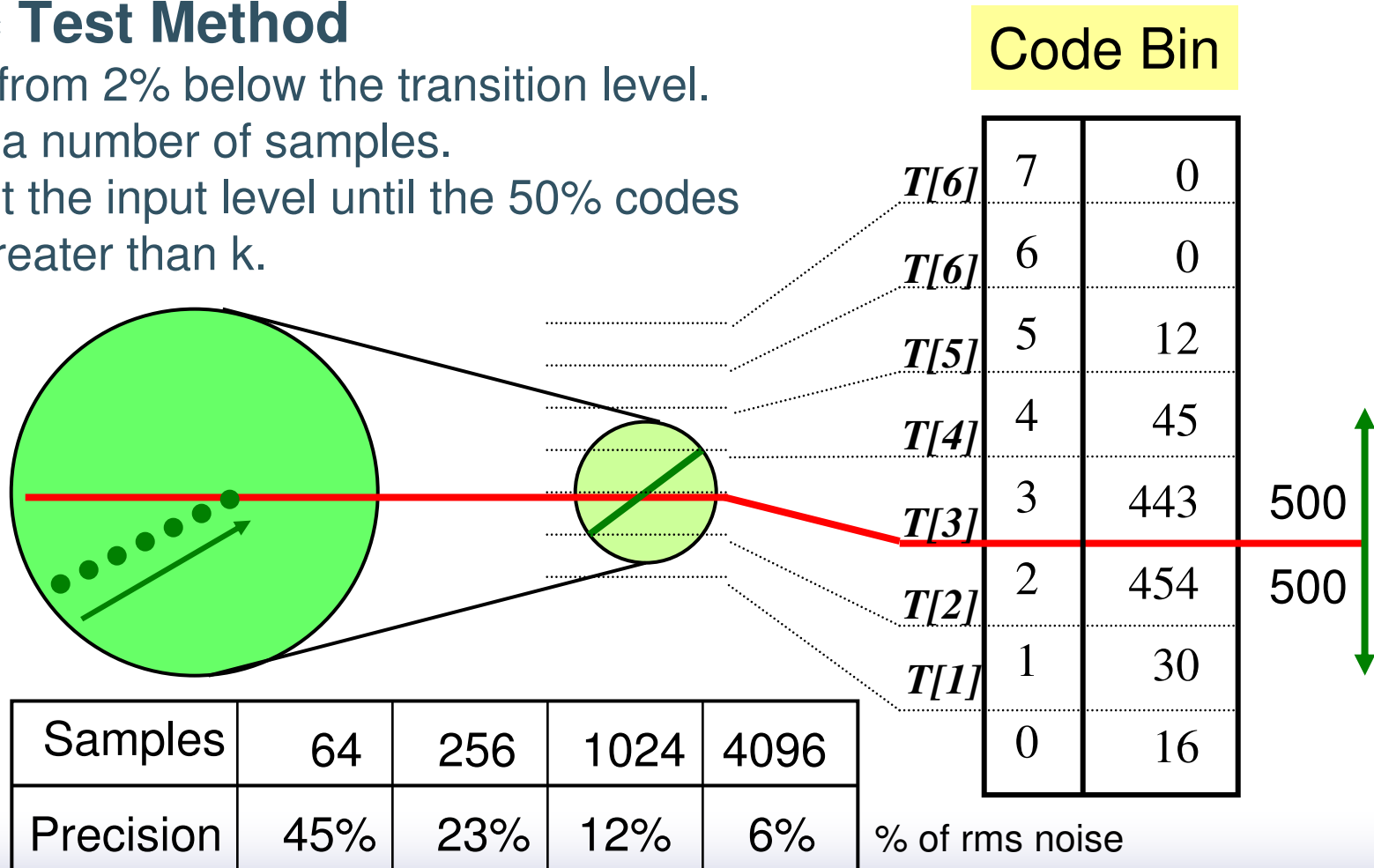
## Static Test Method


- Start from 2% below the transition level.
- Take a number of samples.
- Adjust the input level until the 50% codes are greater than k.



# Test Methods - Code Transition Level
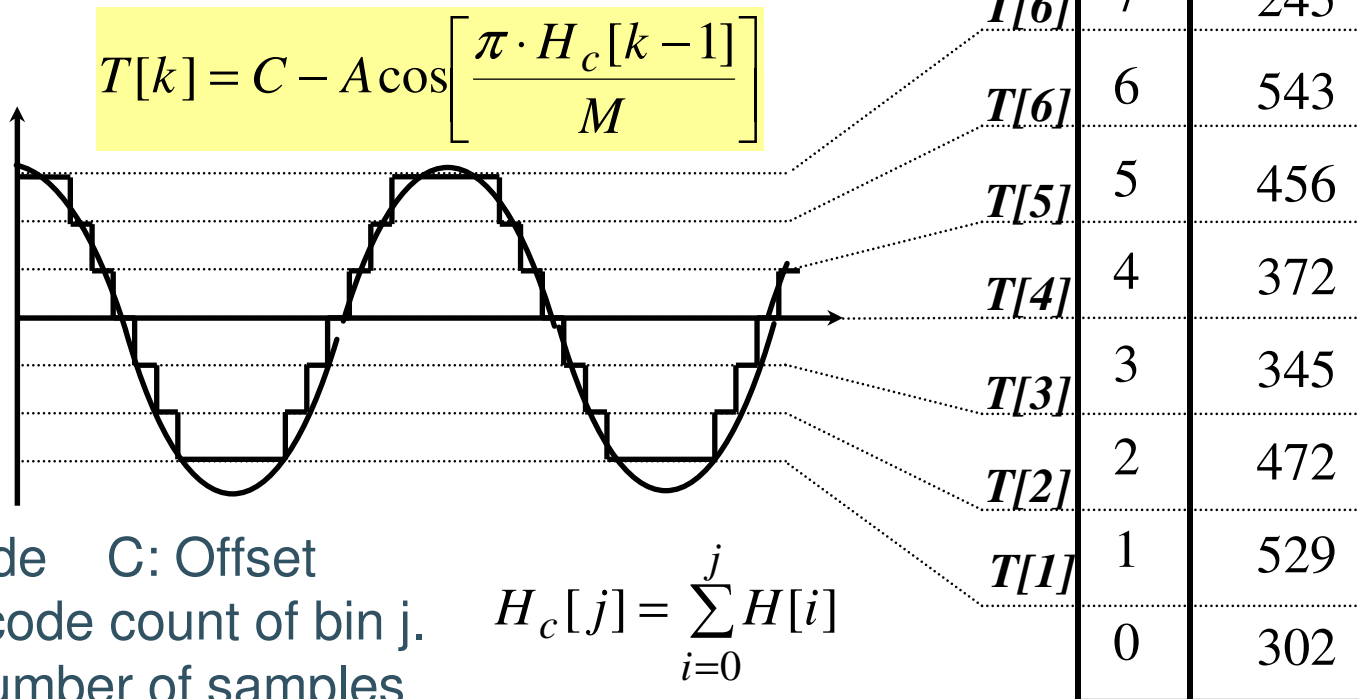
## Dynamic Test Method

- Apply full range sine wave
- Calculate the transition level from the bin count



- A: Amplitude    C: Offset
- $H[j]$ : The code count of bin j.
- M: Total number of samples
- Record Length M and Number of Cycles  $M_c$  must not have common term.

$$H_c[j] = \sum_{i=0}^j H[i]$$




# Test Methods - Gain and Offset

- Apply a slow ramp signal
- Construct the code bin table

Q: ideal width of the code bin
 
$$G \cdot T[k] + V_{os} + \varepsilon[k] = Q \cdot (k - 1) + T_1$$







$$V_{os} = T_1 + Q(2^N - 1) - \frac{G}{2^N - 1} \sum_{k=1}^{2^N - 1} T[k]$$





$$G = Q \frac{(2^N - 1) \sum_{k=1}^{2^N - 1} kT[k]}{(2^N - 1) \sum_{k=1}^{2^N - 1} T^2[k] - \left( \sum_{k=1}^{2^N - 1} T[k] \right)^2} - Q \frac{(2^N - 1)(2^N - 1) \sum_{k=1}^{2^N - 1} T[k]}{(2^N - 1) \sum_{k=1}^{2^N - 1} T^2[k] - \left( \sum_{k=1}^{2^N - 1} T[k] \right)^2}$$

# Test Methods - Gain and Offset (Example)

## Transfer Curves

    

## Histograms

    

Ideal

Gain Error

Offset Error


Gain/Offset

# Test Methods - Nonlinearity

Differential Nonlinearity

$$DNL[k] = \frac{G \cdot W[k] - Q}{Q}$$

$$DNL = \max \left| \frac{G \cdot W[k] - Q}{Q} \right|$$

 

Integral Nonlinearity


$$INL = 100 \frac{\max |\epsilon[k]|}{Q 2^N}$$

Maximal Static Error

$$MSE = 100 \frac{\max |T[k] - Q(k-1) - T_1|}{Q 2^N}$$
 
# Test Methods - Sine Wave Fitting

- Try to fit the sine wave to find the gain  $A'$ , offset  $C_0$ , and phase shift  $\theta$ .
- There are matrix based and nonmatrix methods.



$$y_i = A \sin \omega_o t_i + C_o$$



$$y'_i = A' \sin(\omega t_i + \theta) + C$$



$$y'_i = A \sin(\omega t_i) + B \cos(\omega t_i) + C$$



$$\text{Min} \left[ \sum_{i=1}^m (y_i - A \cos(\omega t_i) - B \cos(\omega t_i) - C)^2 \right]$$

# Test Methods - Sine Wave Fitting

**Original Signal:**  $y(t) = A_o \sin(\omega_o t) + C_o$

**Curve Fitted:**  $y'(t) = A \sin(\omega t) + B \cos(\omega t) + C$

**Gain Error:** 
$$\frac{\sqrt{A^2 + B^2} - A_o}{A_o}$$

**Offset Error:**  $C - C_o$

**Phase Error:** 
$$\theta = \tan^{-1}\left(-\frac{B}{A}\right)$$


**Frequency Error:** 
$$\frac{(\omega - \omega_o)}{\omega_o}$$

## ***11.3 Mixed-Signal Testing***

- Introduction to Analog-Digital Conversion
- ADC and DAC Circuit Structure
- ADC/DAC Specification and Fault Models
- IEEE Std. 1057
- Time-Domain ADC Testing
- **Frequency-Domain ADC Testing**
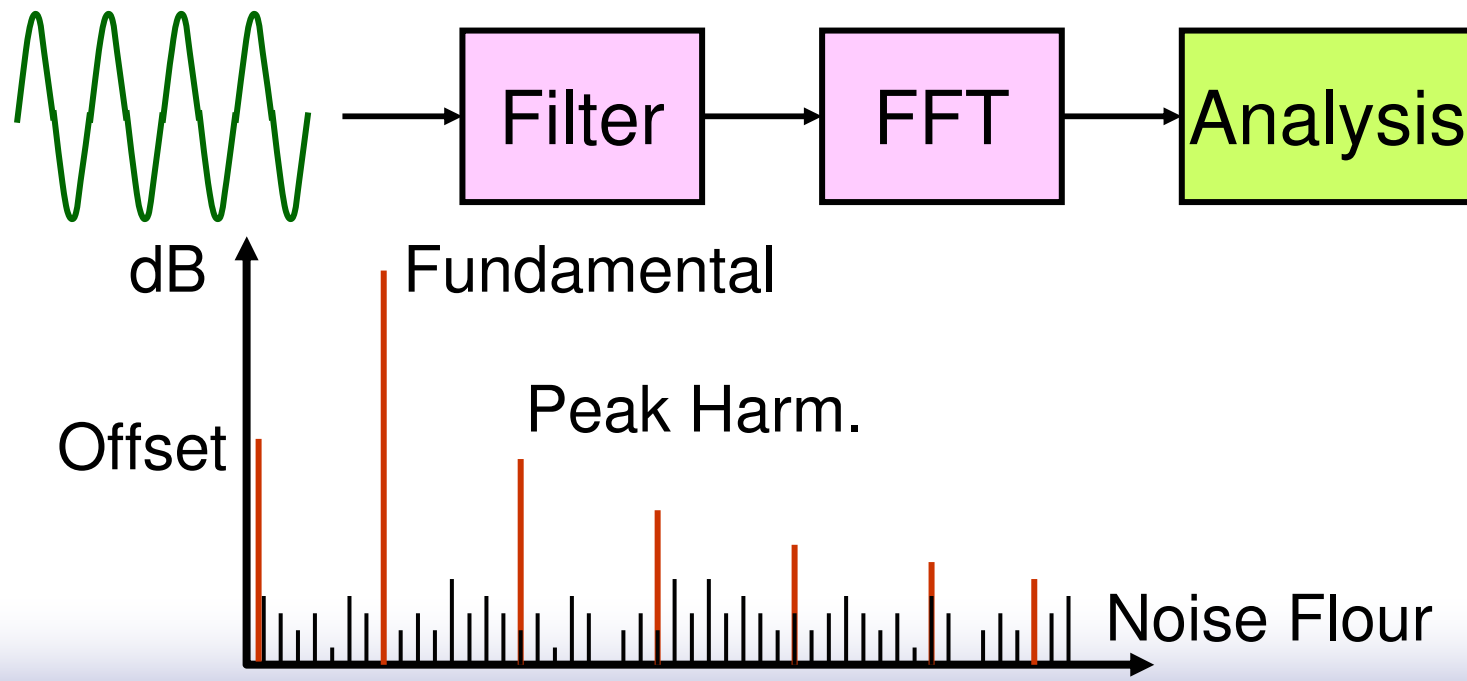
# ADC – Frequency Domain Testing

- Similar to Analog AC Testing
- Apply sinusoidal waveform
- Do Fourier transform on response waveform
- Obtain F domain properties mathematically.




# ADC – Frequency Domain Testing

$$THD = 10 \log \frac{F^2}{\sum H_i^2} = 100 \times \frac{F^2}{\sum H_i^2} \%$$

$$SNR = 10 \log \frac{F^2}{\sum N_i^2}$$
 
$$SNDR = 10 \log \frac{F^2}{\sum H_i^2 + \sum N_i^2}$$





# ***11.4 IEEE Std. 1149.4 Standard for a Mixed-Signal Test Bus***

- **IEEE Std. 1149.4 Overview**
- IEEE Std. 1149.4 Circuit Structures
- IEEE Std. 1149.4 Instructions
- IEEE Std. 1149.4 Test Modes


# IEEE 1149.4 - Overview

□ Target mixed signal Printed Circuit Assemblies (**PCA**).

□ Components:

- Mixed Signal
- Digital
- Analog
- Discrete

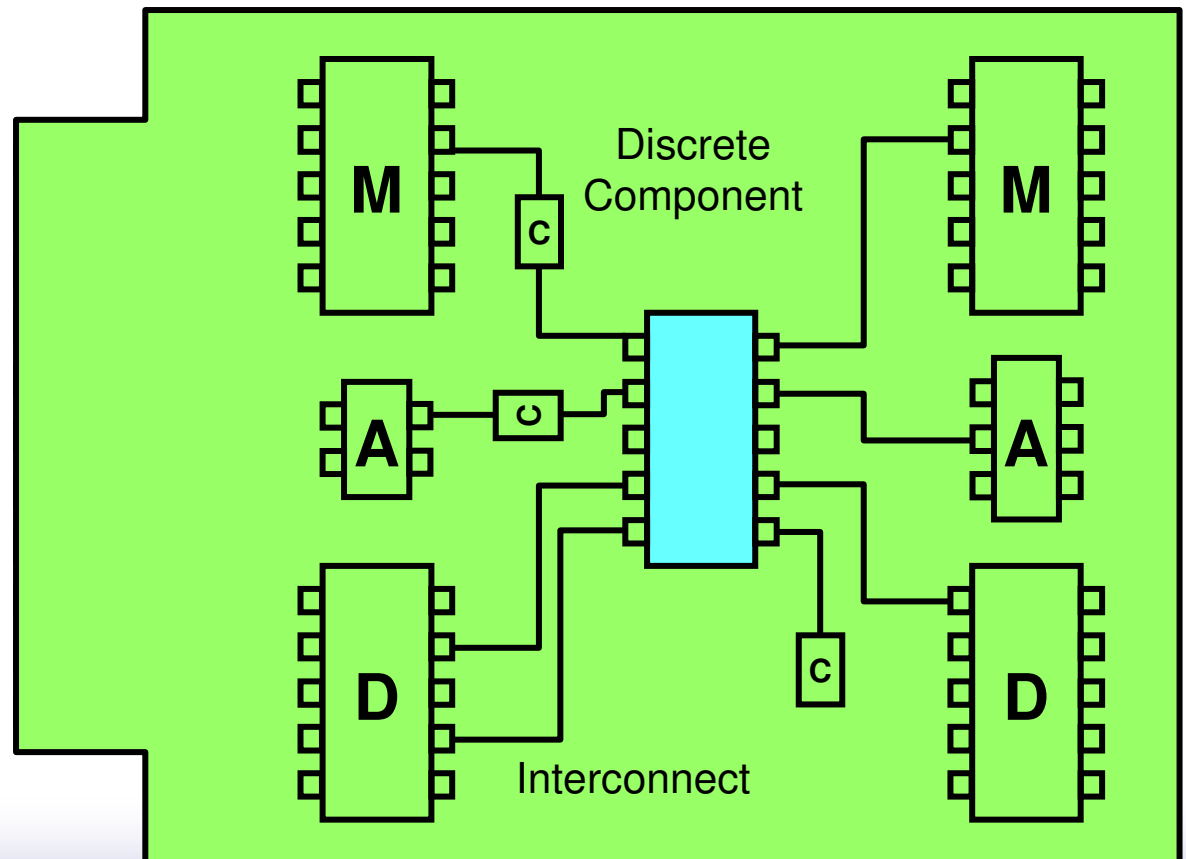
M: Mixed-signal Component  
A: Analog Component  
D: Digital Component




## ***IEEE 1149.4 - Scope***

- Provide standardized approaches to
  - ***Interconnect Test***
  - ***Parametric Test***
  - ***Internal Test***

# IEEE 1149.4 - Interconnect Test

 


**Open Defects**

 

**Short Defects**


# IEEE 1149.4 - Parametric Test

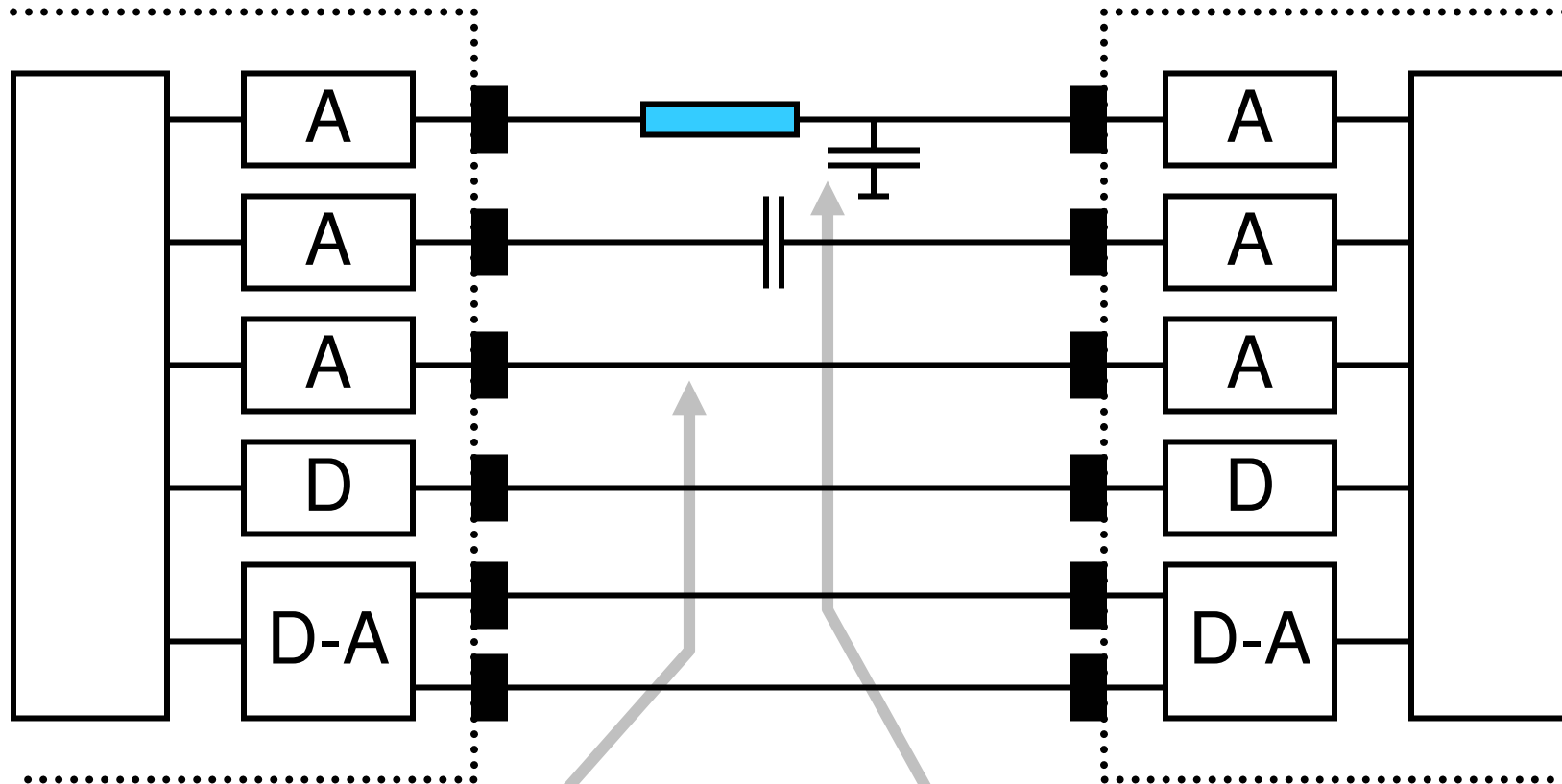


Simple Interconnect

Extended Interconnect

# IEEE 1149.4 - Internal Test

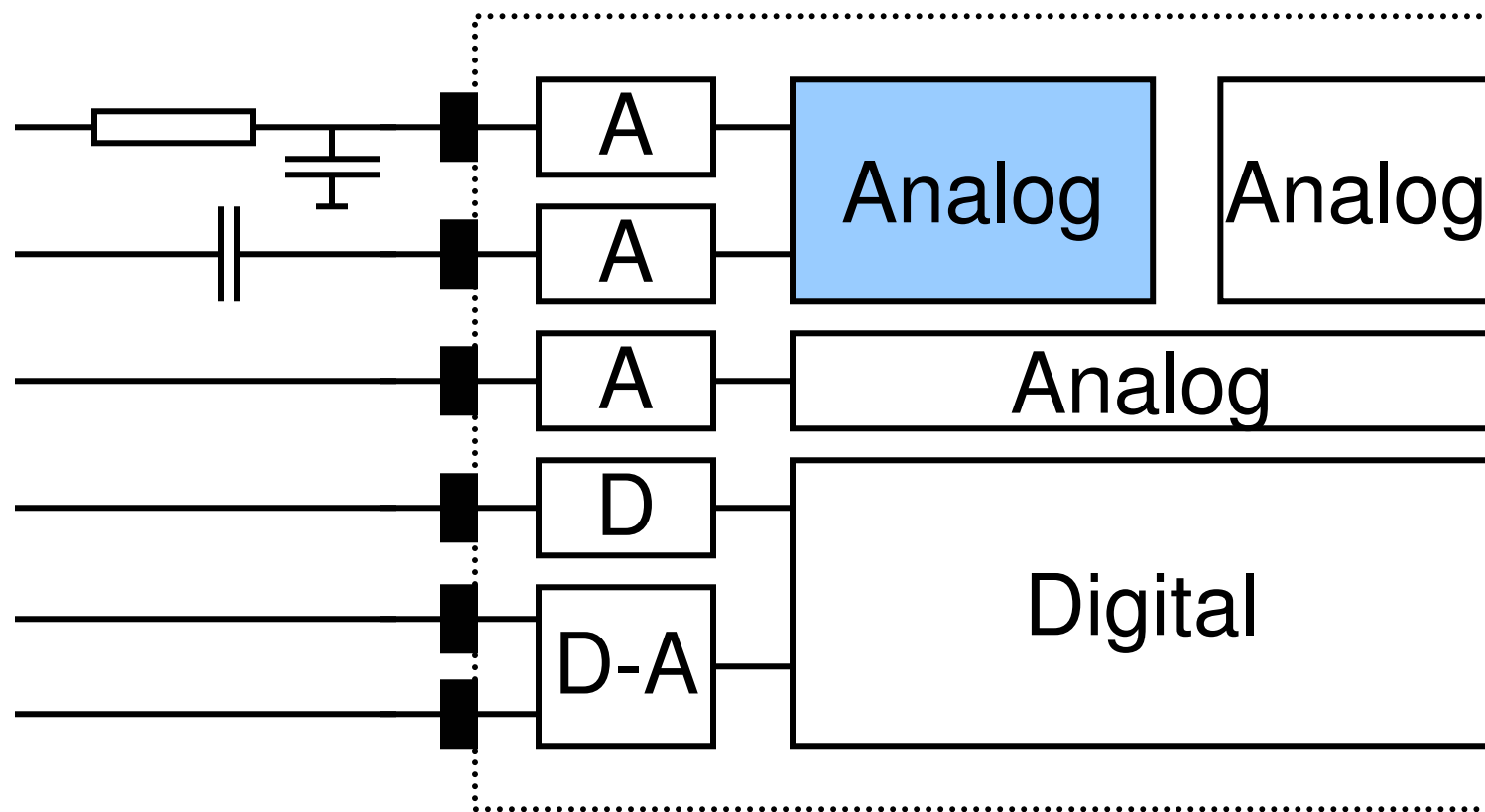

# IEEE 1149.4 - Architecture

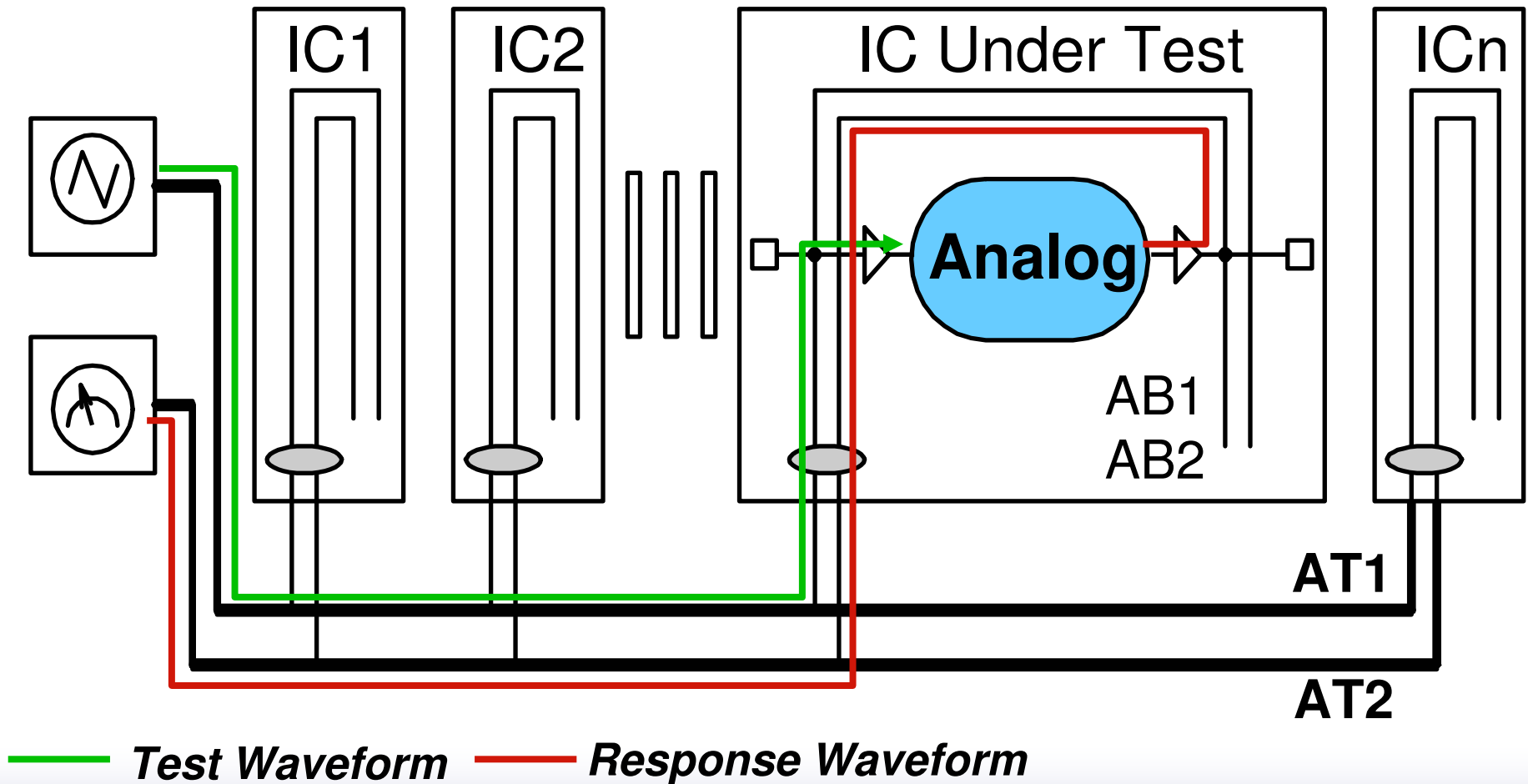


## ***11.4 IEEE Std. 1149.4 Standard for a Mixed-Signal Test Bus***


- IEEE Std. 1149.4 Overview
- **IEEE Std. 1149.4 Circuit Structures**
- IEEE Std. 1149.4 Instructions
- IEEE Std. 1149.4 Test Modes





# IEEE 1149.4 - Architecture

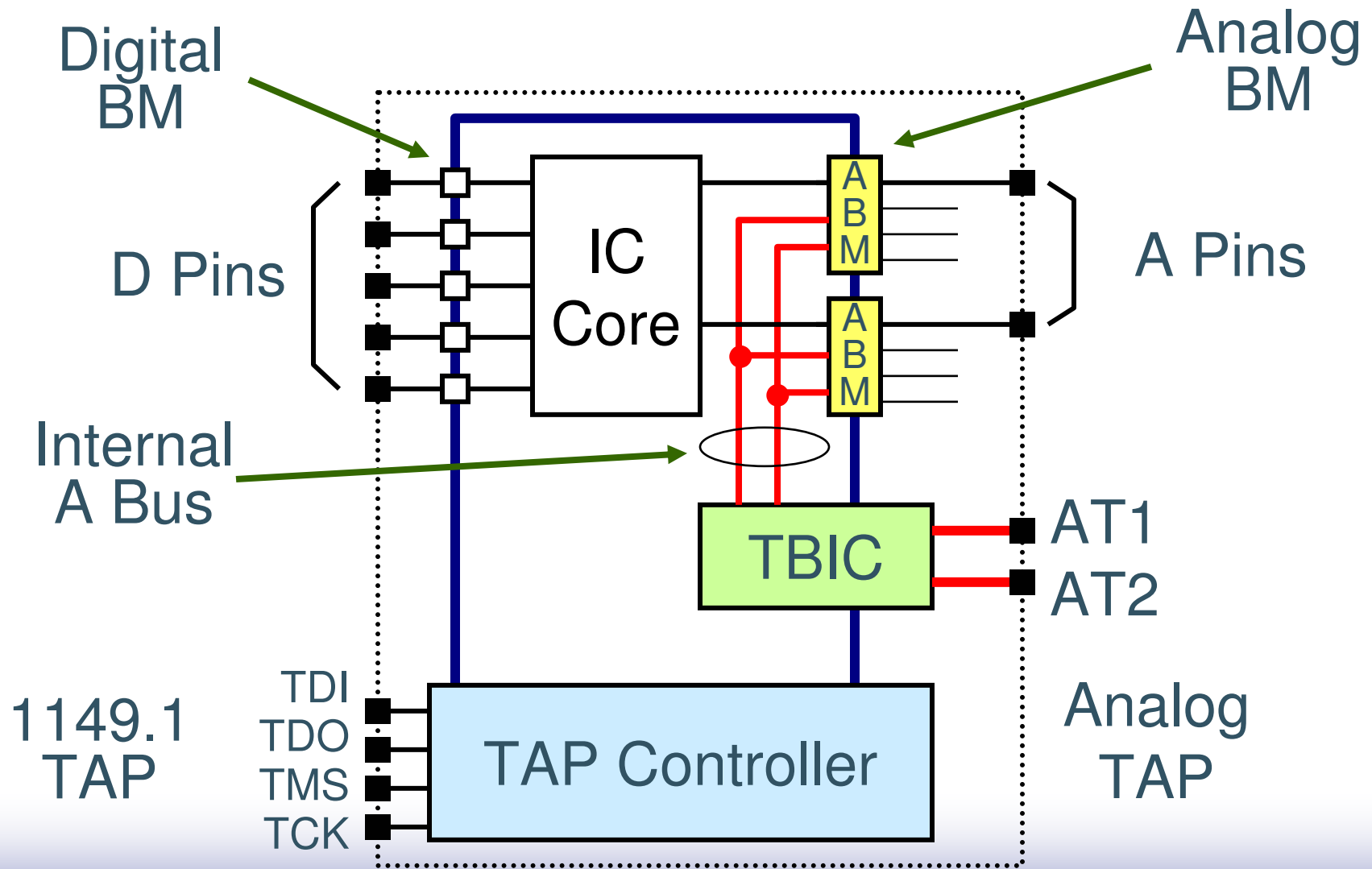


# IEEE 1149.4 - TBIC

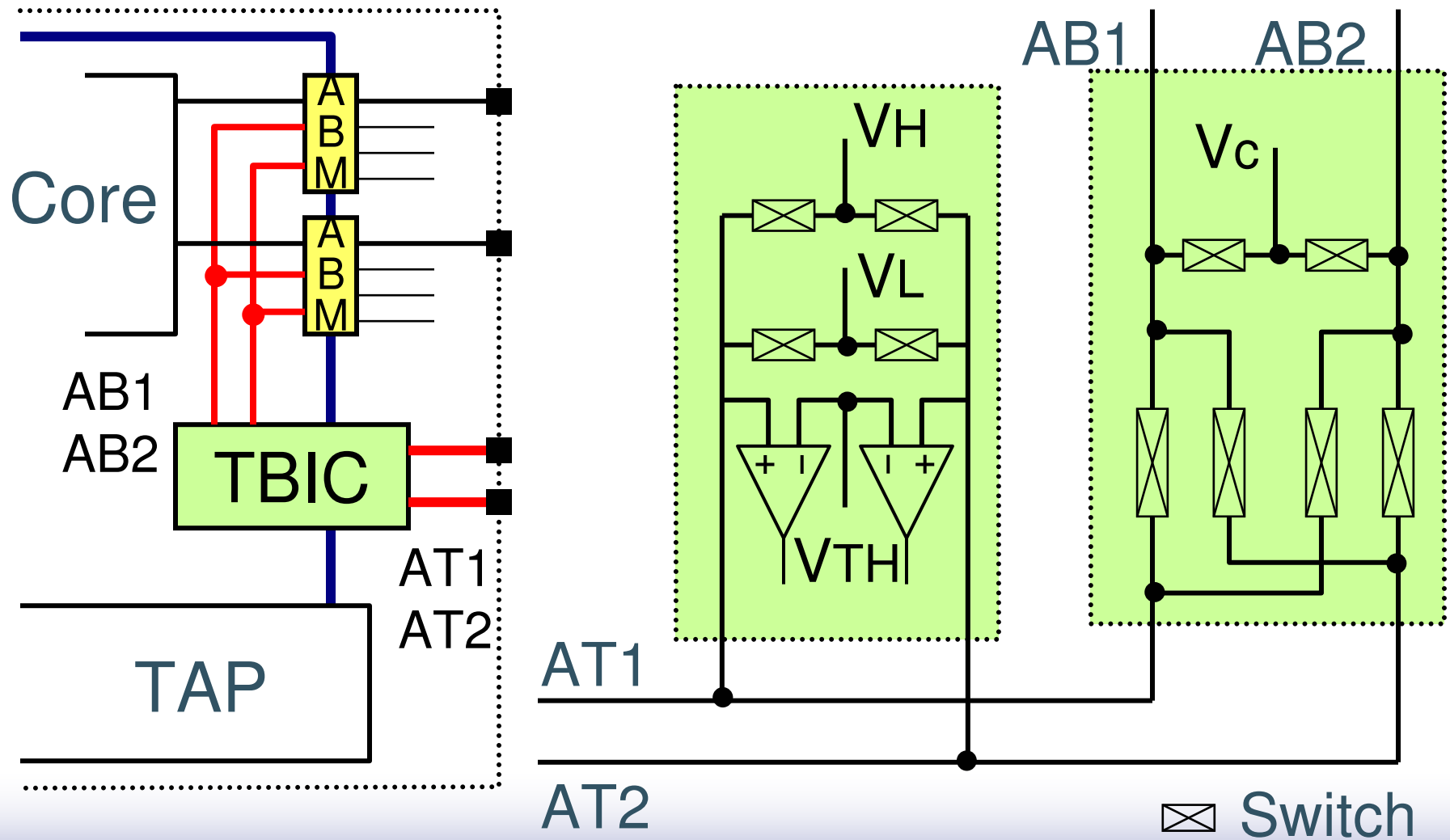

# IEEE 1149.4 - ABM

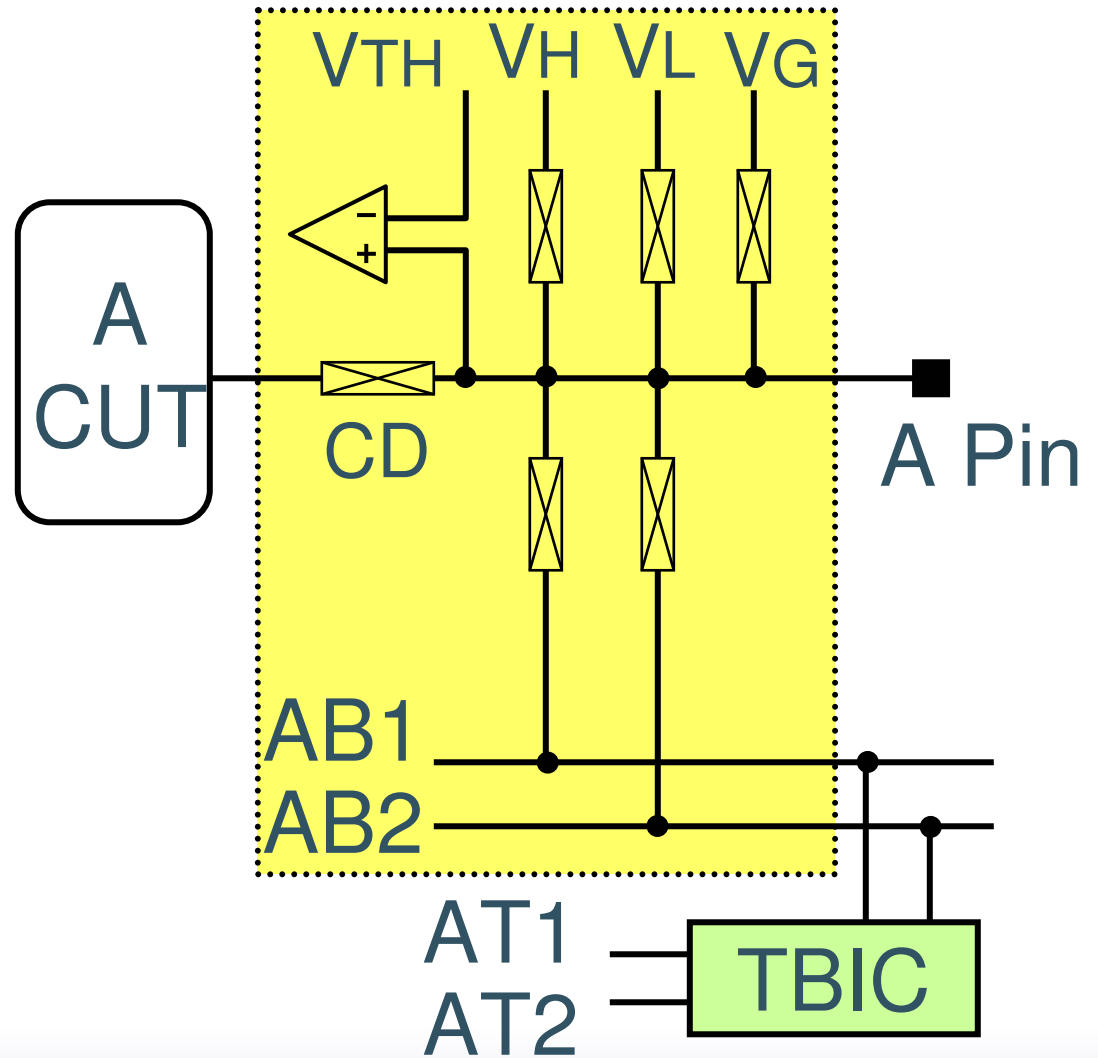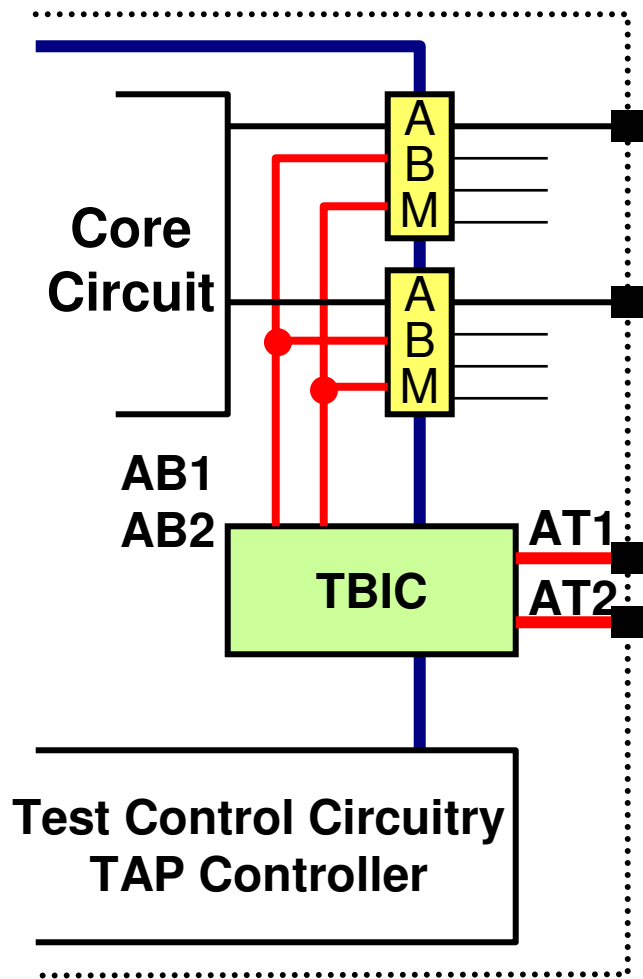

# 1149.4 – Mixed-Signal Architecture

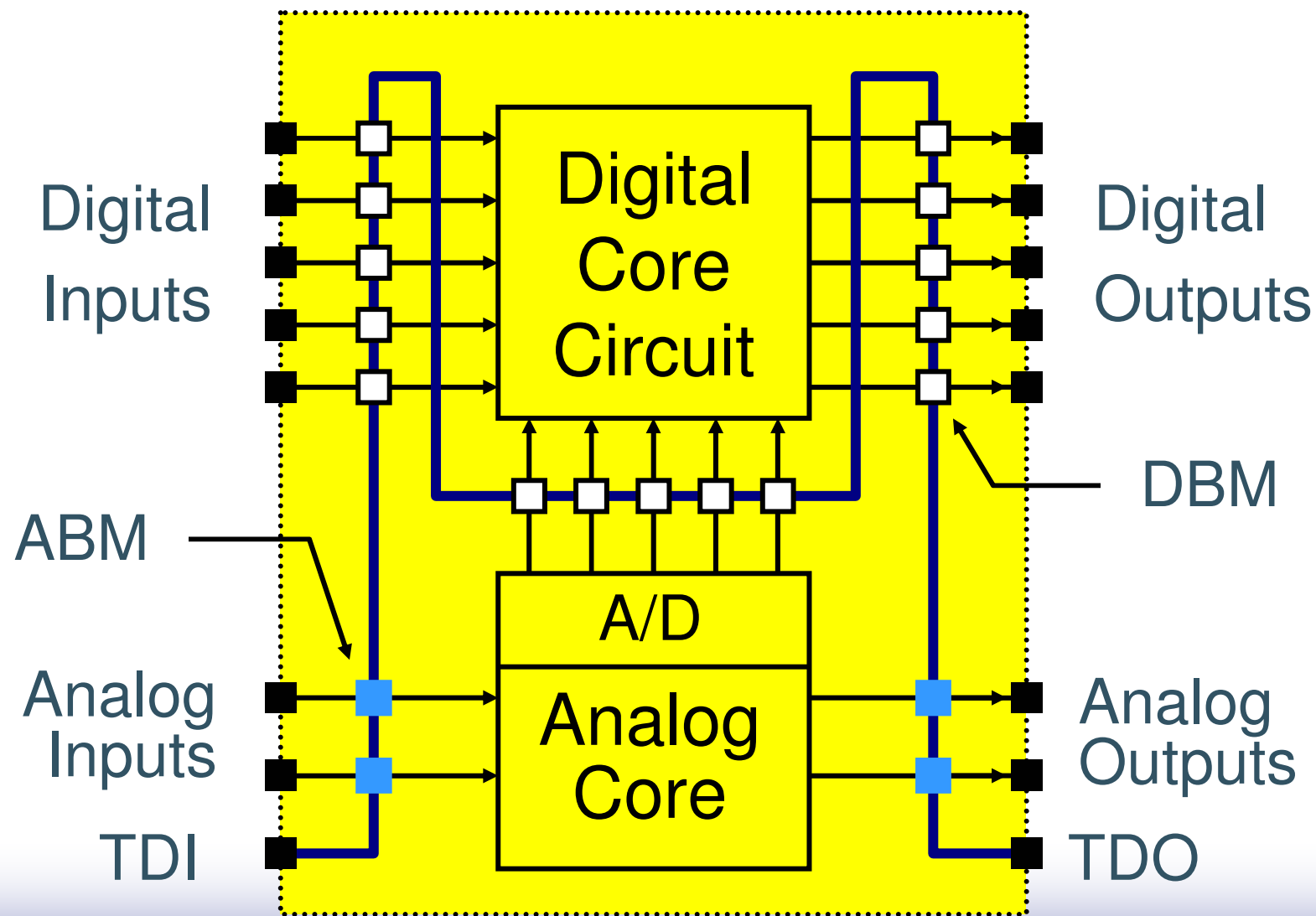

## ***11.4 IEEE Std. 1149.4 Standard for a Mixed-Signal Test Bus***

- IEEE Std. 1149.4 Overview
- IEEE Std. 1149.4 Circuit Structures
- **IEEE Std. 1149.4 Instructions**
- IEEE Std. 1149.4 Test Modes

# ***IEEE 1149.4 - Instructions***

- Mandatory Instructions
  - BYPASS
  - SAMPLE/PRELOAD
  - EXTEST
  - PROBE
- Same as IEEE 1149.1

# ***IEEE 1149.4 - Instructions***


- Optional Instructions
  - INTEST
  - IDCODE/USERCODE
  - RUNBIST
  - CLAMP
  - HIGHZ
- Same as IEEE 1149.1

## ***11.4 IEEE Std. 1149.4 Standard for a Mixed-Signal Test Bus***

- IEEE Std. 1149.4 Overview
- IEEE Std. 1149.4 Circuit Structures
- IEEE Std. 1149.4 Instructions
- **IEEE Std. 1149.4 Test Modes**




# 1149.4 – Open/Short Interconnect Test

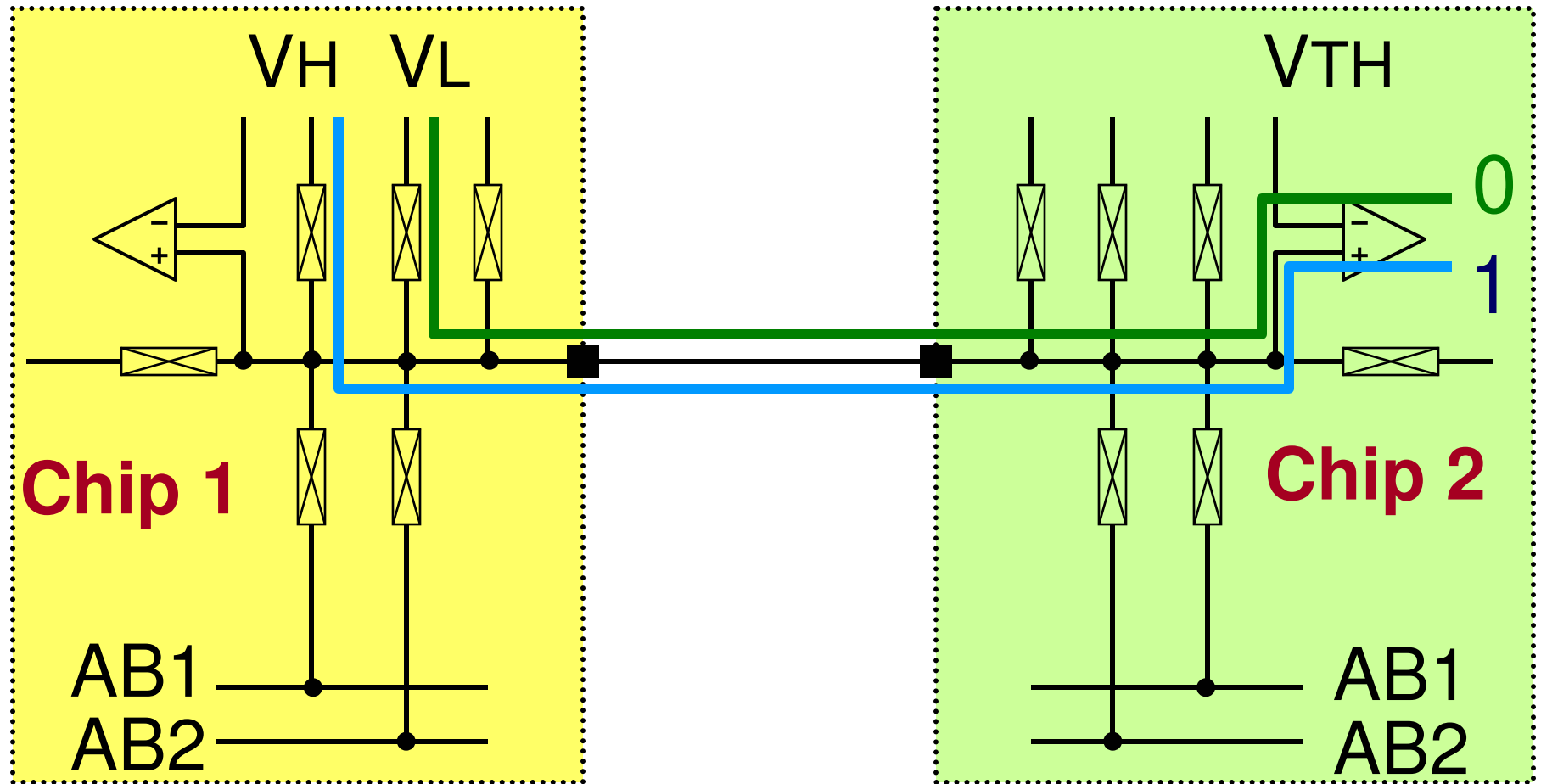
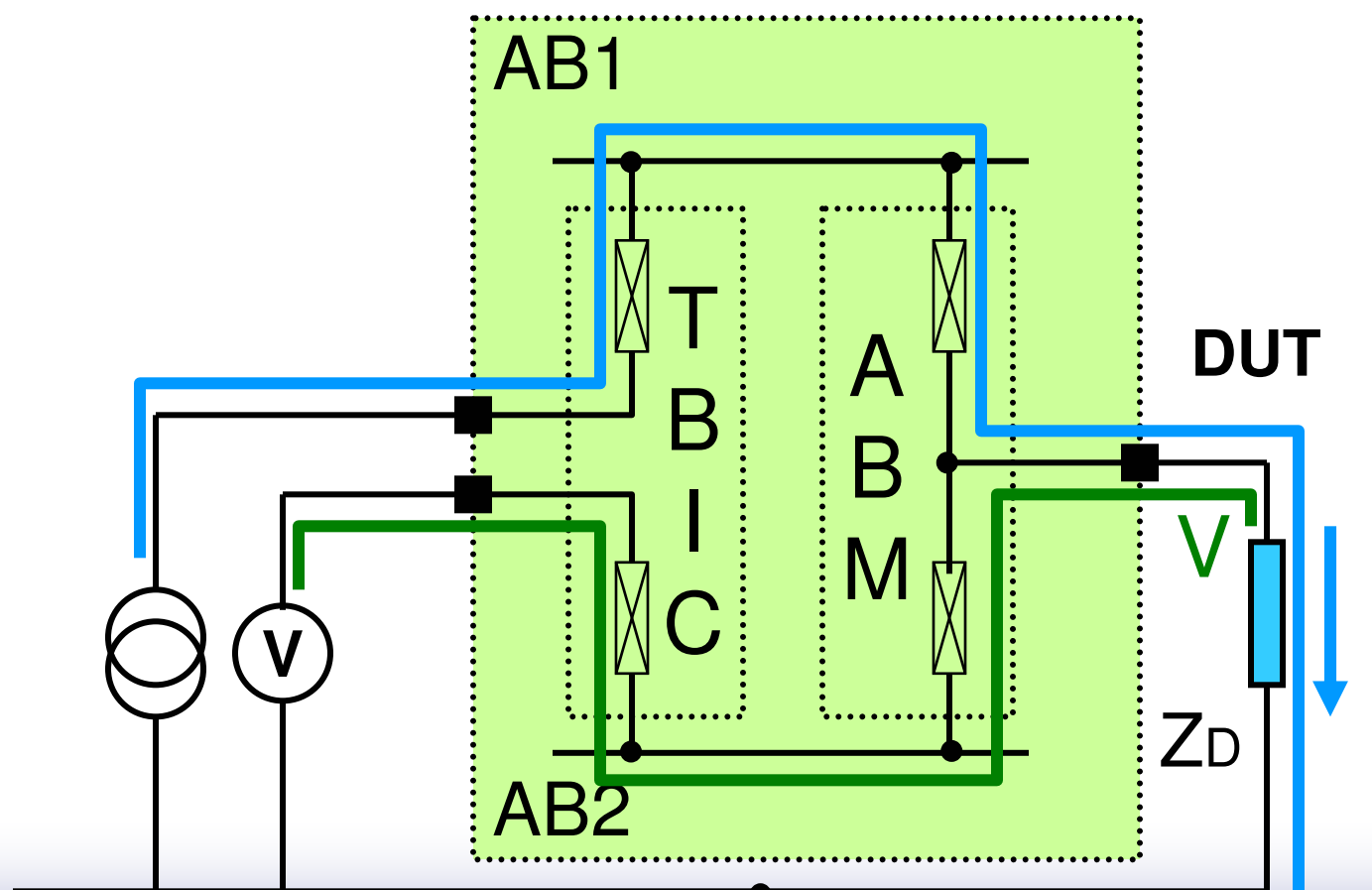
# 1149.4 – Extended Interconnect Test

- Grounded Impedance Measurement
- Apply current and measure voltage




# 1149.4 – Extended Interconnect Test

- Equivalent Circuit Model.


$$I_{DUT}(t) = I_s(t) \cdot \frac{R_{SIO}}{R_{SIO} + Z_{P1} + Z_{DUT}}$$
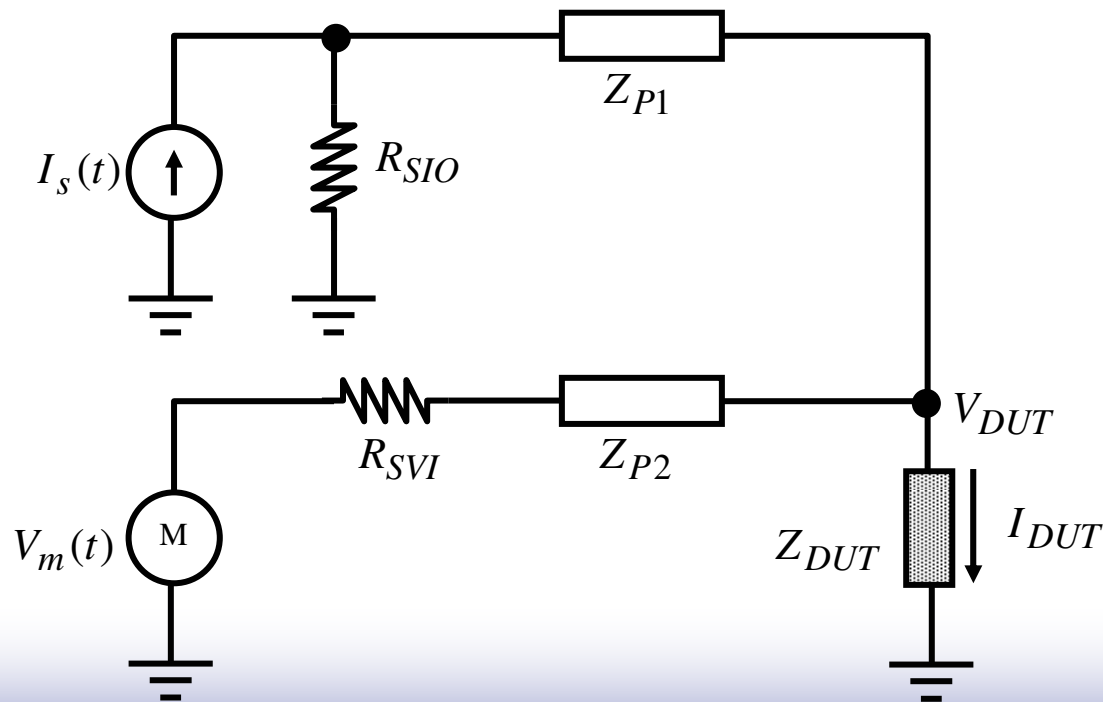
$$V_M(t) = V_{DUT}(t) \cdot \frac{R_{SVI}}{R_{SVI} + Z_{P2} + Z_{DUT}}$$




# 1149.4 – Extended Interconnect Test

- Floating Impedance  $Z_D$  Measurement

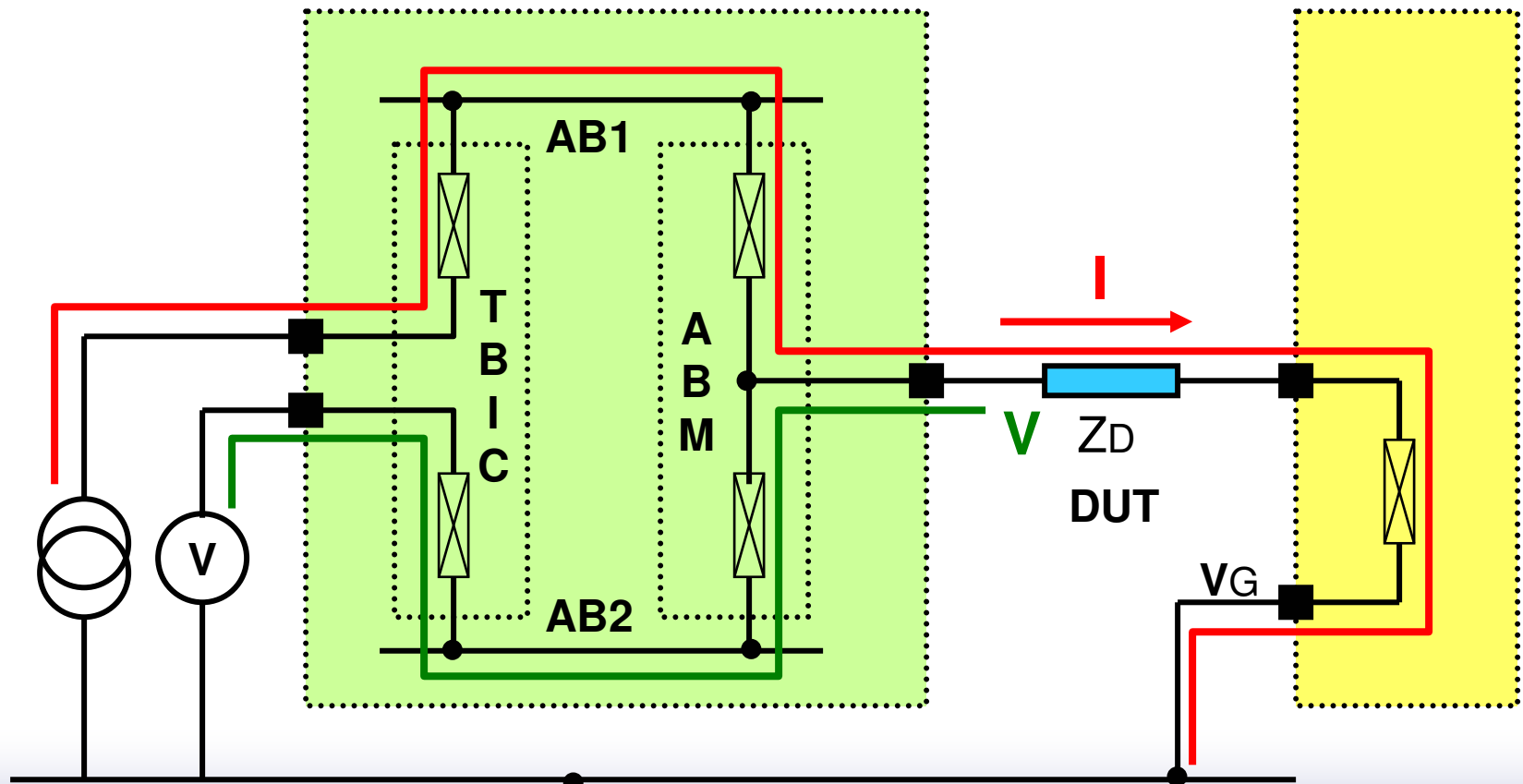

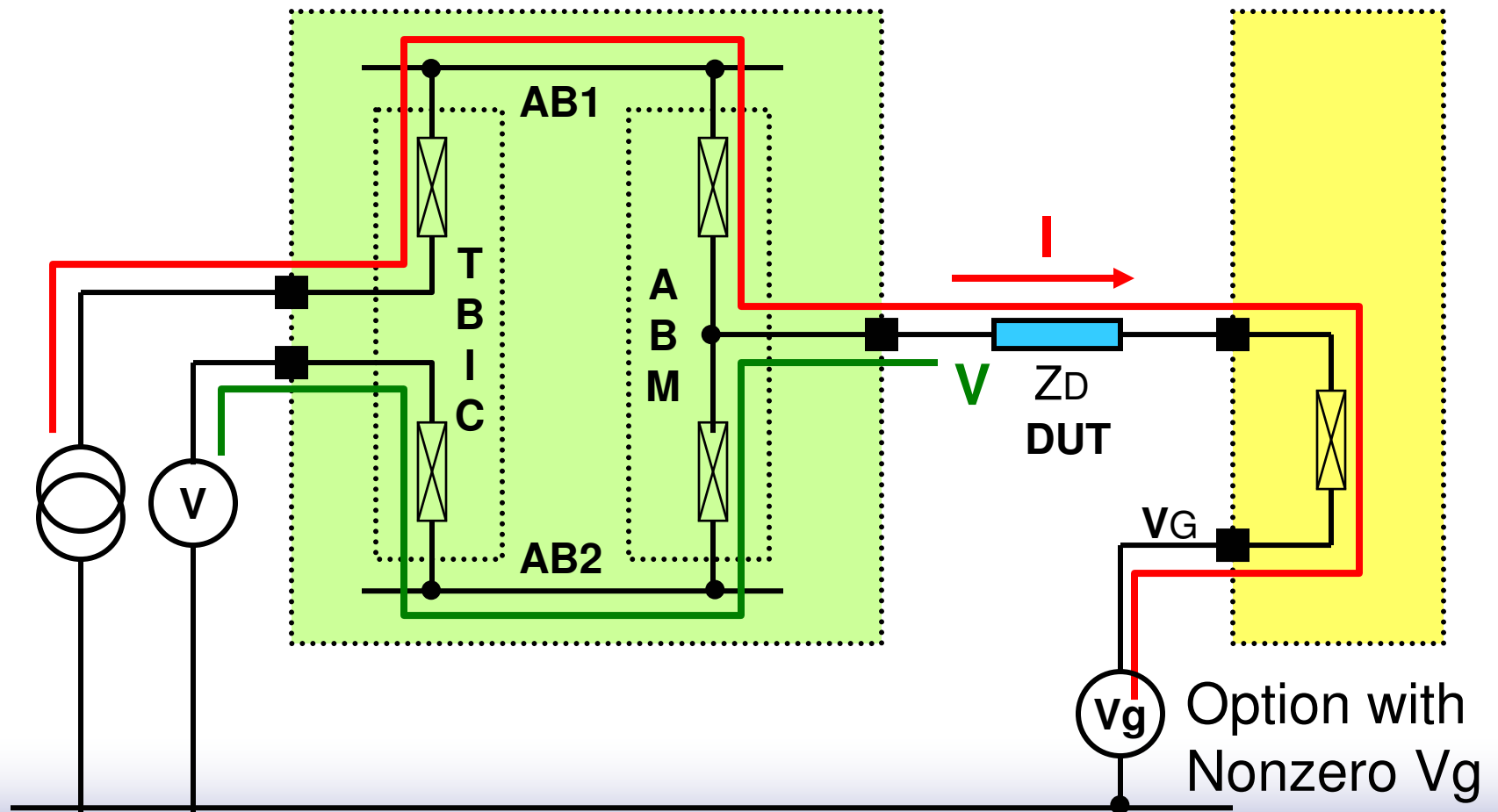
# 1149.4 – Extended Interconnect Test

- Floating Impedance  $Z_D$  with optional  $V_g$



# 1149.4 – Extended Interconnect Test

- Apply voltage and measure current

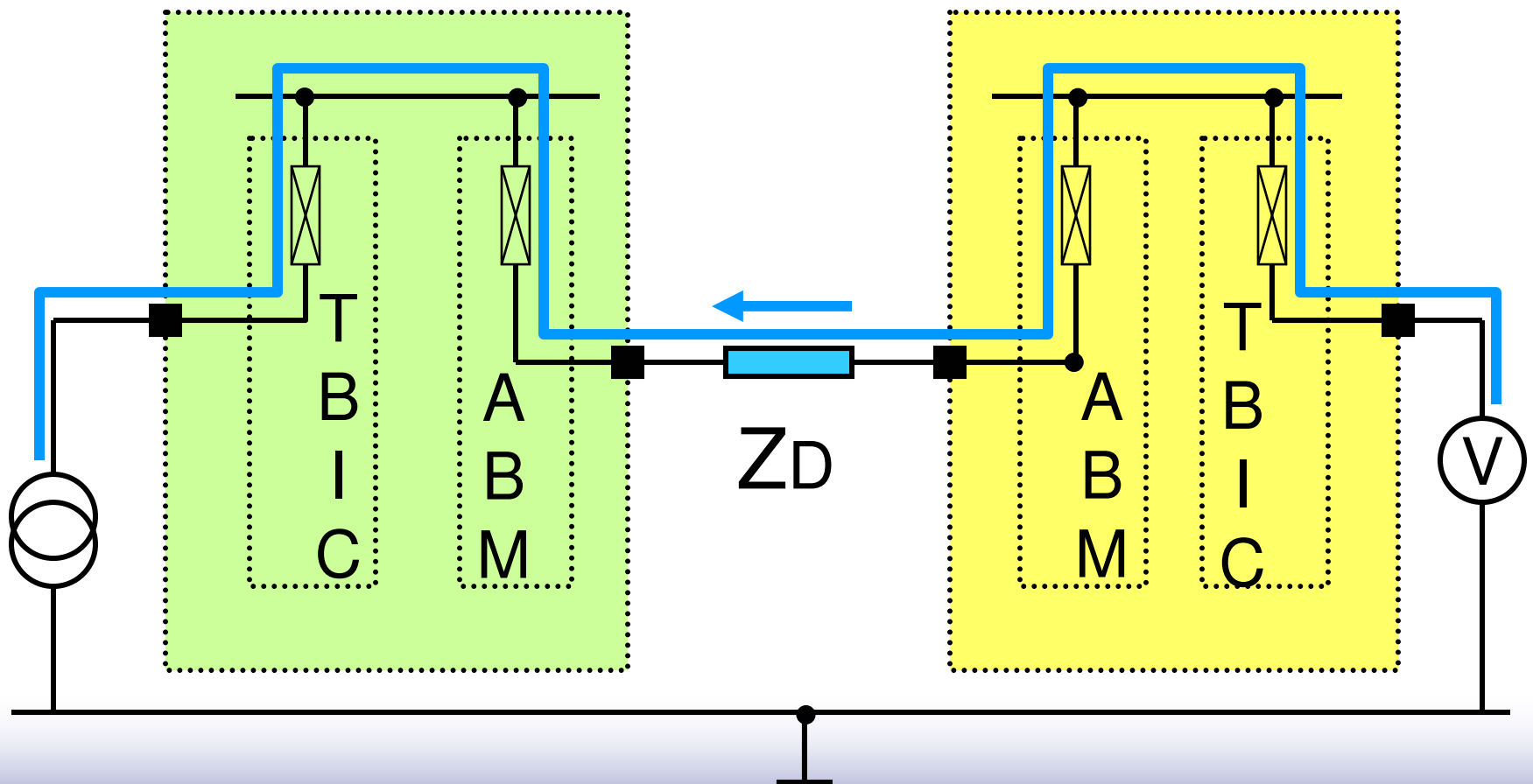

# 1149.4 – Extended Interconnect Test

- Equivalent Circuit Model


$$V_{DUT}(t) = V_s(t) \cdot \frac{Z_{DUT}}{R_{SVO} + Z_{P1} + Z_{DUT} + Z_{P2} + R_{SII}}$$

$$I_m(t) = \frac{V_s(t)}{R_{SVO} + Z_{P1} + Z_{DUT} + Z_{P2} + R_{SII}}$$

**With Ideal Voltage Source  
and Current Meter**


$$V_{DUT}(t) = V_s(t) \cdot \frac{Z_{DUT}}{Z_{P1} + Z_{DUT} + Z_{P2}}$$
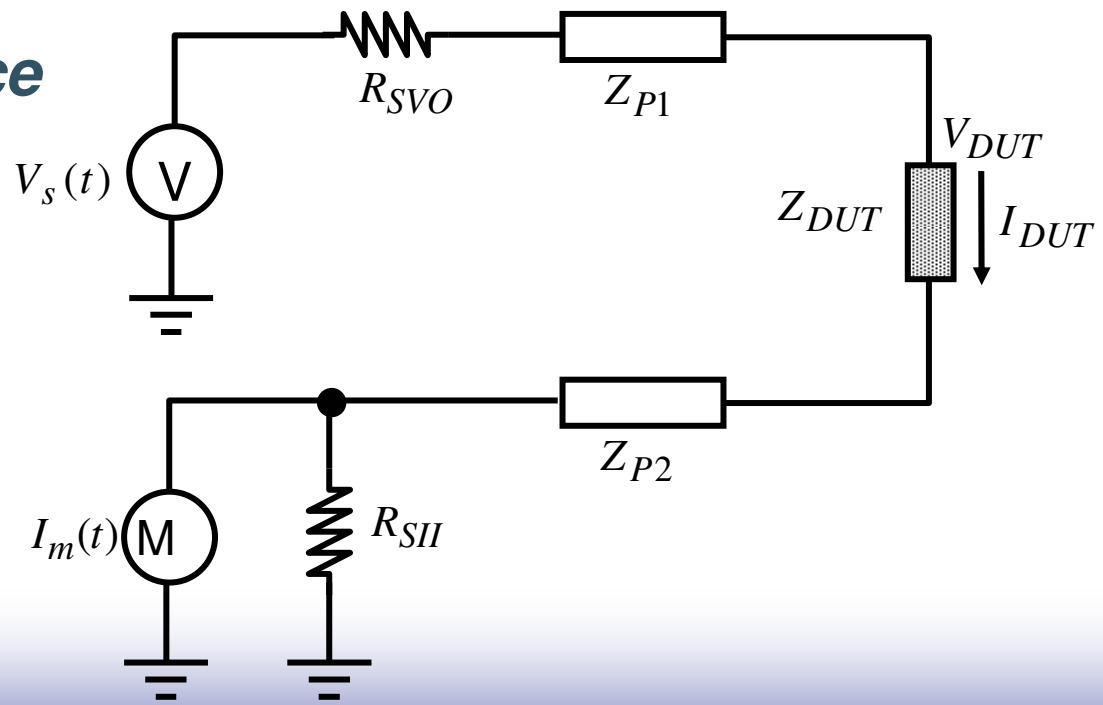
$$I_m(t) = \frac{V_s(t)}{Z_{P1} + Z_{DUT} + Z_{P2}}$$




# 1149.4 – Extended Interconnect Test

- Measure complex interconnect network

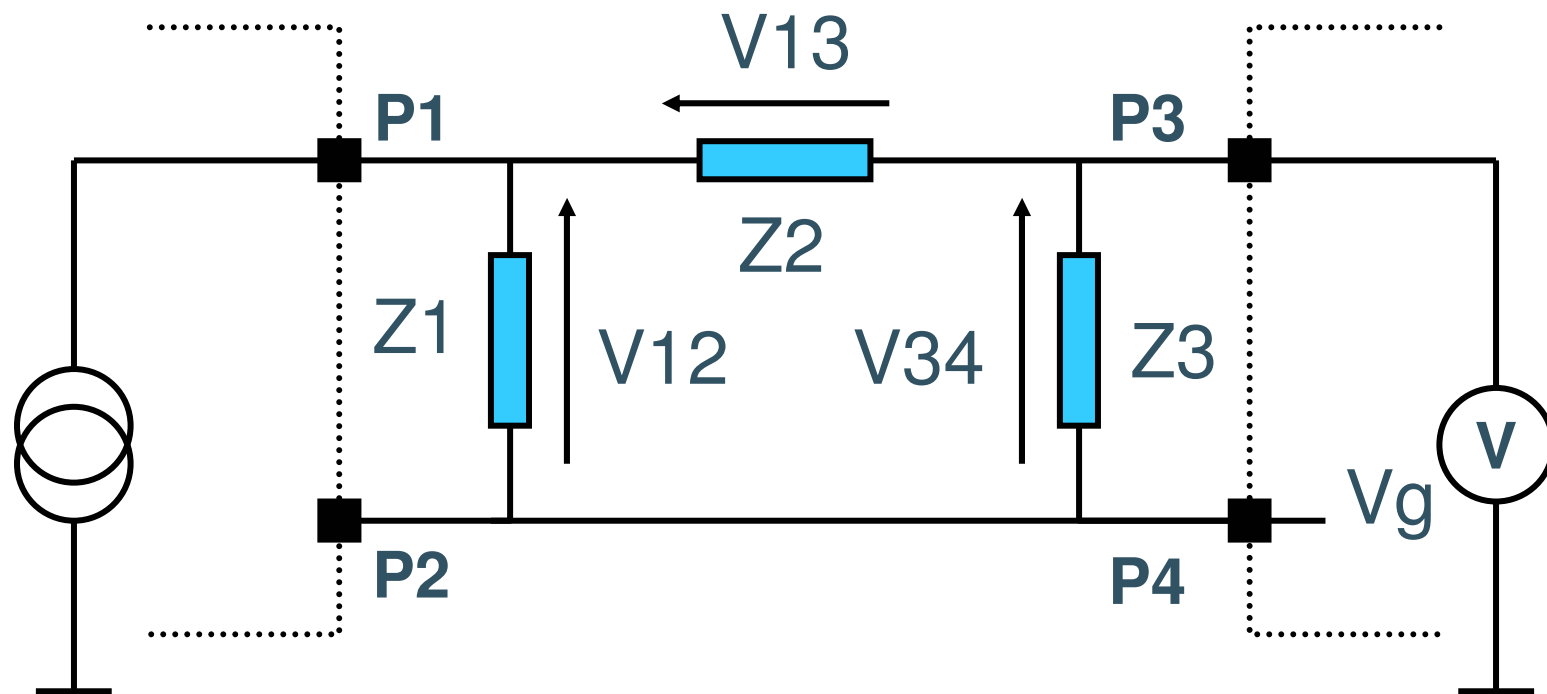



# 1149.4 – Extended Interconnect Test

 

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$


$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

| H         | P1                | P2  | P3                  | P4  |
|-----------|-------------------|-----|---------------------|-----|
| h11       | Is/Vm             | GND | GND                 | GND |
| h12       | Vm                | GND | Vs                  | GND |
| h21       | Is                | GND | Im                  | GND |
| h22       | Open              | GND | Vs/Im               | GND |
| Notations | Is: Apply Current |     | Vm: Measure Voltage |     |
|           | Vs: Apply Voltage |     | Im: Measure Current |     |

# 1149.4 - High Speed Applications

- Use buffers for better frequency response

- ▶ Current Buffer
- ▶ Voltage Buffer

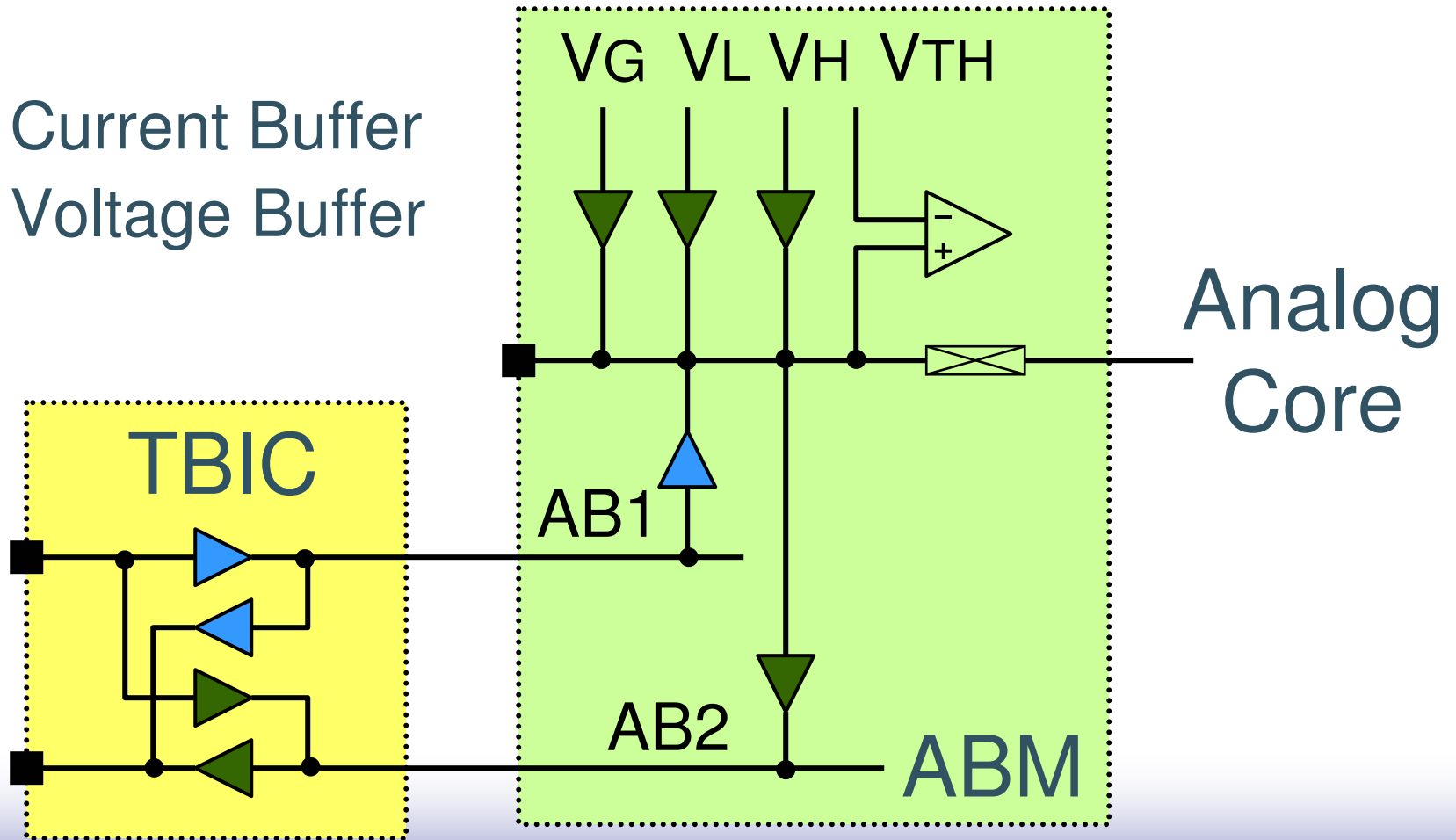

## ***11.5 Concluding Remarks***

- ❑ AMS testing requires specialized approaches and experienced engineers because of the large varieties of signals, functions and circuits.
- ❑ DSP approaches are so pervasive that even basic analog test items can be accomplished.
- ❑ IEEE 1057 with formal terminologies and standardized test methods provides a solid theoretical background for ADC/DAC testing.
- ❑ IEEE 1149.4 is one solution to extending and incorporating the digital counterpart.